
ECE 4514 Digital Design II Spring 2008

Behavioral Modeling: Non-blocking assignments

A Language Lecture

Patrick Schaumont

Today

- ❑ First part on writing *behavioral models* - models which make use of more advanced constructs to design always and initial blocks
- ❑ Today: Introduce *non-blocking procedural assignments*
- ❑ The first 20 minutes of this lecture are really important

***Pay Attention Now
.. it will earn itself back later***


The assignment statements so far

	Continuous Assignment	Procedural Assignment
Operation	=	=
Where	using stand-alone <i>assign</i> statement	inside of <i>always</i> and <i>initial</i>
Example	<pre>wire q; reg a, b; assign q = a & b;</pre>	<pre>wire q; reg a, b; always @(b) a = b + 5;</pre>
Valid LHS	net (wire)	reg
Valid RHS	expression of net or reg	expression of net or reg
Evaluated	when any part of RHS changes	procedural execution

What is 'procedural execution' ?


- ❑ An always block is either executing, or it is waiting for an event from its sensitivity list
- ❑ When it is executing, it proceeds in a sequential fashion through the statements of the code, until it runs into an *event control statement* (@, wait, #)
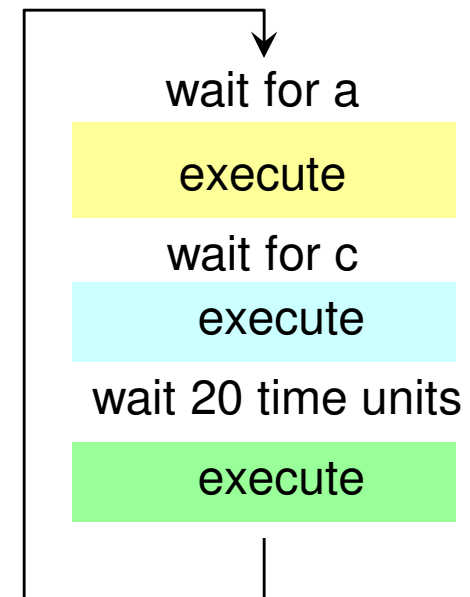
```
always begin  
  @(upedge a);  
  b = a + 1;  
  wait (c == 3);  
  #20 b = a + 1;  
end
```



What is 'procedural execution' ?

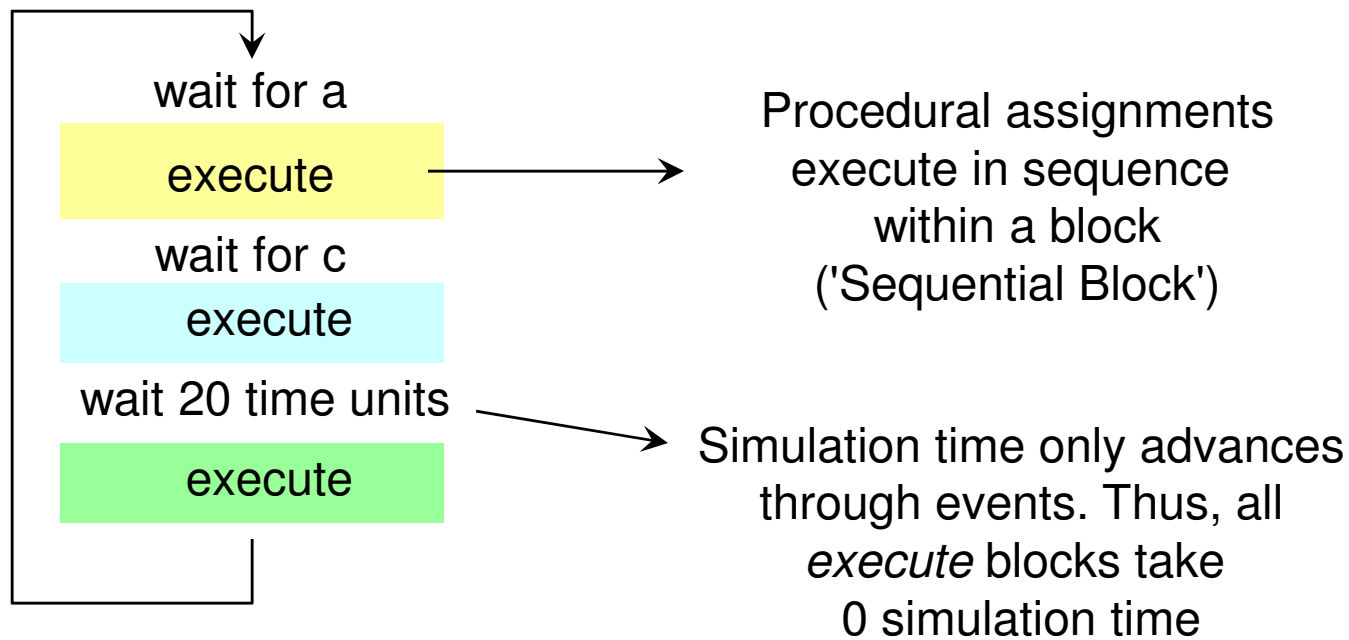- ❑ An always is either executing, or it is waiting for an event from its *sensitivity list*
- ❑ When it is executing, it proceeds in a sequential fashion through the statements of the code, until it runs into an *event control statement* (@, wait, #)



The assignment statements so far

	Continuous Assignment	Procedural Assignment
Operation	=	=
Wire	net (wire)	reg
Example	<code>a = b + 5;</code>	<code>a = b + 5;</code>
Valid LHS	net (wire)	reg
Valid RHS	expression of net or reg	expression of net or reg
Evaluated	when any part of RHS changes	procedural execution

The full name of this assignment is:
Procedural *Blocking* Assignment

Procedural Blocking Assignment

- ❑ Execution in a sequential block cannot complete without the assignment being complete

```
reg [7:0] a, b;  
always @(posedge clk) begin  
    a = b + 2;  
    b = a * 3;  
end
```

Blocking assignment:

assignment on *a* MUST complete before
assignment on *b* can start

Procedural Blocking Assignment

- ❑ Execution in a sequential block cannot complete without the assignment being complete

```
reg [7:0] a, b;  
always @(posedge clk) begin  
    #10 a = b + 2;  
    b = a * 3;  
end
```

1. **Wait 10;**
2. Read value of b and add 2 to it;
3. Assign the result to a;
4. Read the value of a and multiply by three;
5. Assign the result to b;

Procedural Blocking Assignment

- ❑ Execution in a sequential block cannot complete without the assignment being complete

```
reg [7:0] a, b;  
always @(posedge clk) begin  
    a = #10 b + 2;  
    b = a * 3;  
end
```

1. Read value of b and add 2 to it;
2. **Wait 10;**
3. Assign the result to a;
4. Read the value of a and multiply by three;
5. Assign the result to b;

Procedural Blocking Assignment

- ❑ Execution in a sequential block cannot complete without the assignment being complete

```
reg [7:0] a, b;  
always @(posedge clk) begin  
    #5 a = #10 b + 2;  
    #5 b = a * 3;  
end
```

1. **Wait 5;**
2. Read value of b and add 2 to it;
3. **Wait 10;**
4. Assign the result to a;
5. **Wait 5;**
6. Read the value of a and multiply by three;
7. Assign the result to b;

Procedural Blocking Assignment

- ❑ Execution in a sequential block cannot complete without the assignment being complete

*Blocking Assignment means
a will always be assigned before b*

```
reg [7:0] a, b;  
always @(posedge clk) begin  
    #5 a = #10 b + 2;  
    #5 b = a * 3;  
end
```

1. **Wait 5;**
2. Read value of b and add 2 to it;
3. **Wait 10;**
4. **Assign the result to a;**
5. **Wait 5;**
6. Read the value of a and multiply by three;
7. **Assign the result to b;**

Procedural Non-Blocking Assignment

	Continuous Assignment	Proc. Blocking Assignment	Proc. Non-Blocking Assignment
Operation	=	=	<=
Where	using stand-alone <i>assign</i> statement	inside of <i>always</i> and <i>initial</i>	inside of <i>always</i> and <i>initial</i>
Example	<pre>wire q; reg a, b; assign q = a & b;</pre>	<pre>wire q; reg a, b; always @(b) a = b + 5;</pre>	<pre>wire q; reg a, b; always @(b) a <= 5;</pre>
Valid LHS	net (wire)	reg	reg
Valid RHS	expression of net or reg	expression of net or reg	expression of net or reg
Evaluated	when any part of RHS changes	procedural execution	at the end of current time step

What does 'at the end of current time step' mean?

- The simulator processes all the events with a given timestamp according to the nature of the event

Given the set of evaluate-events at time T

First, do the following (in any order)

Evaluate the RHS of *all* assignments

Assign the LHS of all procedural blocking assignments

Assign the LHS of all continuous assignments

Evaluate inputs and outputs of all primitives (gates)

Print \$display statements

Then, do the following (in any order)

Change the LHS of all nonblocking assignments

Then, do the following (in any order)

Print \$monitor statements

What does 'at the end of current time step' mean?

- ❑ The simulator processes all the events with a given timestamp according to the nature of the event

Given the set of evaluate-events at time T

First, do the following (in any order)

So, it looks like non-blocking assignments can 'split' a given point in time in two

Evaluate the RHS of *all* assignments
Assign the LHS of all procedural blocking assignments
Assign the LHS of all continuous assignments
Evaluate inputs and outputs of all primitives (gates)
Print \$display statements

Then, do the following (in any order)

Change the LHS of all nonblocking assignments

Then, do the following (in any order)

Print \$monitor statements

Effect of a non-blocking statement

Blocking

```
reg [7:0] a, b;
```

```
initial b = 0;
```

```
initial a = 4;
```

```
always @(a or b)
```

```
begin
```

```
    a = b + 2;
```

```
    b = a * 3;
```

```
end
```

Non-Blocking

```
reg [7:0] a, b;
```

```
initial b = 0;
```

```
initial a = 4;
```

```
always @(a or b)
```

```
begin
```

```
    a <= b + 2;
```

```
    b <= a * 3;
```

```
end
```

Effect of a non-blocking statement

Blocking

```
reg [7:0] a, b;
```

```
initial b = 0;
```

```
initial a = 4;
```

```
always @(a or b)
```

```
begin
```

```
    a = b + 2;
```

```
    b = a * 3;
```

```
end
```

$$a = 0 + 2 = 2$$

$$b = 2 * 3 = 6$$

Non-Blocking

```
reg [7:0] a, b;
```

```
initial b = 0;
```

```
initial a = 4;
```

```
always @(a or b)
```

```
begin
```

```
    a <= b + 2;
```

```
    b <= a * 3;
```

```
end
```

$$a = 0 + 2 = 2$$

$$b = 4 * 3 = 12$$

Effect of a non-blocking statement

Blocking

```
reg [7:0] a, b;
```

```
initial b = 0;
```

```
ini
```

```
always @(a or b)
```

```
begin
```

```
  a = b + 2;
```

```
  b = a * 3;
```

```
end
```

$$a = 0 + 2 = 2$$

$$b = 2 * 3 = 6$$

Non-Blocking

```
reg [7:0] a, b;
```

```
initial b = 0;
```

```
ini
```

```
always @(a or b)
```

```
begin
```

```
  a <= b + 2;
```

```
  b <= a * 3;
```

```
end
```

$$a = 0 + 2 = 2$$

$$b = 4 * 3 = 12$$

*Non-Blocking Assignment means
a and b are updated at the same time*

Another example



Using blocking assignments:


```
module fsm_mod(q1, q0, in, clk);
    output q1, q0;
    input clk, in;
    reg q1, q0;

    always @(posedge clk) begin
        q1 = in;
        q0 = in | q1;
    end
endmodule
```

Another example

Using blocking assignments:


```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input  clk, in;  
    reg   q1, q0;  
  
    always @(posedge clk) begin  
        q1 = in;  
        q0 = in | q1;  
    end  
endmodule
```

 

Another example

Using blocking assignments:


```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input clk, in;  
    reg q1, q0;  
  
    always @(posedge clk) begin  
        q1 = in;  
        q0 = in | q1;  
    end  
endmodule
```

 

Another example

Using non-blocking assignments:


```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input clk, in;  
    reg q1, q0;  
  
    always @(posedge clk) begin  
        q1 <= in;  
        q0 <= in | q1;  
    end  
endmodule
```

 

Another example

Using non-blocking assignments:





```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input  clk, in;  
    reg   q1, q0;  
  
    always @(posedge clk) begin  
        q1 <= in;  
        q0 <= in | q1;  
    end  
endmodule
```

 

Think about the *meaning* of this behavior


```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input clk, in;  
    reg q1, q0;  
  
    always @(posedge clk) begin  
        q1 = in;  
        q0 = in | q1;  
    end  
end  
endmodule
```

```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input clk, in;  
    reg q1, q0;  
  
    always @(posedge clk) begin  
        q1 <= in;  
        q0 <= in | q1;  
    end  
end  
endmodule
```

    


Think about the *meaning* of this behavior

```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input clk, in;  
    reg q1, q0;  
  
    always @(posedge clk) begin  
        q1 = in;  
        q0 = in | q1;  
    end  
endmodule
```

 

```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input clk, in;  
    reg q1, q0;  
  
    always @(posedge clk) begin  
        q1 <= in;  
        q0 <= in | q1;  
    end  
endmodule
```

 

Non-blocking assignments for registers

- ❑ Non-blocking assignments are used to model registers in a consistent fashion in the context of an always block
 - A single reg variable used to express register
 - Writing to the variable (using `<=`) means connecting to the register input
 - Reading from the variable means connecting to the register output

- ❑ More compact than gate-level model of a register

- ❑ More compact than the 'multiplexed datapath' method (with wire/reg combo)

Another example: A chain of 3 registers

```
module chain(q, i, clk);
    output q;
    input i, clk;

    reg q, q1, q2;

    always @(posedge clk) begin
        q <= q1;
        q1 <= q2;
        q2 <= i;
    end
endmodule
```

Another example: A chain of 3 registers

```
module chain(q, i, clk);  
  output q;  
  input i, clk;  
  
  reg q, q1, q2;  
  
  always @(posedge clk) begin  
    q <= q1;  
    q1 <= q2;  
    q2 <= i;  
  end  
endmodule
```

```
q <= q1;  
q1 <= q2;  
q2 <= i;
```

all of these have the same behavior

```
q1 <= q2;  
q <= q1;  
q2 <= i;
```

```
q2 <= i;  
q1 <= q2;  
q <= q1;
```

Another example: A chain of 3 registers

□ Mux-datapath method:

```
module chain(q, i, clk);
    output q;
    input i, clk;

    reg q, q1, q2;
    wire q_next, q1_next, q2_next;

    always @(posedge clk) begin
        q = q_next;
        q1 = q1_next;
        q2 = q2_next;
    end

    assign q_next = q1;
    assign q1_next = q2;
    assign q2_next = i;

endmodule
```


Another example: A chain of 3 registers

□ Structural method:

```
module flipflop(q, i, clk);  
    output q;  
    input i, clk;  
    // implementation of flipflop ..  
endmodule
```

```
module chain(q, i, clk);  
    output q;  
    input i, clk;  
  
    wire q1, q2;  
  
    flipflop F1(q, q1, clk);  
    flipflop F2(q1, q2, clk);  
    flipflop F3(q2, i, clk);  
  
endmodule
```

Non-blocking assignments in a nutshell:

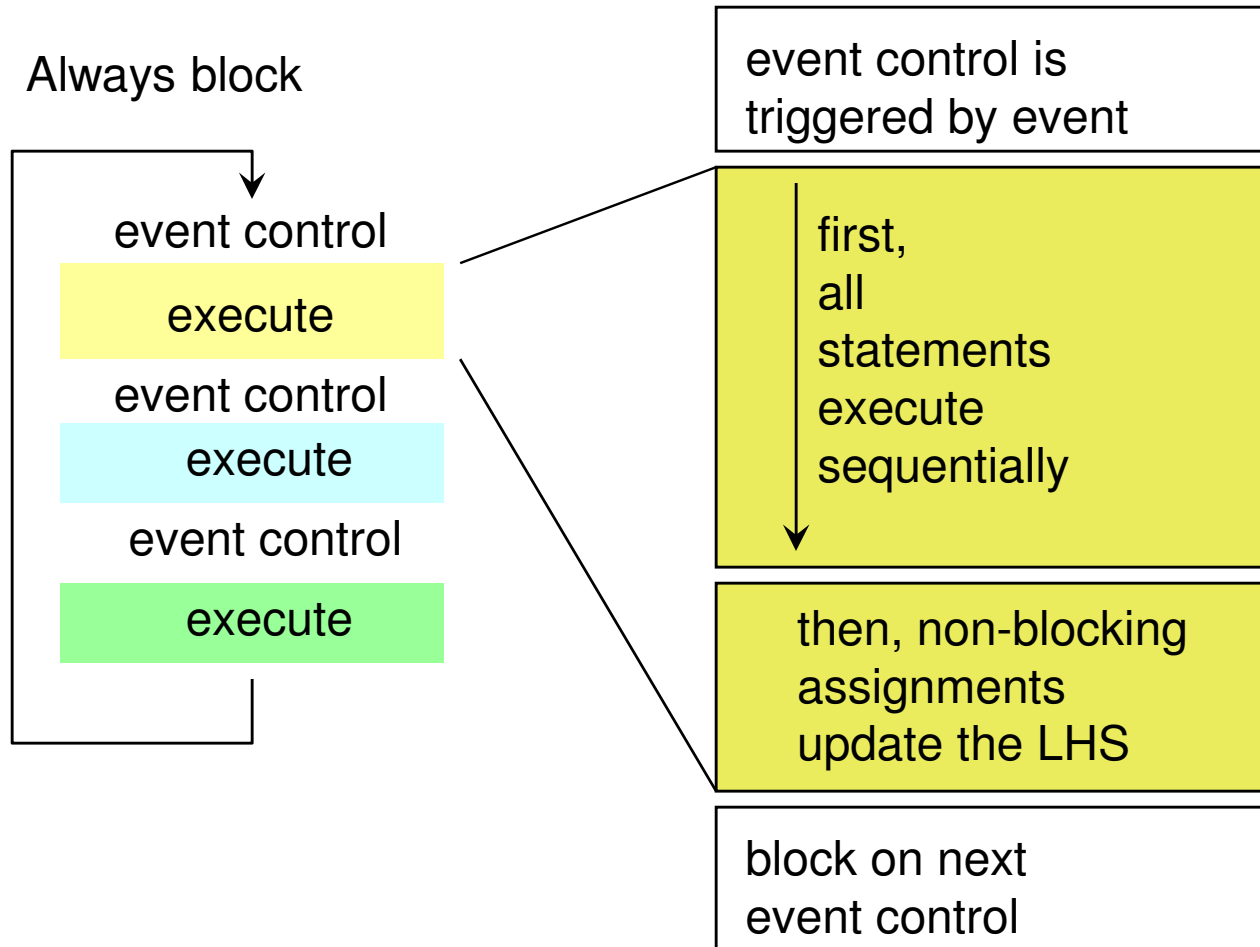

Delays and non-blocking assignments

```
initial
begin
    a = 1;
    #5 b = a + 1;
end
```

```
initial
begin
    a <= 1;
    #5 b <= a + 1;
end
```

Delays and non-blocking assignments

initial

begin

a = 1;

#5 b = a + 1;

end

t = 0: assign a with 1

t = 5: evaluate a + 1 and assign b

initial

begin

a <= 1;

#5 b <= a + 1;

end

t = 0: assign a with 1 at the end of timestep 0

t = 5: evaluate a + 1 and assign b at the
end of timestep 5

Can avoid indeterminate results !

```
initial
```

```
  a = 0;
```

```
initial
```

```
  #5 a = a + 1;
```

```
initial
```

```
  #5 b = a + 1;
```

```
initial
```

```
  a = 0;
```

```
initial
```

```
  #5 a <= a + 1;
```

```
initial
```

```
  #5 b <= a + 1;
```

Can avoid indeterminate results !

initial

a = 0;

initial

#5 a = a + 1;

t = 5: a is assigned with 6

initial

#5 b = a + 1;

t = 5: b is indeterminate, because a changes at t=5 using a blocking assignment

initial

a = 0;

initial

#5 a <= a + 1;

t = 5: a is assigned with 6 *at the end of t=5*


initial

#5 b <= a + 1;

t = 5: b assigned with 6 *at the end of t = 5*


We can use intra-assignment delay, too
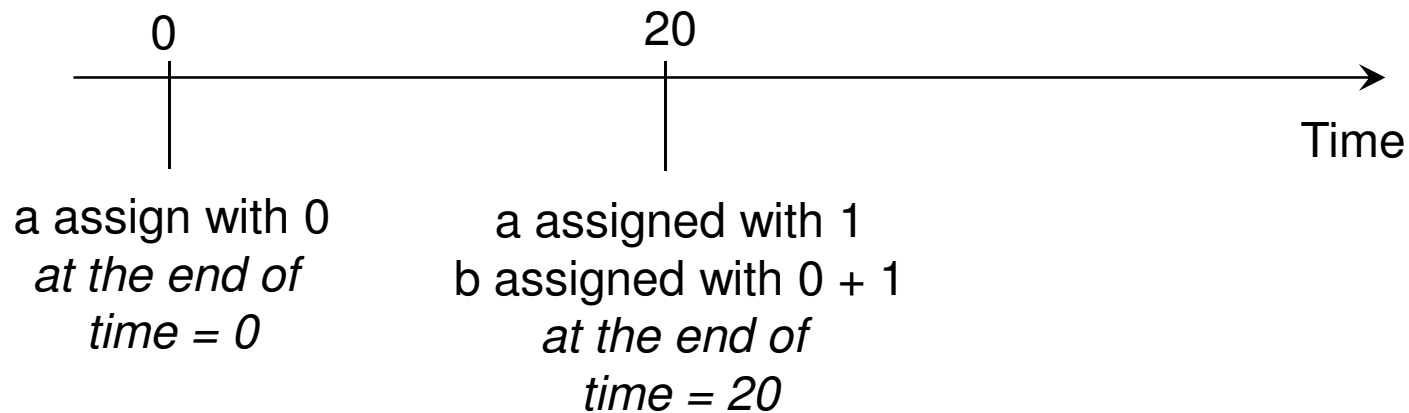
```
initial
begin
  a <= 0;
  #20 a <= 1;
      b <= a + 1;
end
```



We can use intra-assignment delay, too

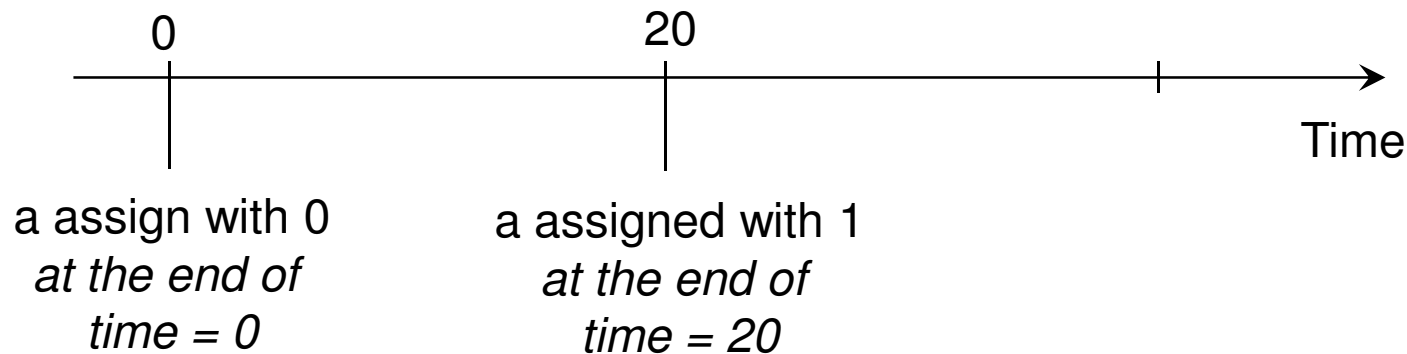
```
initial
begin
  a <= 0;
  #20 a <= 1;
      b <= #20 a + 1;
end
```



We can use intra-assignment delay, too

```
initial
begin
a <= 0;
#20 a <= 1;
    b <= #20 a + 1;
end
```

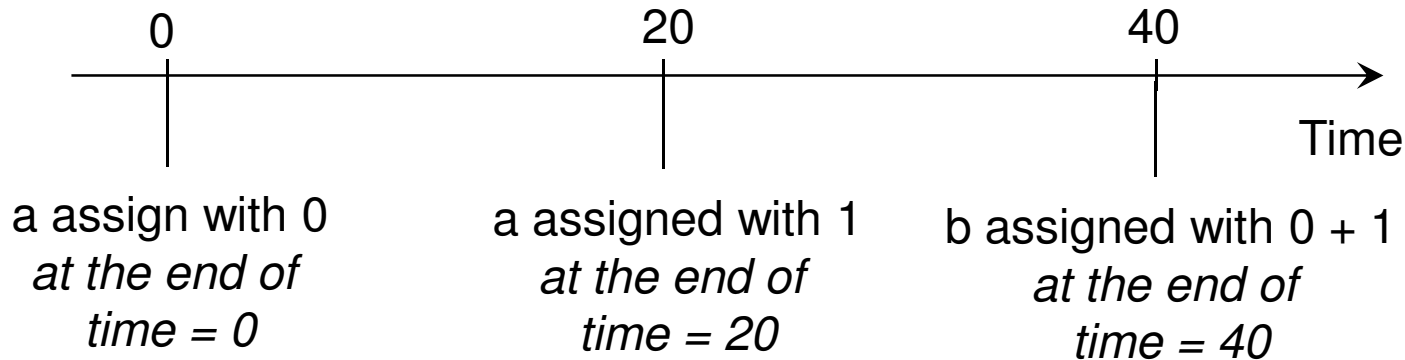
- 1) This is one 'sequential block'
- 2) All these statements will execute at time t = 20.
- 3) b will only be assigned at the end of time = 40



We can use intra-assignment delay, too

```
initial
begin
  a <= 0;
  #20 a <= 1;
      b <= #20 a + 1;
      c <= #20 b + 1;
end
```

When is c assigned?

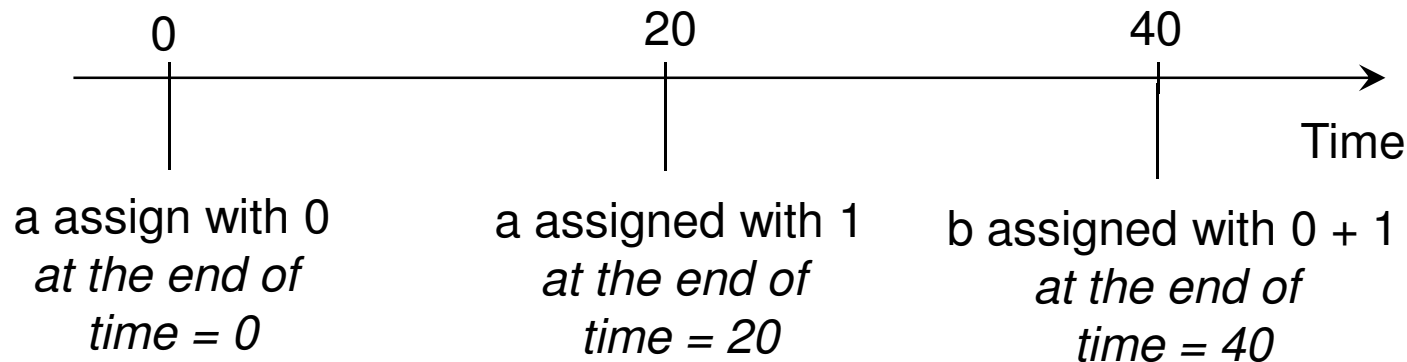

**c assigned with (b-value @20)
at the end of time = 40**

Summary of non-blocking assignments

- ❑ Commonly used to model registers in always blocks
- ❑ Simulate the effect of multiple concurrent expressions
- ❑ We will use non-blocking assignments to design hardware modules, FSM, datapaths etc in a single always block.
- ❑ In practice DO NOT MIX non-blocking and blocking assignments in the same always block
- ❑ Further Reading:
 - Covered in part in Palnitkar Chapter 7
 - Covered in IEEE 1364 standard Chapter 9.2 (also, check out the examples)