

---


# **ECE 4514 Digital Design II Spring 2008**

## **Lecture 14: The Spartan 3E FPGA**

Patrick Schaumont

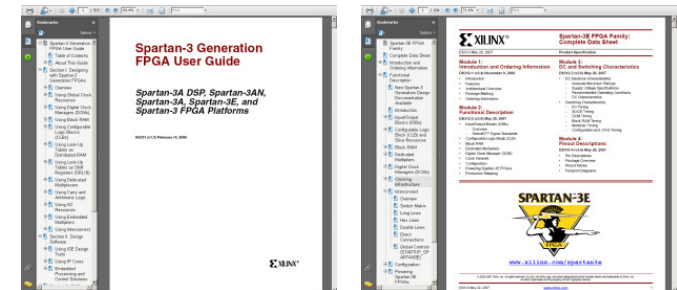
# FPGA Internals: The Spartan 3ES500 FPGA

- ❑ The internals of an FPGA
  - focus on the Spartan 3ES500 FPGA
- ❑ Objectives:
  - Understand how an FPGA can implement arbitrary circuits written in Verilog
  - Identify important metrics of FPGA capacity and features
  - Understand FPGA 'speak' used by design tools: LUT, LC, BRAM, DCM, IOB, ..
- ❑ Two important documents for the Spartan 3E FPGA
  - 'Spartan 3E Family Complete Datasheet'
  - 'Spartan 3 User Guide'



# Spartan 3


- 5 programmable elements in a regular network

 

DS912-1\_01\_032608

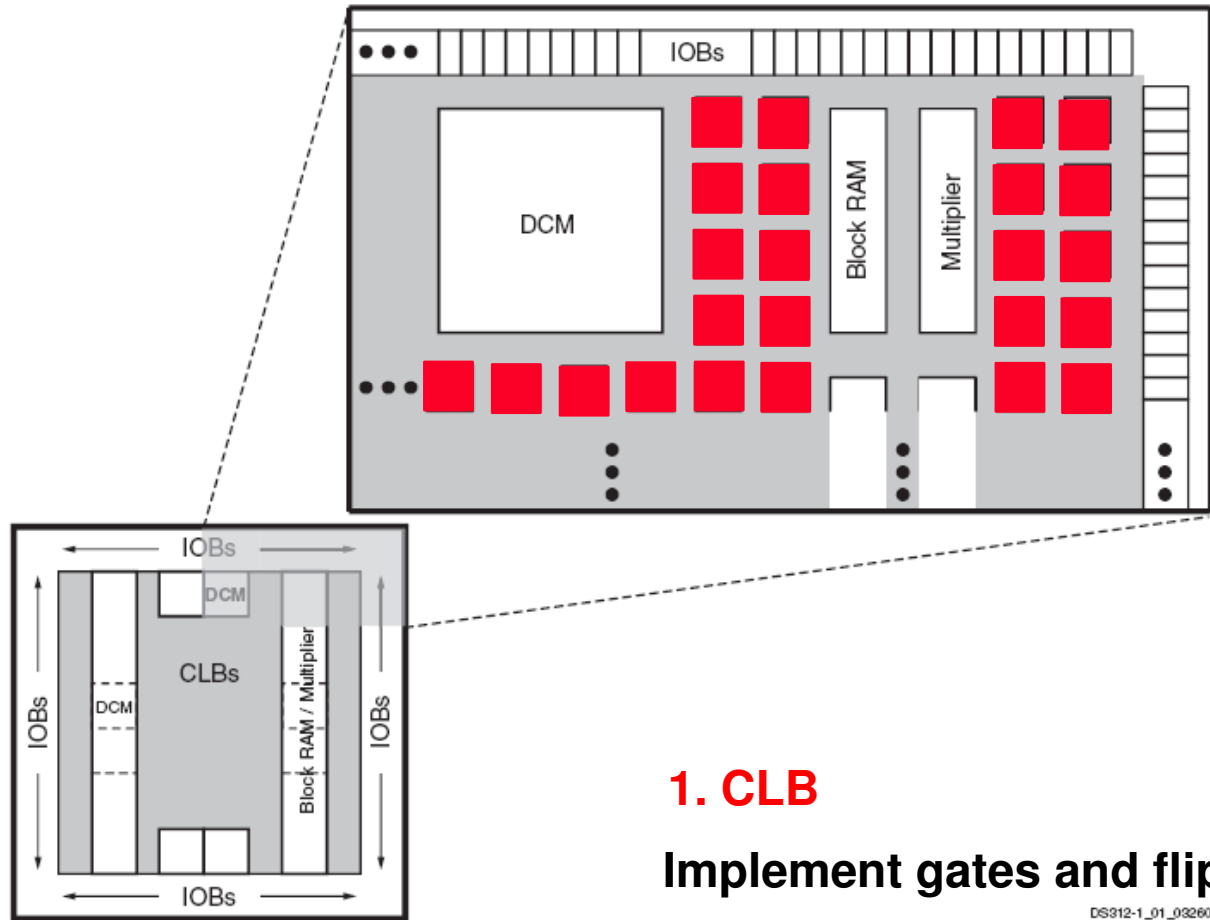
# Spartan 3

- 5 programmable elements in a regular network



 
# Spartan 3

- 5 programmable elements in a regular network



 
# Spartan 3

- 5 programmable elements in a regular network


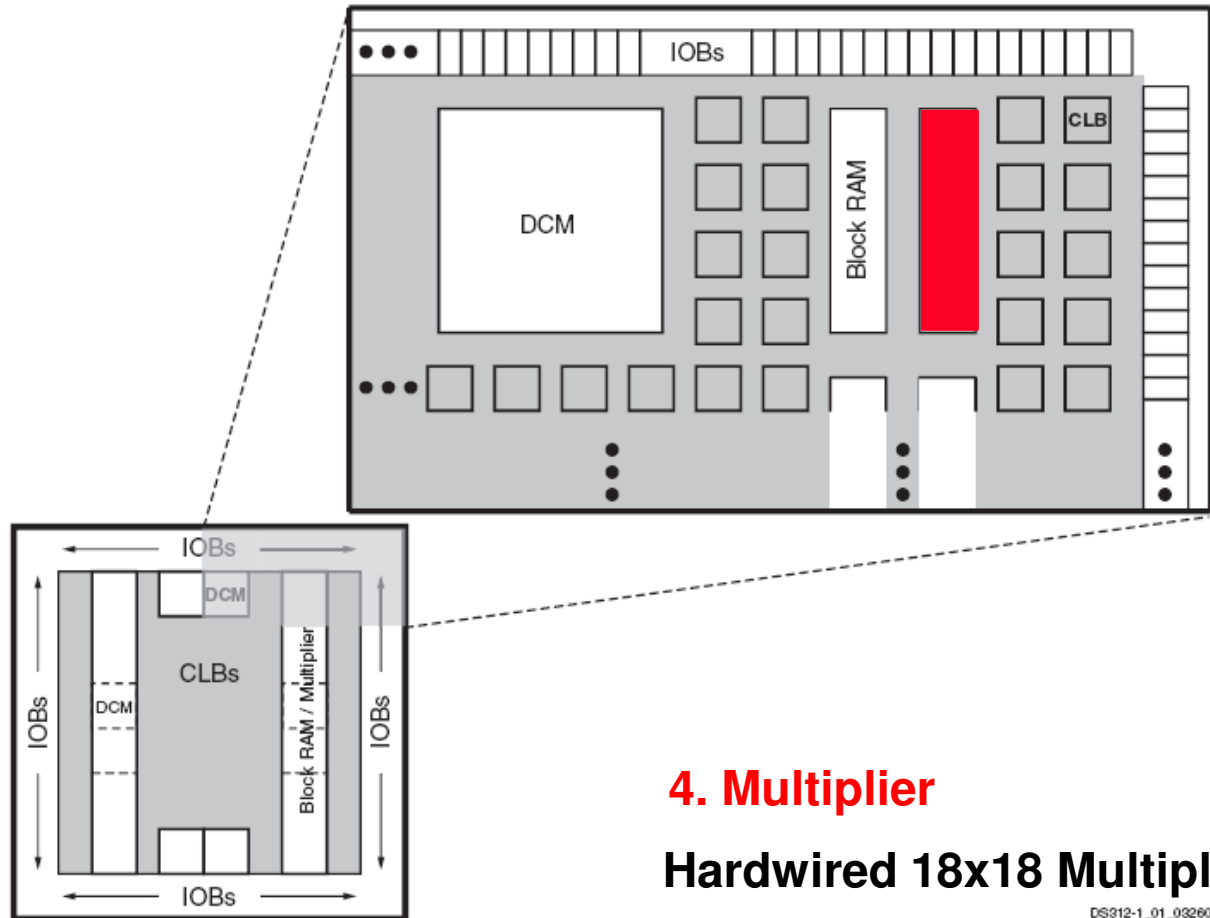
# Spartan 3

- 5 programmable elements in a regular network




## 4. Multiplier

### Hardwired 18x18 Multiplier Cell

DS912-1\_01\_032608
 
# Spartan 3

- 5 programmable elements in a regular network




## 5. DCM

Digital Clock Manager for Clock generation and distribution


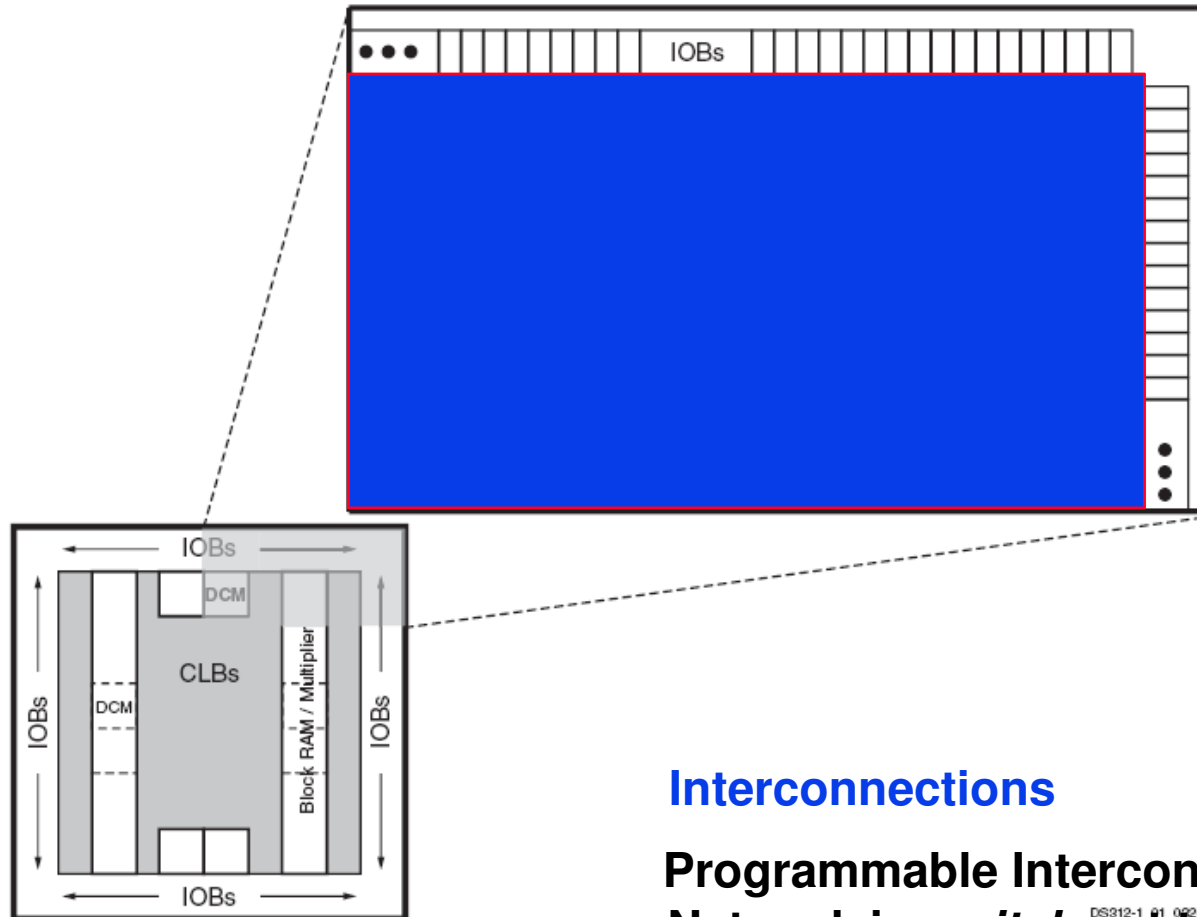
# Spartan 3

- 5 programmable elements in a regular network



## Interconnections

**Programmable Interconnection Network is a *vital* part to FPGA**


# Spartan 3

---

- In this lecture we discuss two elements
  - CLB
  - Interconnection Network
  
- Other elements will be discussed later
  - BRAM
  - Multiplier
  - IOB
  - DCM

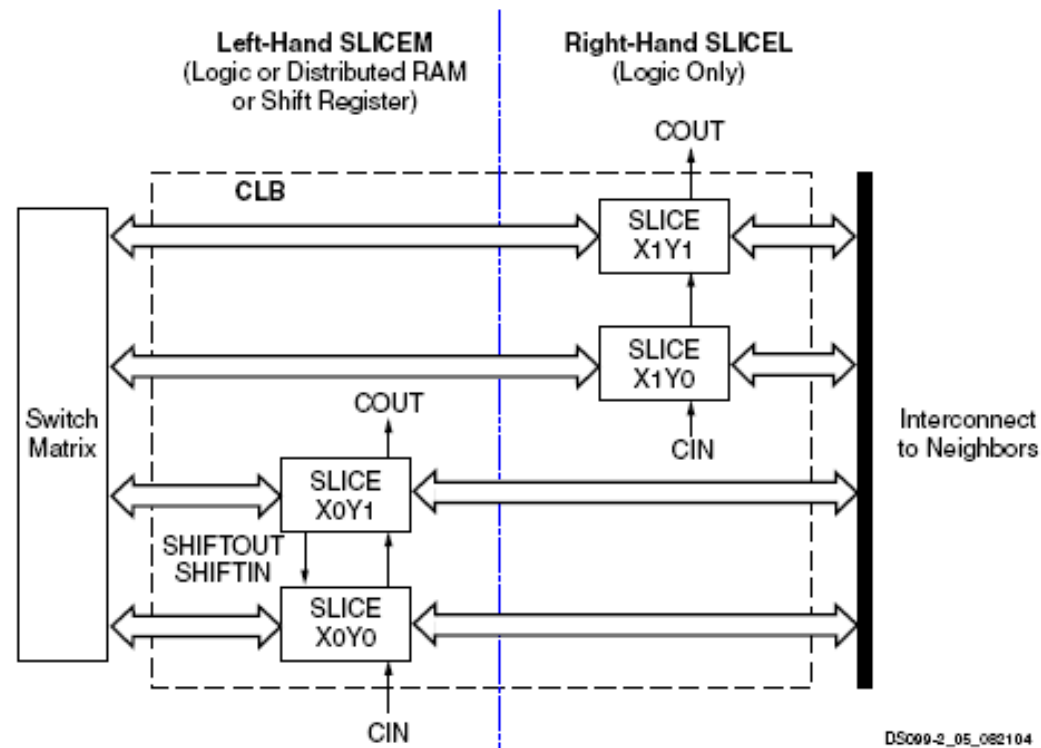
# CLB = Configurable Logic Block

- ❑ 4 'Slices' per CLB
- ❑ Each slice can work as logic (gates + flip-flop), distributed RAM, or shift register
- ❑ Switch Matrix connects to FPGA network



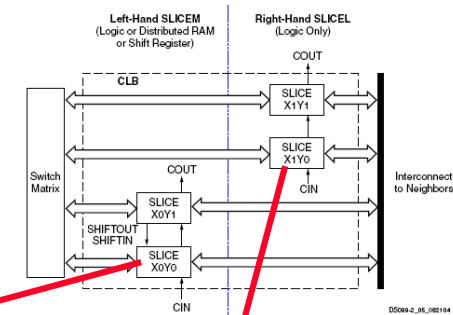
# Left-hand and Right-hand slice

- ❑ SRL16 = 16-bit shift register (~ 16x1 bit memory)
- ❑ RAM16 = 16-bit RAM (~ 16x1 bit memory)
- ❑ LUT4 = 4-bit lookup table (~ 4x4bit memory)
- ❑ SLICEM = Slice that can work as memory or logic
- ❑ SLICEL = Slice that only works as logic




**left-hand slice**

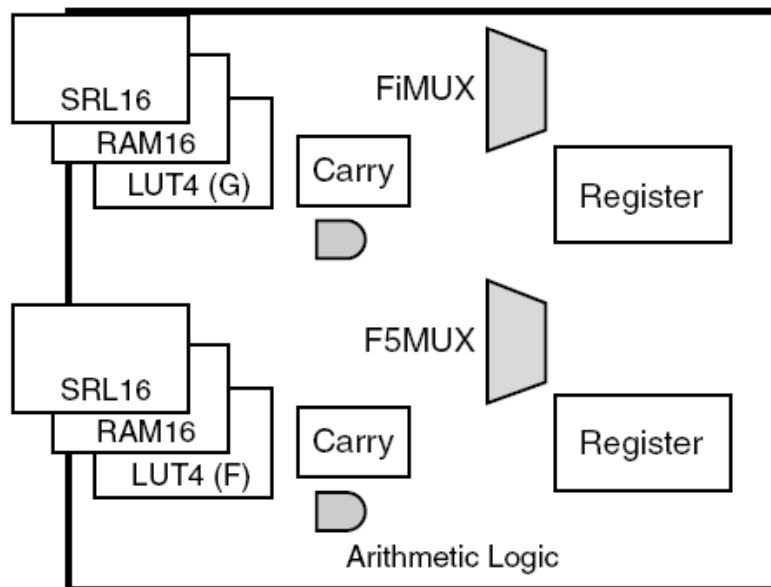

**SLICEM**

**right-hand slice**

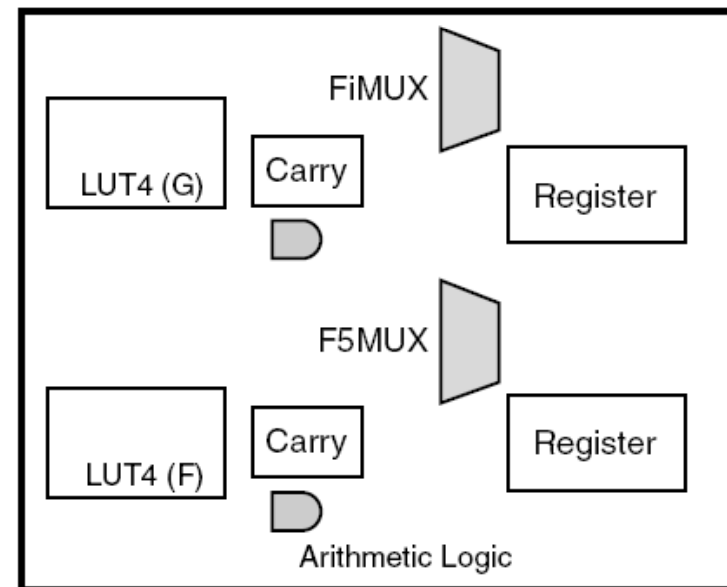


**SLICEL**

DS312-2\_13\_020905
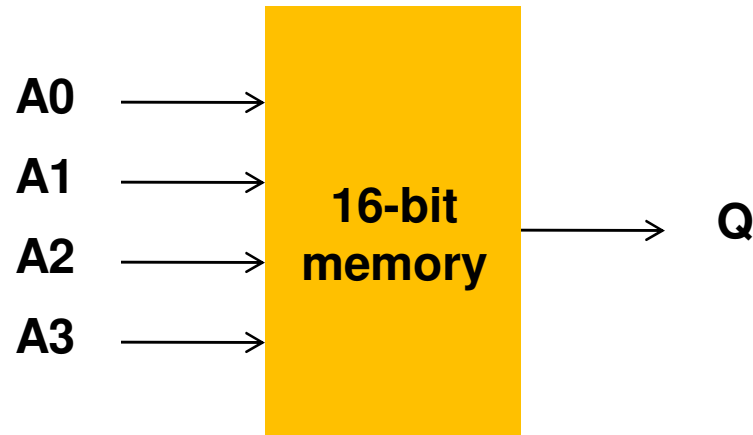
# LUT4: basic building block

---


- ❑ RAM memory 4-bit input, 1-bit output
- ❑ Can implement any logic function of up to 4 inputs



 
# LUT4: basic building block

---



- ❑ Example: Implement 3-input AND
- ❑ Assume A0 - A2 are used




A0	A1	A2	A3	Q
0	0	0	x	0
0	0	1	x	0
0	1	0	x	0
0	1	1	x	0
1	0	0	x	0
1	0	1	x	0
1	1	0	x	0
1	1	1	x	1

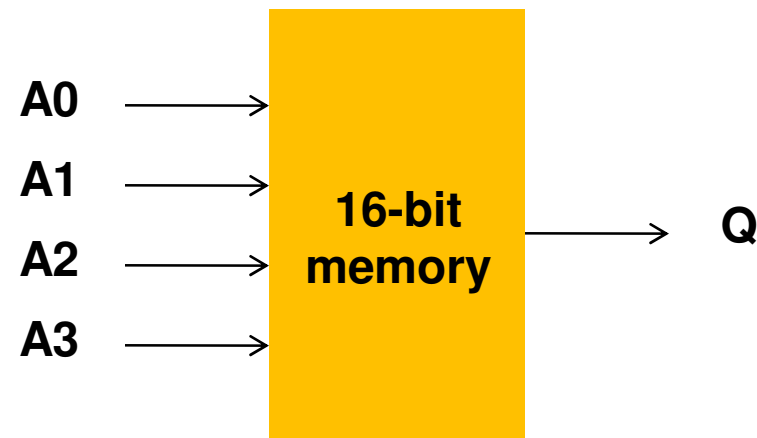

# Slice Muxes extend 4-input LUT

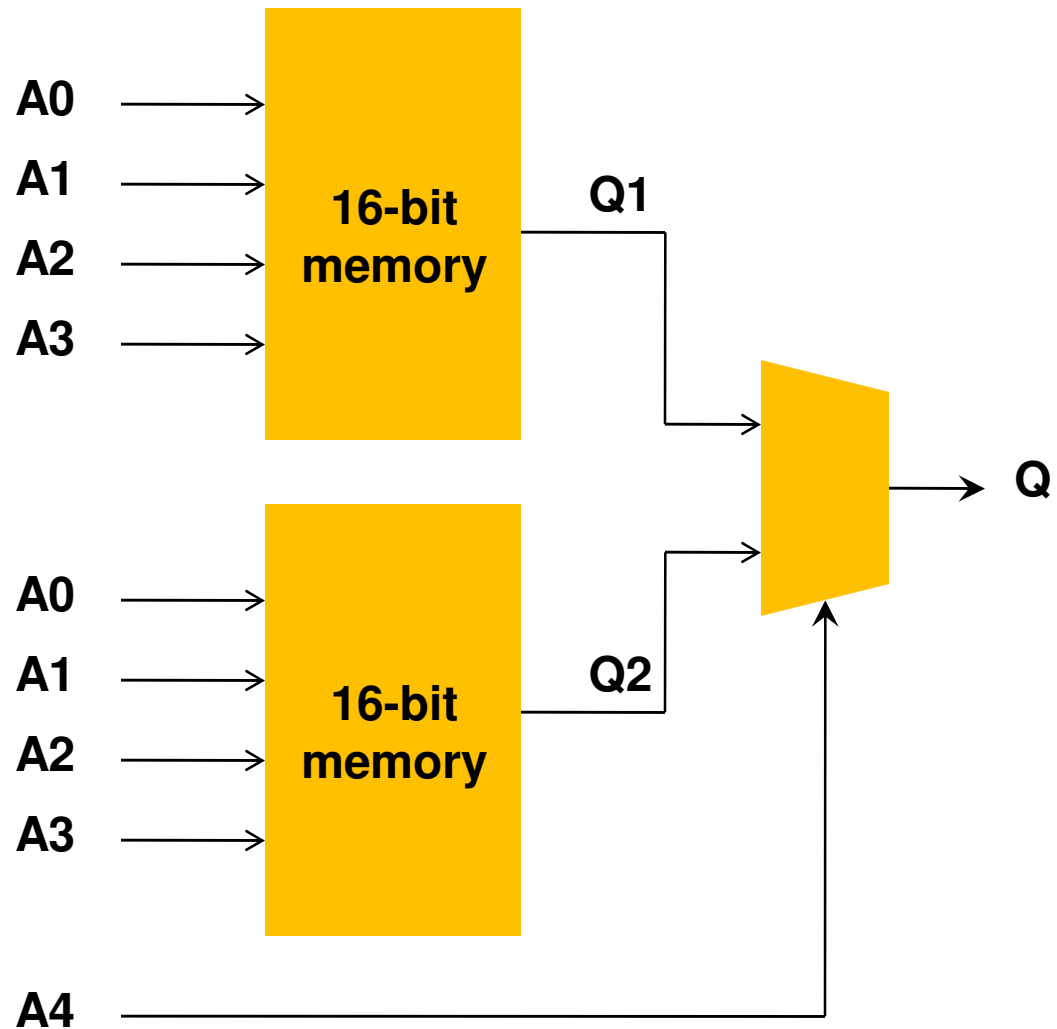
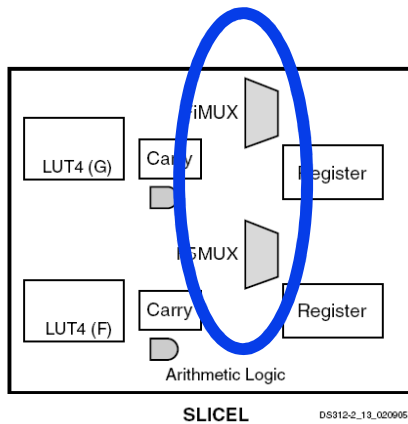

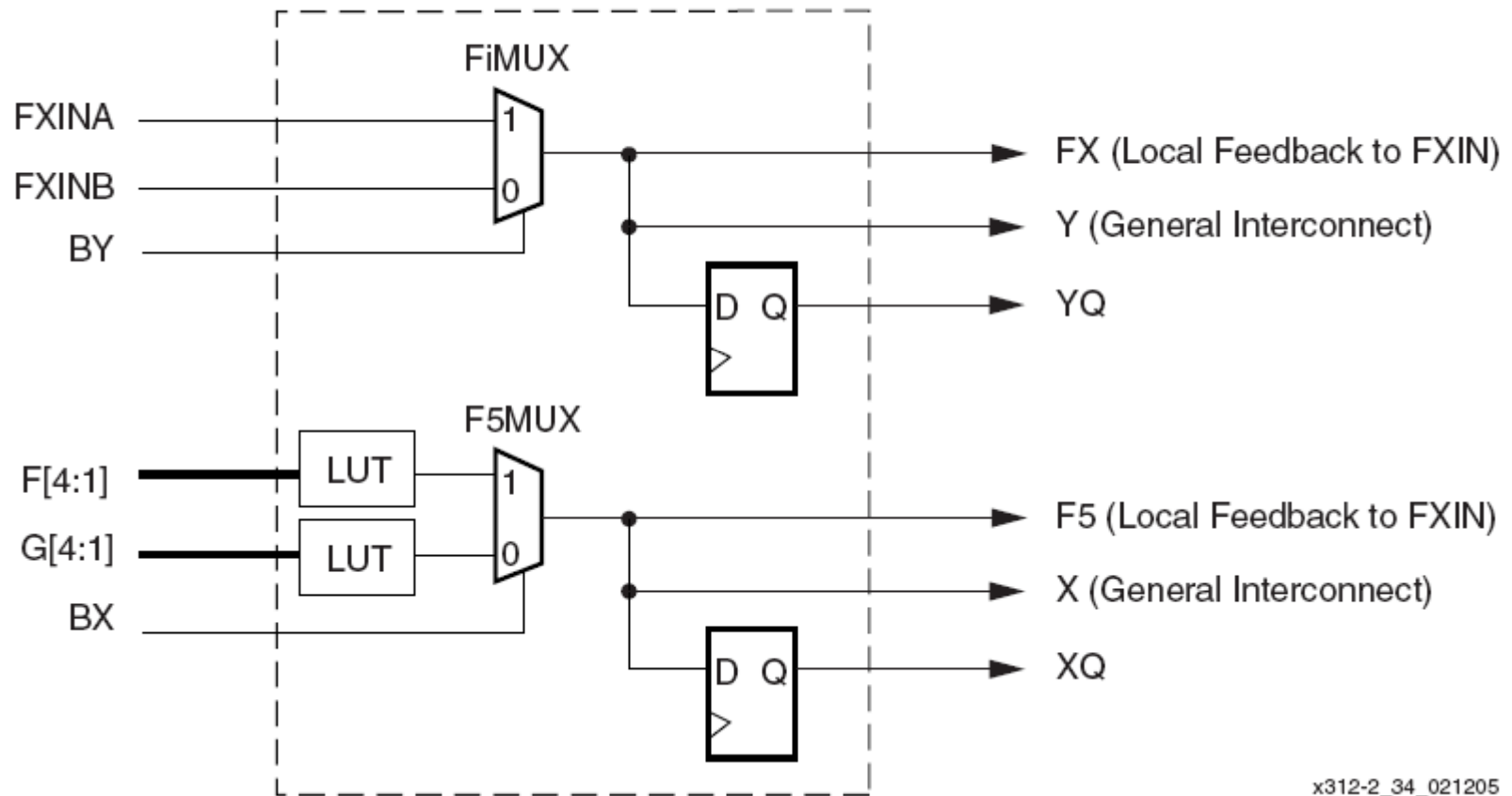
# Upper & Lower LUT can be combined further ..






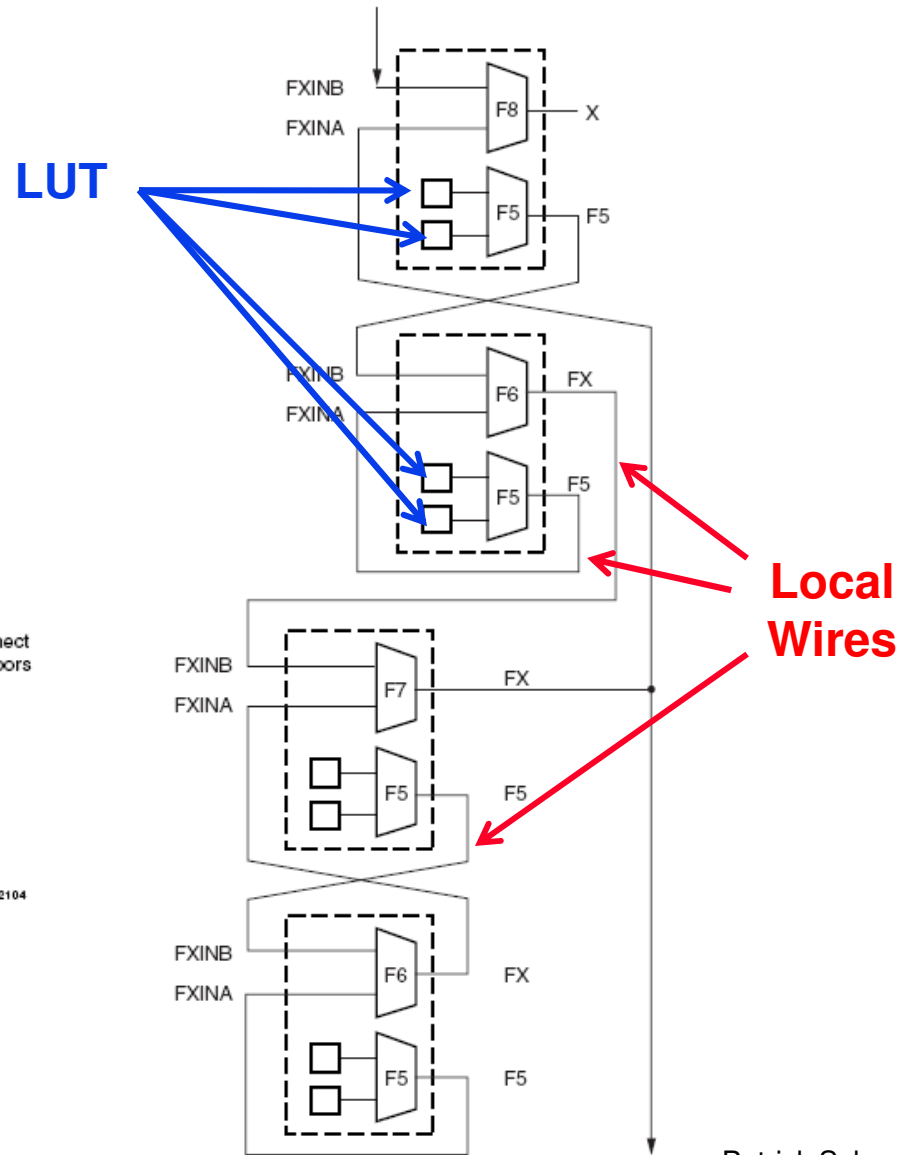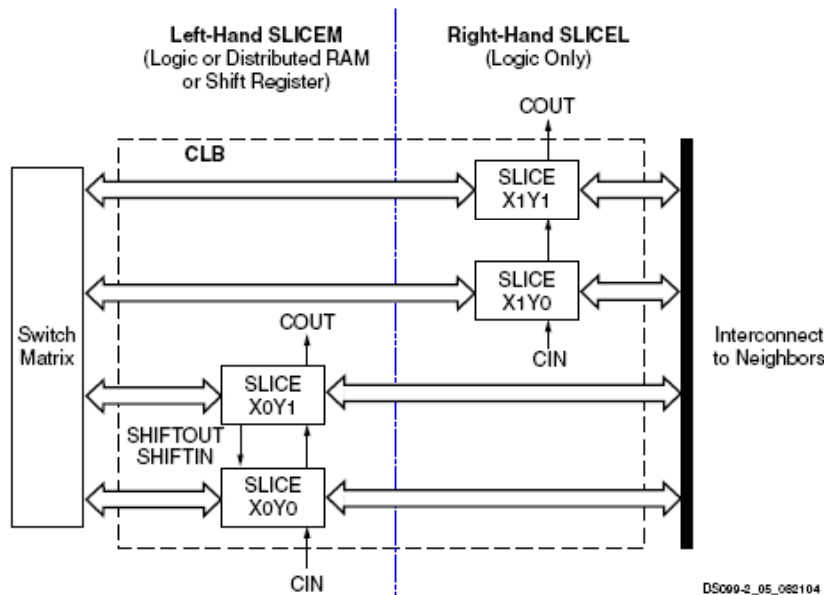
# One CLB can implement up to 7-input LUT




# Top half of a (left-hand) slice

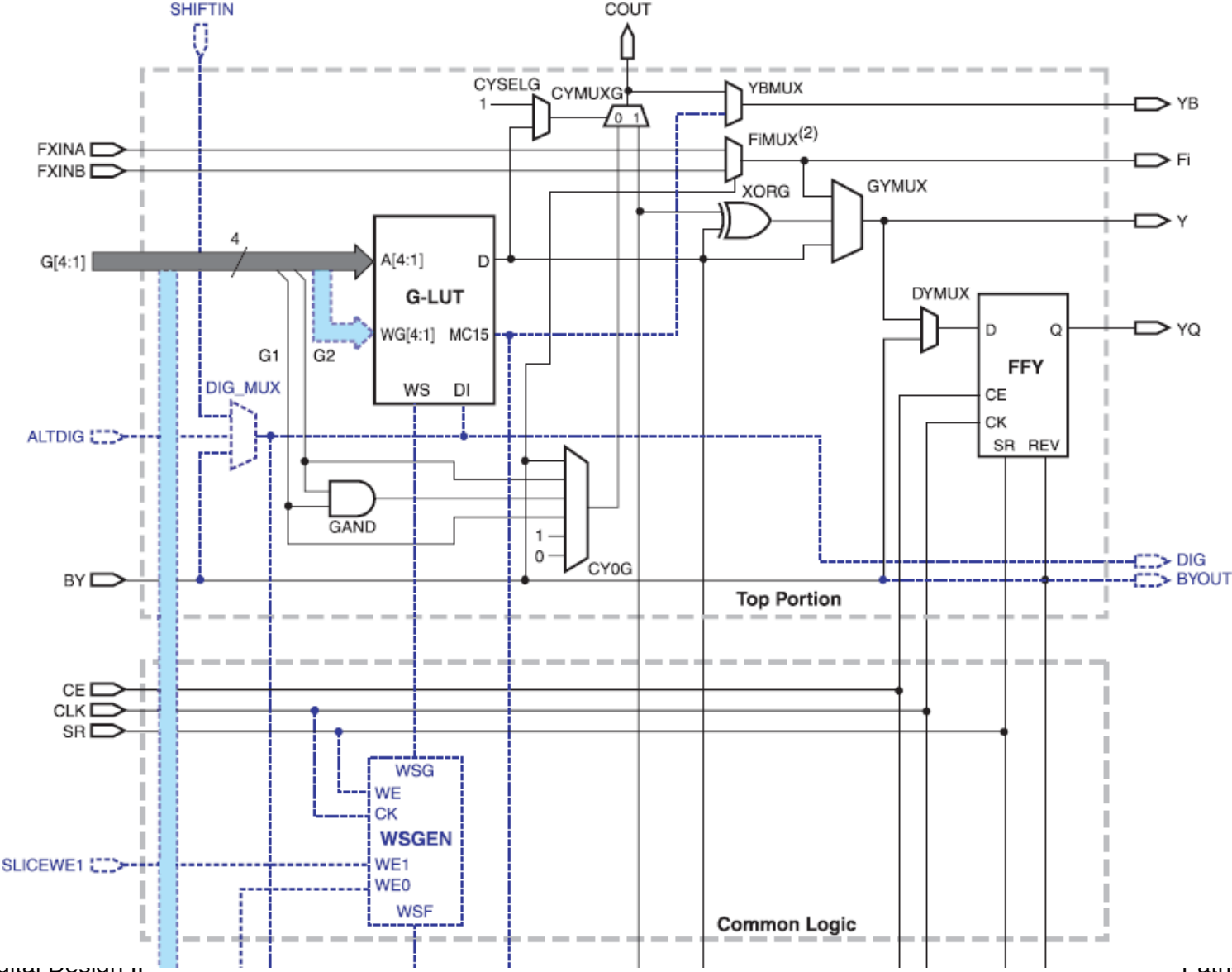


# Top half of a (left-hand) slice

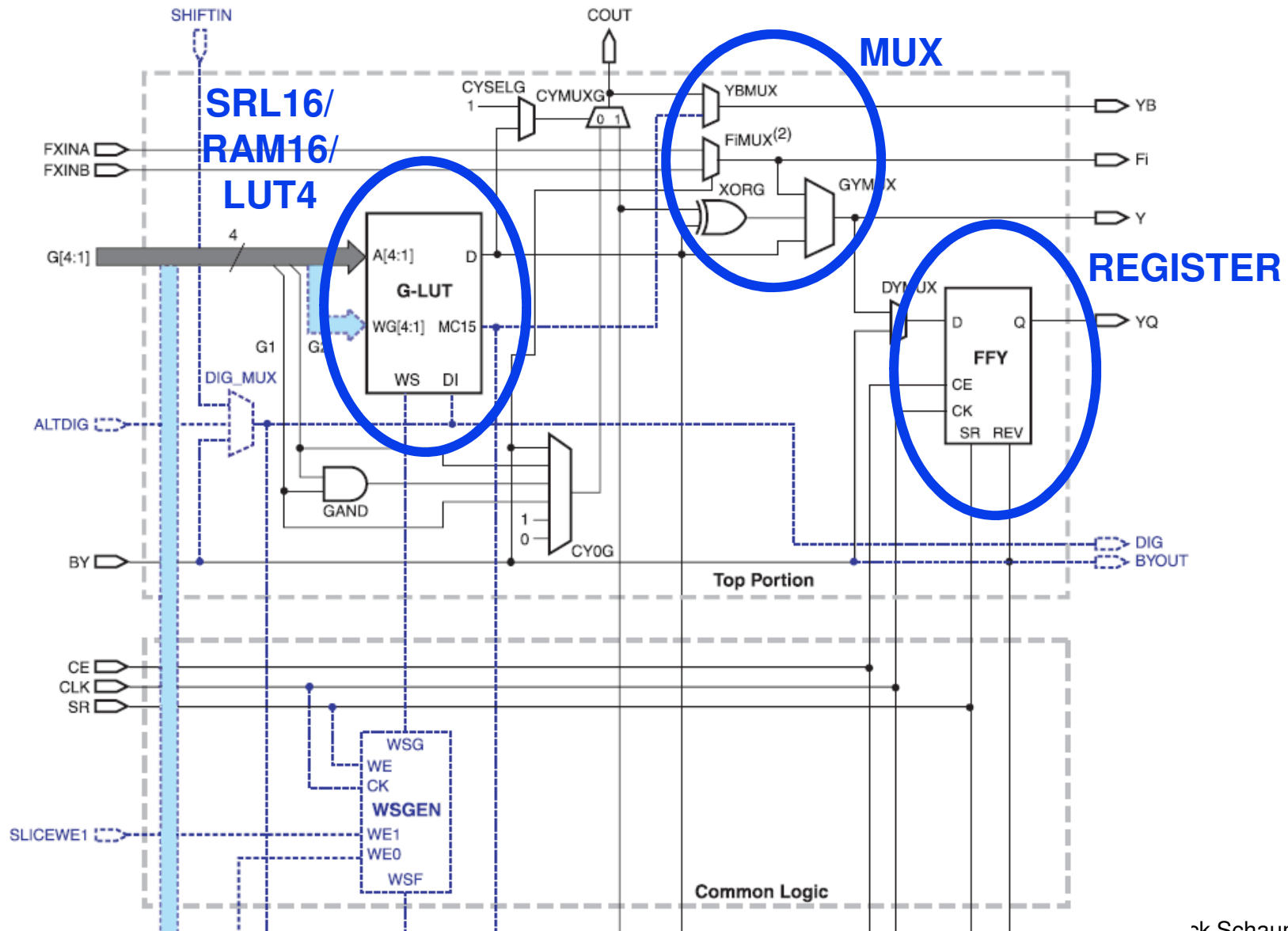


# Works only as logic ..

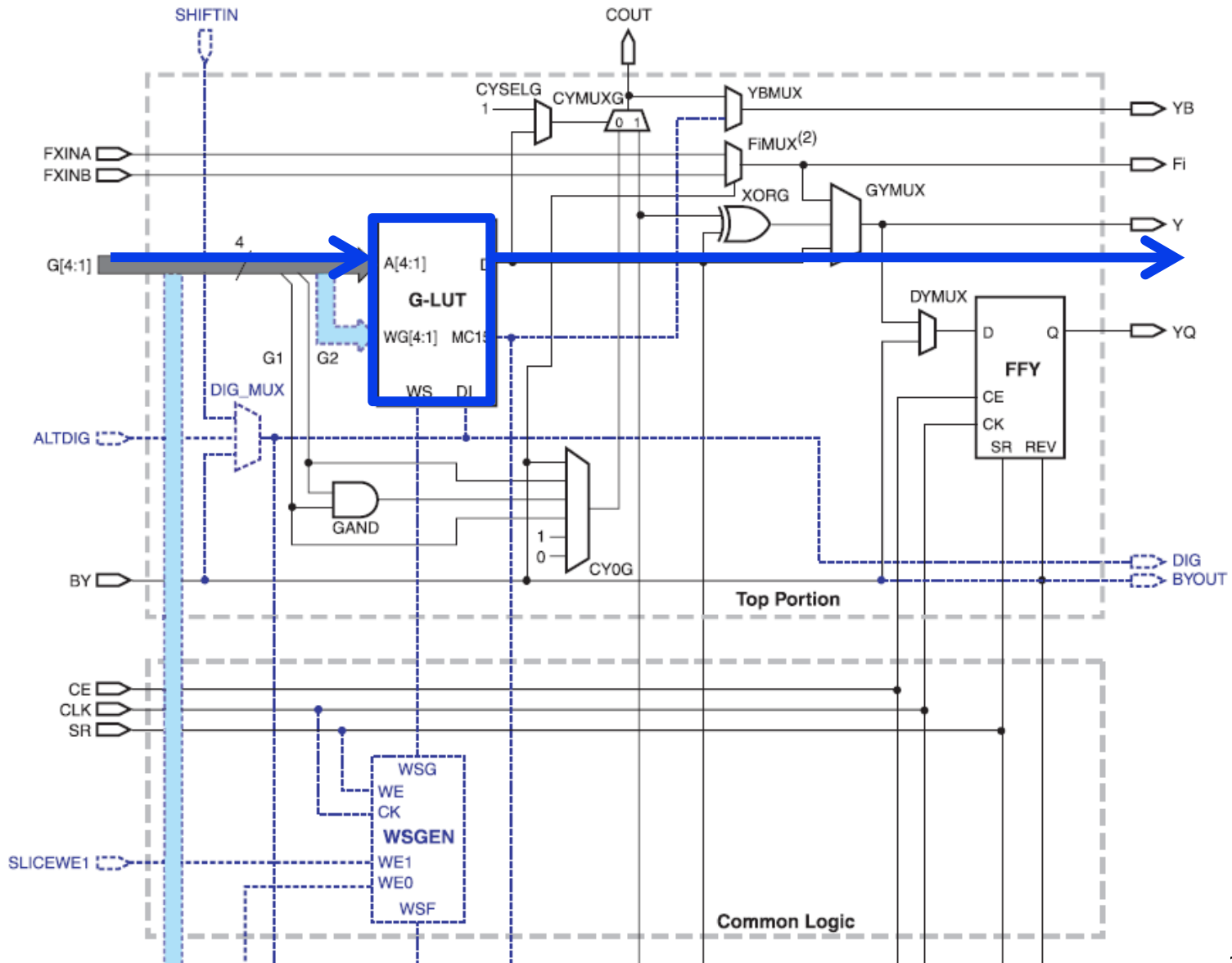

# .. or as logic + register

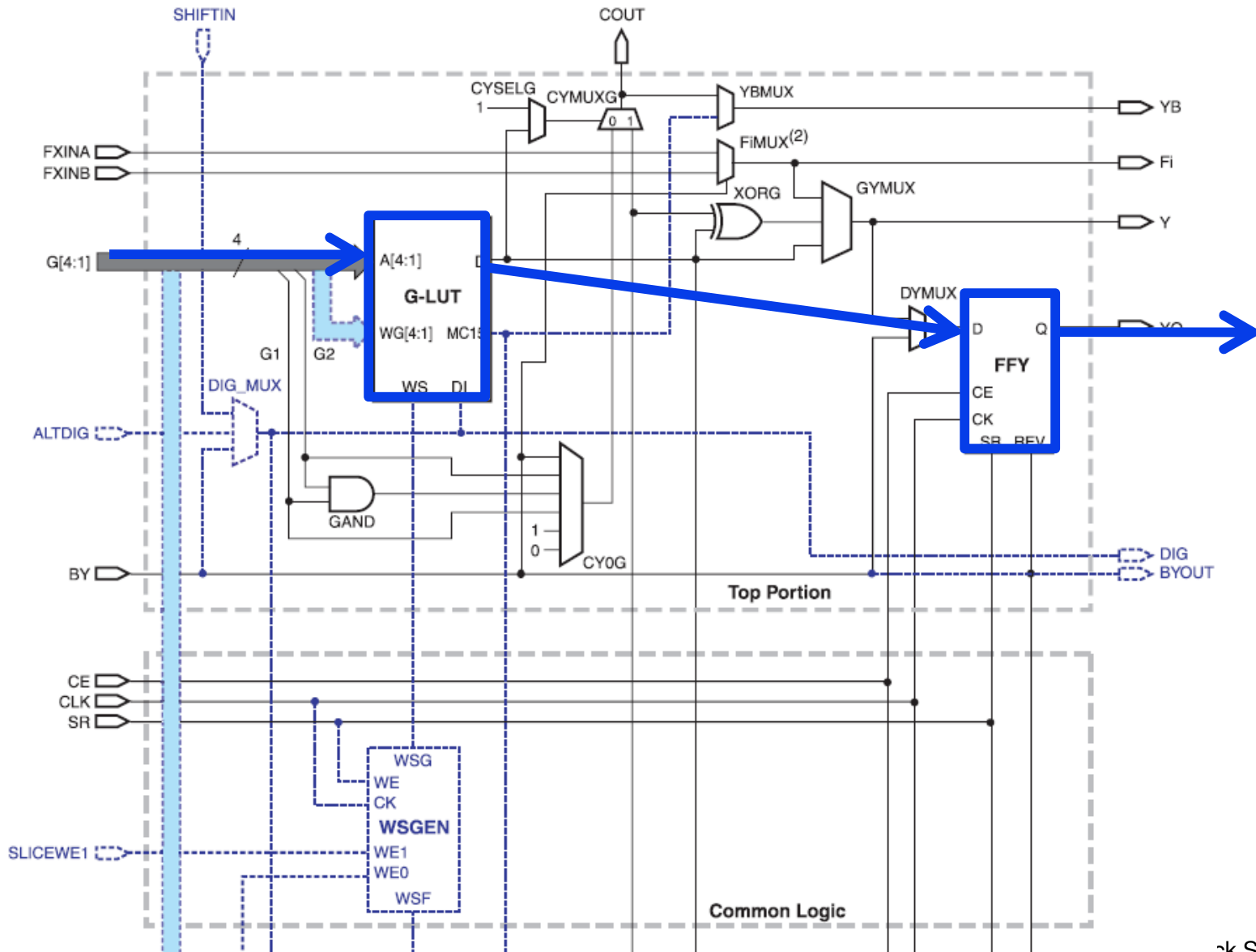


# .. or only as register

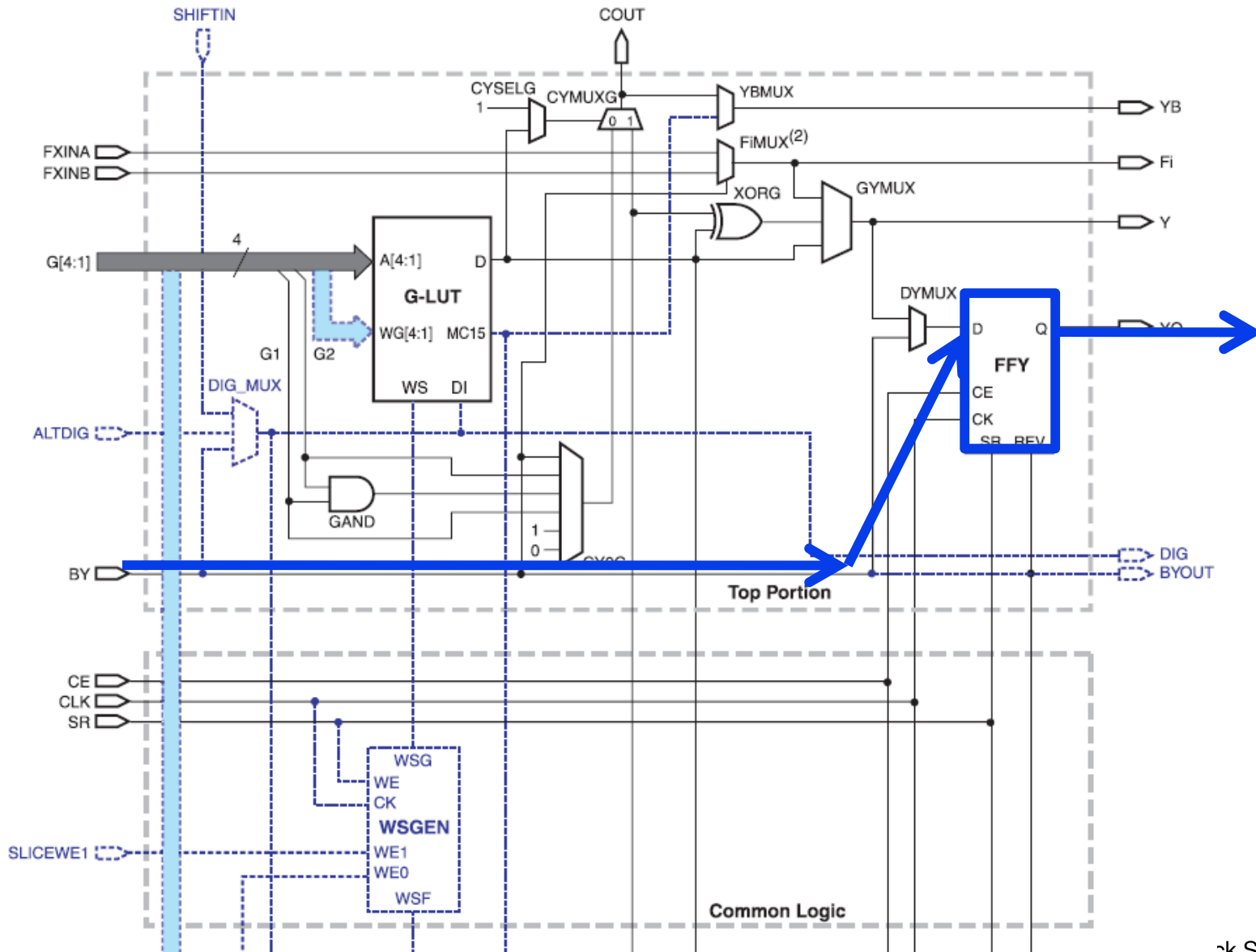
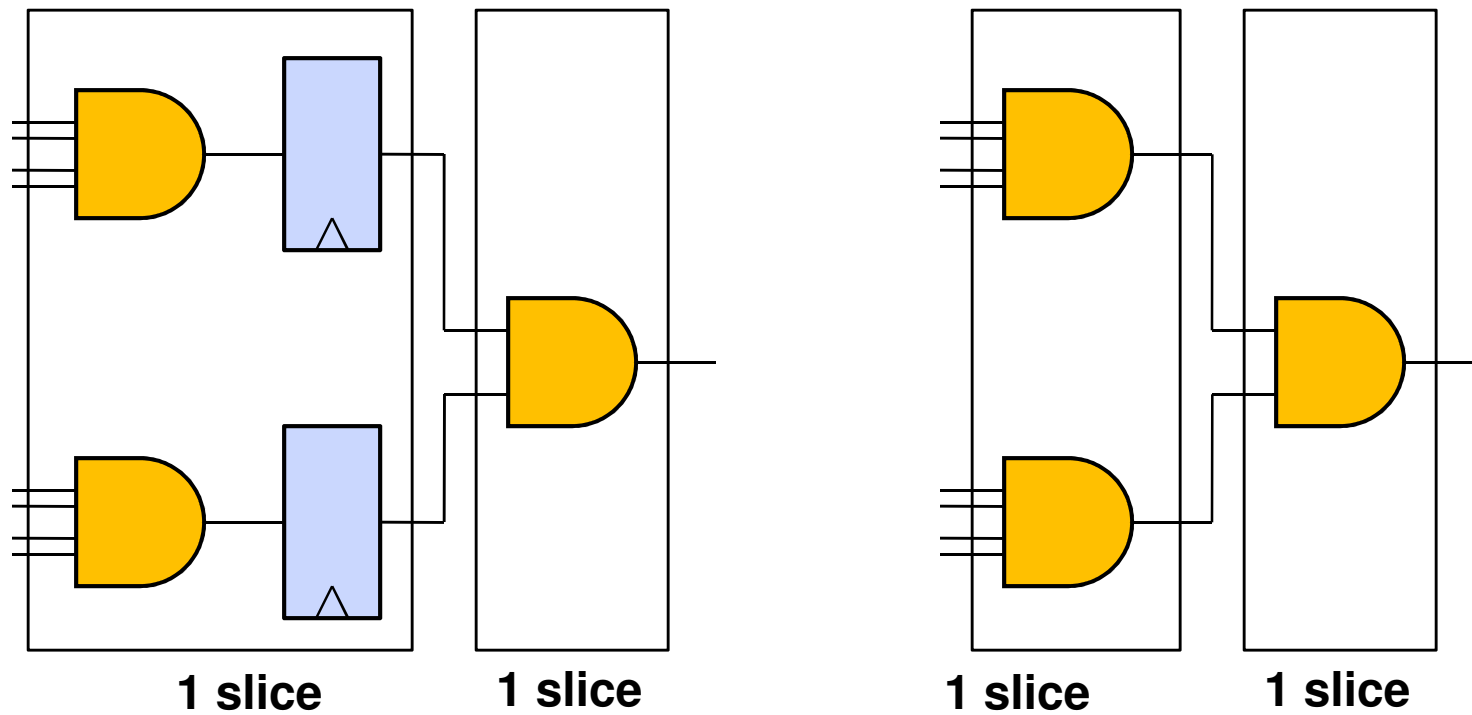
## Each LUT comes with a FF, so:

---



- ❑ In an FPGA, the left circuit uses as much slices as the right circuit


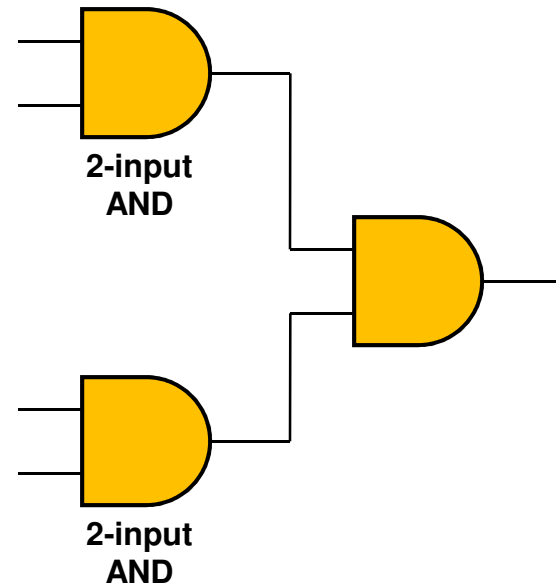 
# What about this case ?

---

- ❑ Do you need the same amount of slices for each circuit?






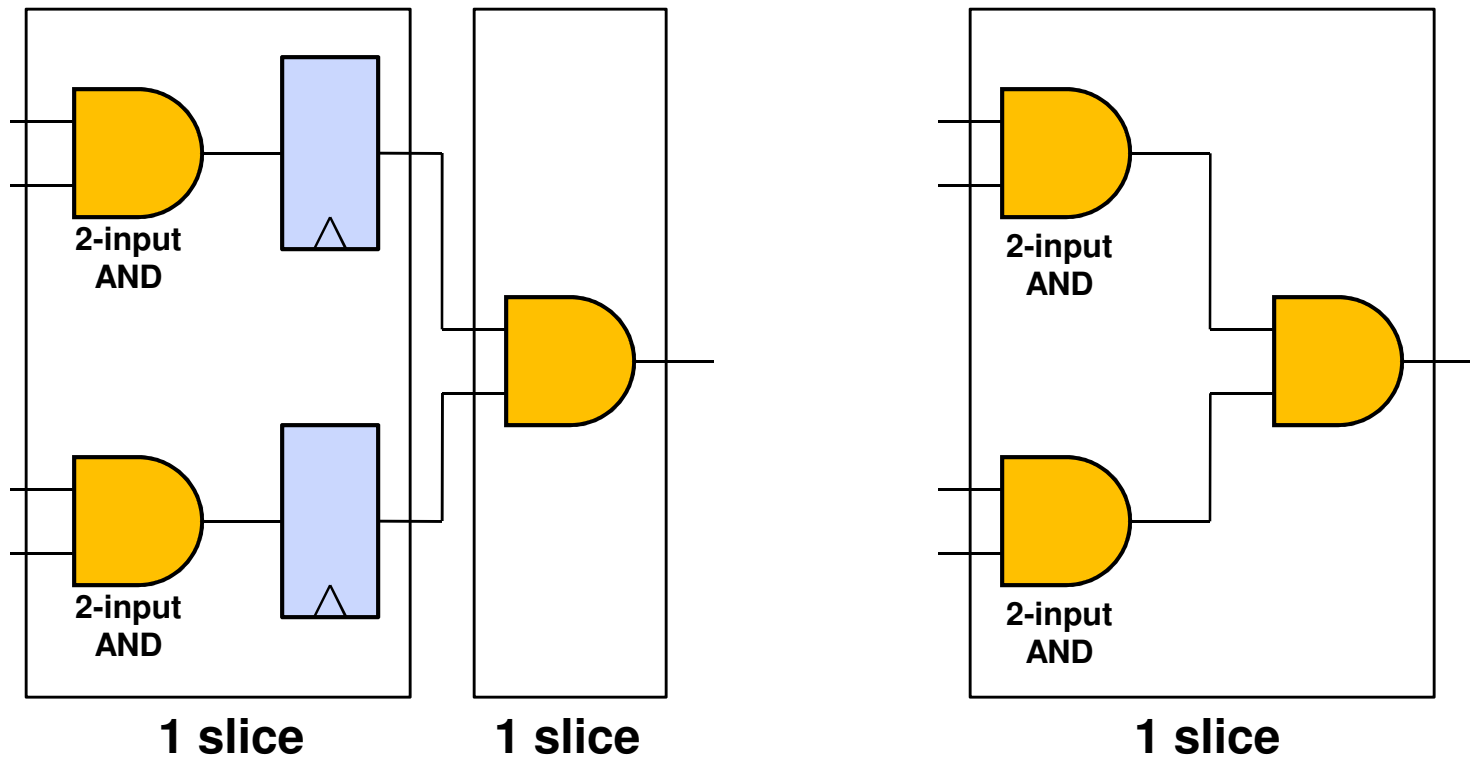
# What about this case ?

---



- ❑ Do you need the same amount of slices for each circuit?
- ❑ No! You can cluster the right circuit in a single slice



# Fast Carry Path (for arithmetic)

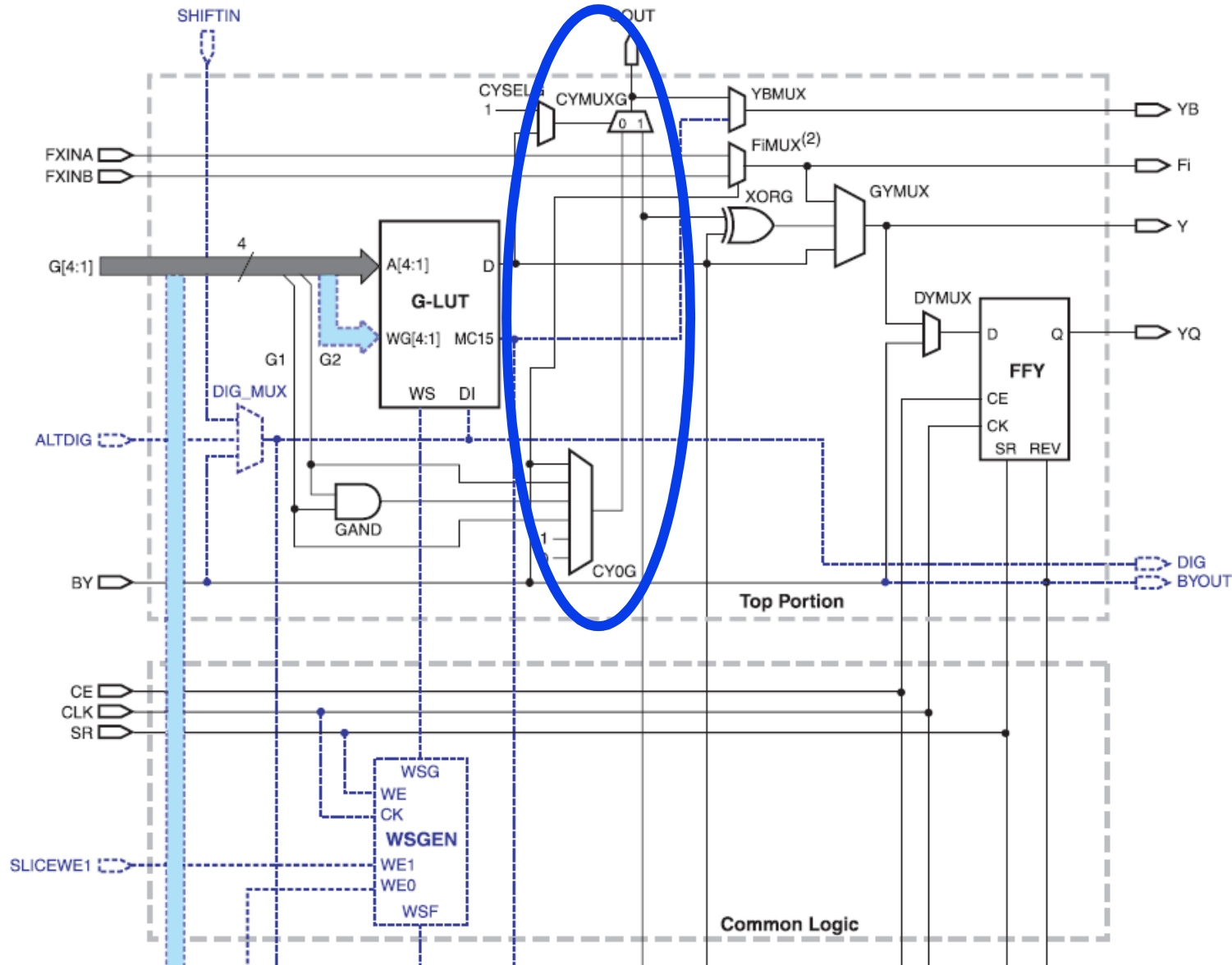

# Typical use of carry path

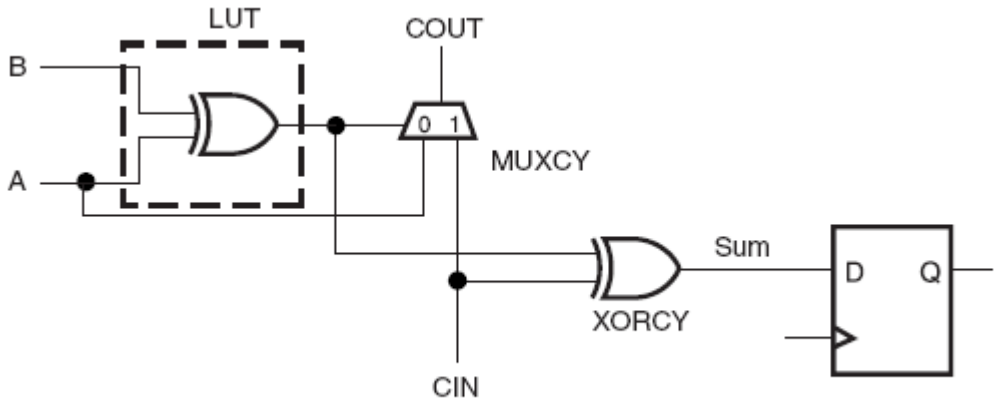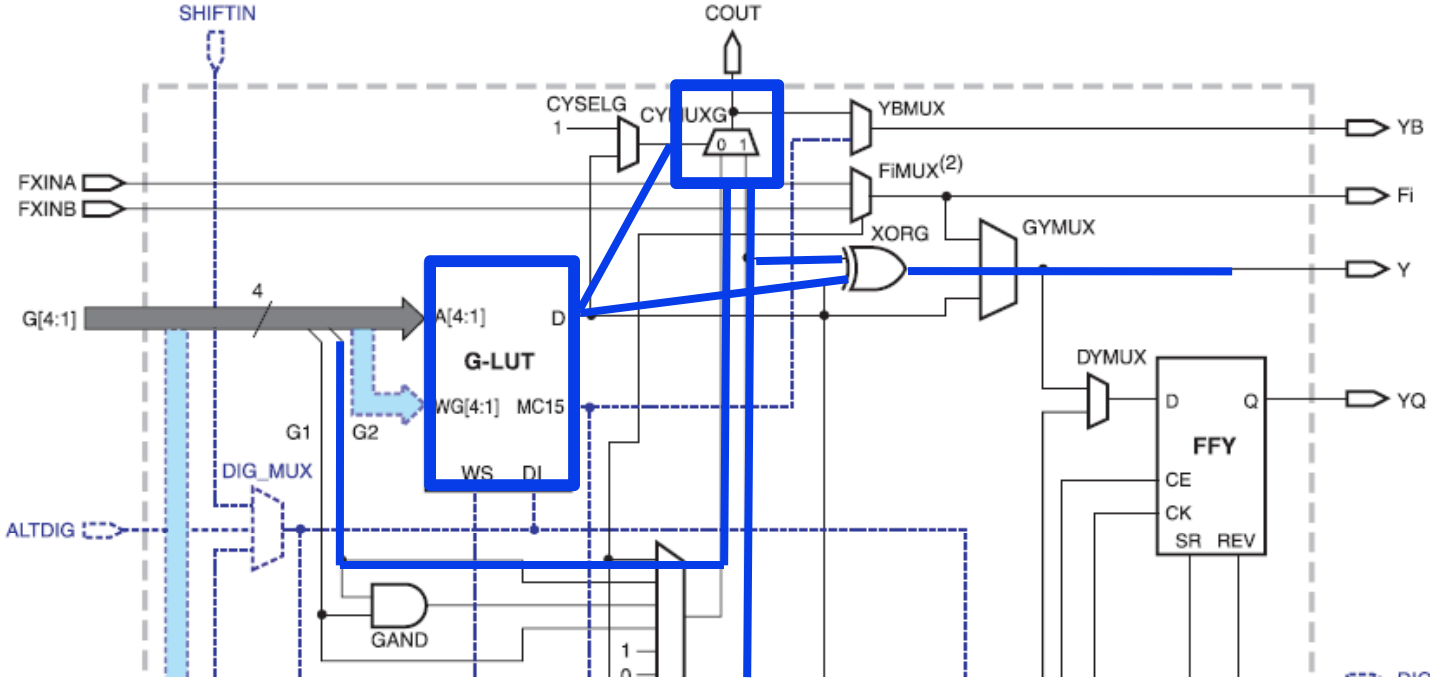

DS312-2\_37\_021305

# Summary CLB

---

- ❑ 1 configurable logic block contains 4 slices
- ❑ Each slice contains a combination of
  - 2 LUT
  - 2 flip flop
  - MUXes
  - Carry-logic
- ❑ A LUT can operate as
  - Random logic function of 4 inputs
  - 16-bit RAM
  - 16-bit shift register
- ❑ Tools report area results in slices
  - Slices can be many different things, depending on configuration


# Interconnect Network

---

- ❑ Interconnections are THE critical component in an FPGA
  - Largest physical area on a die
  - Largest power consumption
  - In most cases, wire delay becomes performance bottleneck
  
- ❑ Ironically, interconnections are hardly mentioned as a feature in FPGA product literature
  - Engineers like to hear about the number of CLBs in an FPGA, not about the number of wires between CLBs ...
  
- ❑ FPGA interconnect network is a hierarchical architecture
  - Many fast, short wires with small drive capacity
  - Few longer wires with high drive capacity
  - Like a slice architecture, design of interconnect network is a 'secret sauce' of the FPGA..

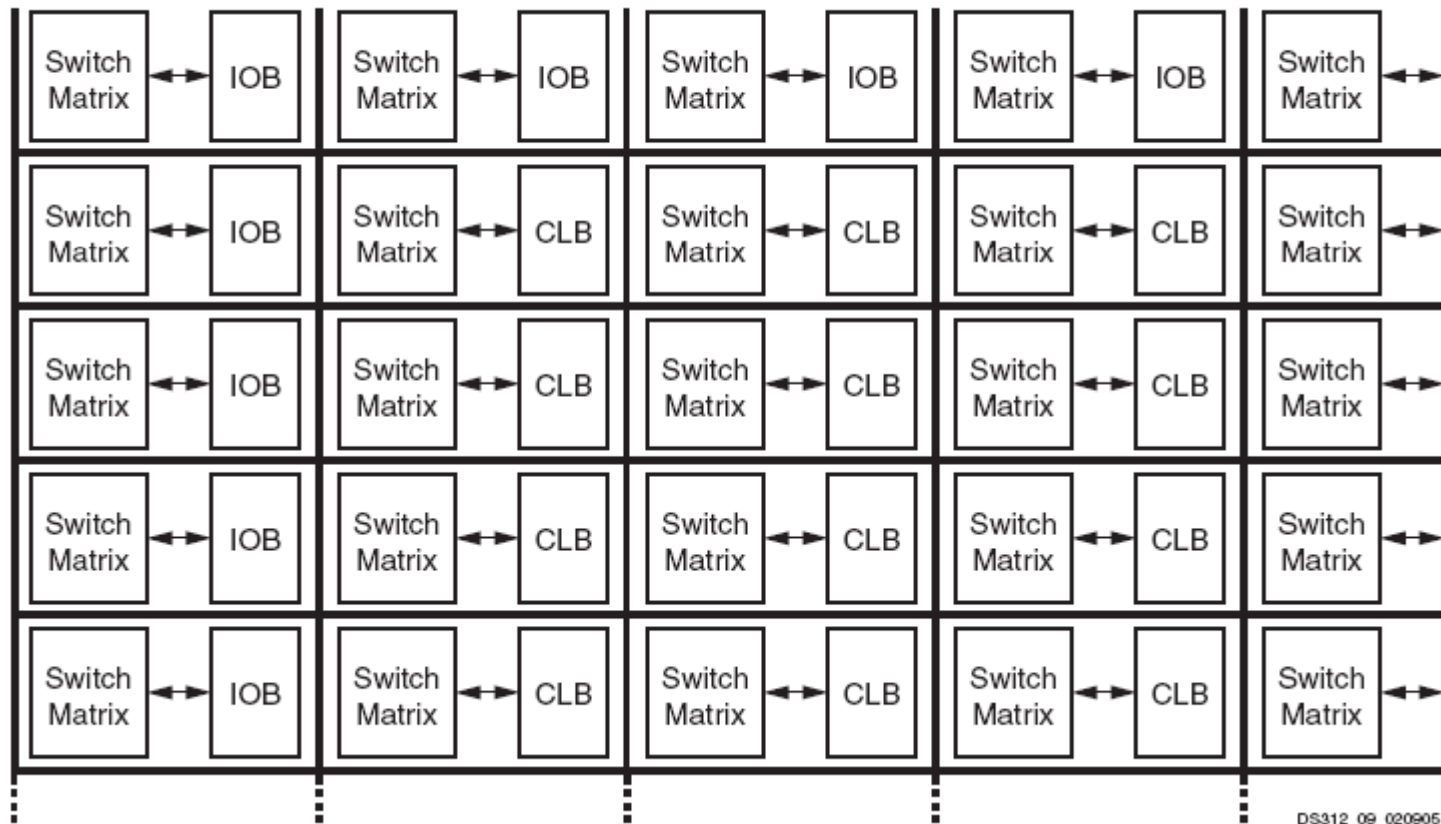
# Interconnection Network in Spartan 3

- ❑ CLBs connect to 'switch matrix' which connects to the on-chip network
- ❑ Each switch matrix interconnects many different wires



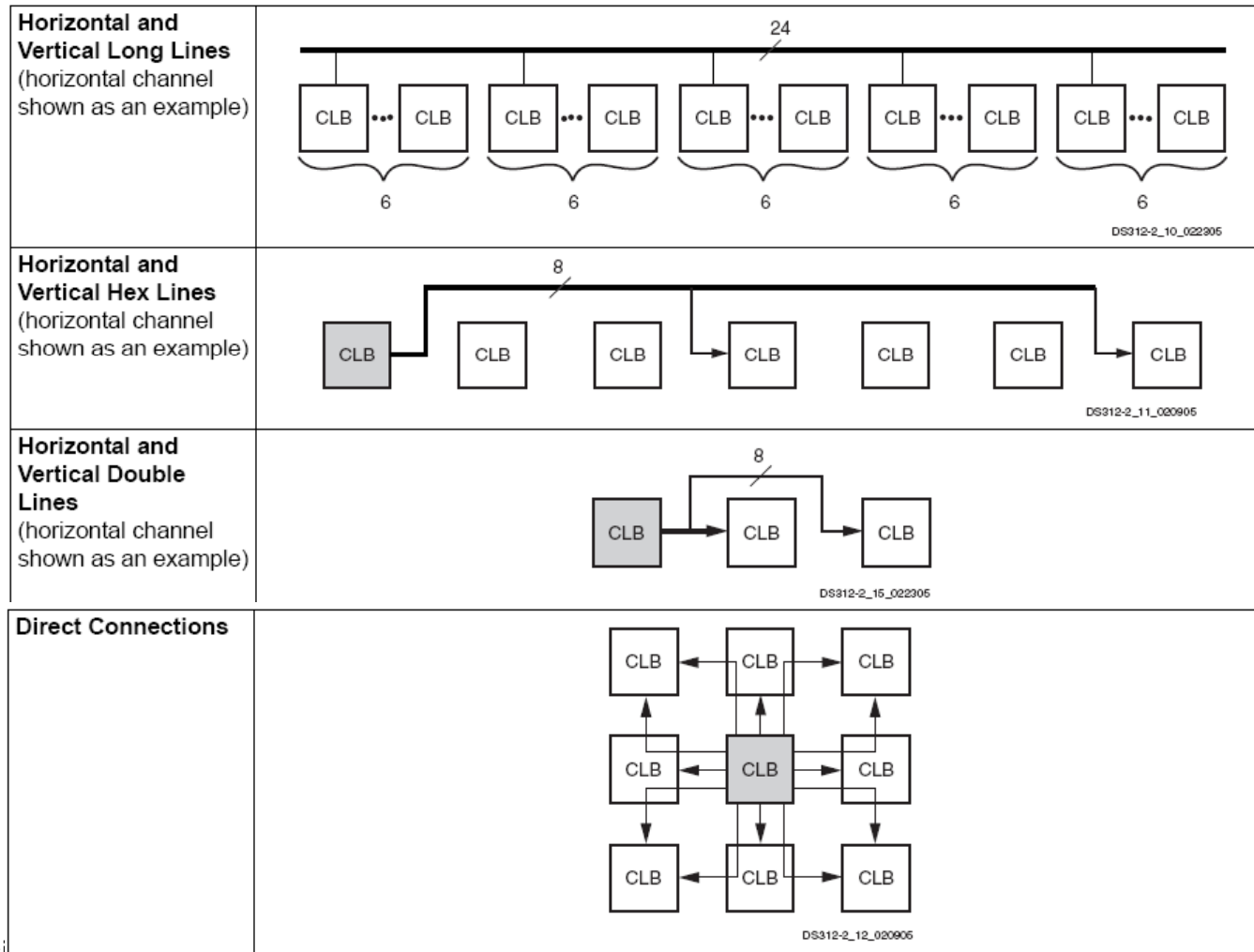
# Interconnection Network

- 4 wire types connected to switch matrix


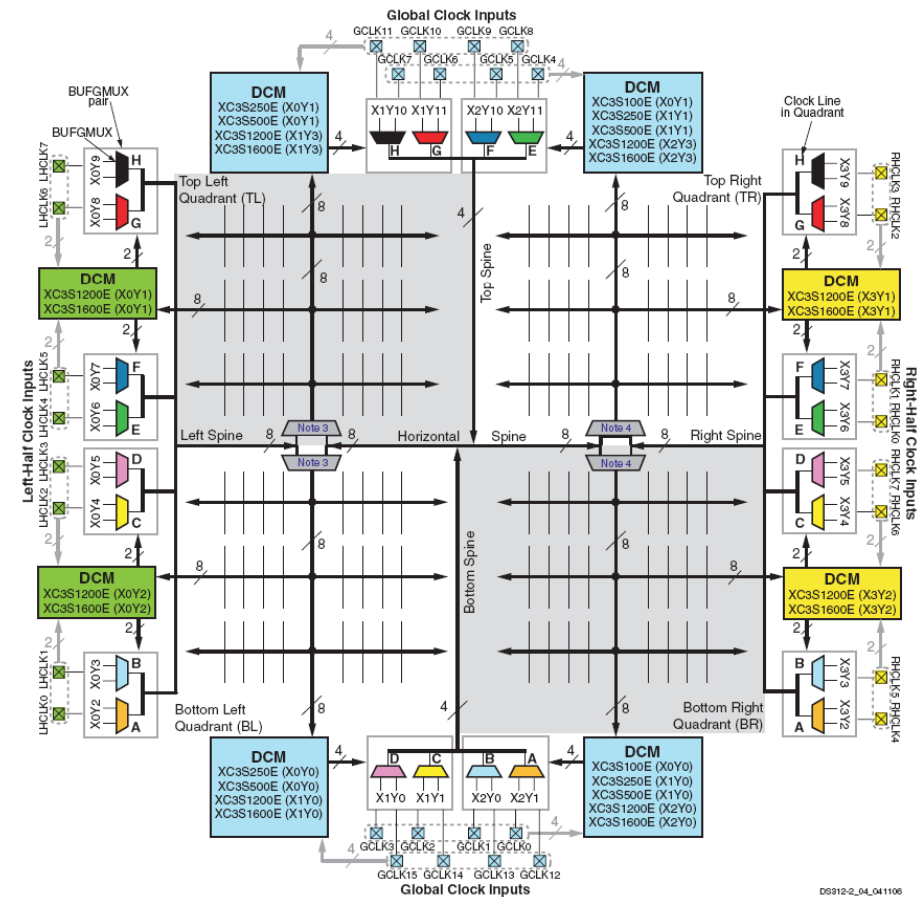
# Interconnection Network

- ❑ Clock signals are distributed with a separate, dedicated network
  - Another reason to avoid gated clocks ..
  
- ❑ A recursive 'fish-bone' network ensures that clock arrives everywhere at the same time
  
- ❑ Clock signals generated externally or else inside of 'DCM'
  - DCM can create multiply/divide external clock to a different on-chip clock





# Now, we understand databook figures

Table 1: Summary of Spartan-3E FPGA Attributes

Device	System Gates	Equivalent Logic Cells	CLB Array (One CLB = Four Slices)				Distributed RAM bits <sup>(1)</sup>	Block RAM bits <sup>(1)</sup>	Dedicated Multipliers	DCMs	Maximum User I/O	Maximum Differential I/O Pairs
			Rows	Columns	Total CLBs	Total Slices						
XC3S100E	100K	2,160	22	16	240	960	15K	72K	4	2	108	40
XC3S250E	250K	5,508	34	26	612	2,448	38K	216K	12	4	172	68
XC3S500E	500K	10,476	46	34	1,164	4,656	73K	360K	20	4	232	92
XC3S1200E	1200K	19,512	60	46	2,168	8,672	136K	504K	28	8	304	124
XC3S1600E	1600K	33,192	76	58	3,688	14,752	231K	648K	36	8	376	156

**Notes:**

1. By convention, one Kb is equivalent to 1,024 bits.



**The Spartan 3E starter kit has a 3ES500 FPGA**

# Summary on 3ES500

Table 1: Summary of Spartan-3E FPGA Attributes

Device	System Gates	Equivalent Logic Cells	CLB Array (One CLB = Four Slices)				Distributed RAM bits <sup>(1)</sup>	Block RAM bits <sup>(1)</sup>	Dedicated Multipliers	DCMs	Maximum User I/O	Maximum Differential I/O Pairs
			Rows	Columns	Total CLBs	Total Slices						
XC3S100E	100K	2,160	22	16	240	960	15K	72K	4	2	108	40
XC3S250E	250K	5,508	34	26	612	2,448	38K	216K	12	4	172	68
XC3S500E	500K	10,476	46	34	1,164	4,656	73K	360K	20	4	232	92
XC3S1000E	1000K	20,952	68	46	2,328	9,312	146K	720K	36	8	464	184
XC3S1600E	1600K	33,192	76	58	3,688	14,752	231K	648K	36	8	376	156

**Notes:**

1. By convention, one Kb is equivalent to 1,024 bits.

**XC3S500E = 500K 'system gates'**

**10,476 Logic Cells**

**A 'Logic Cell' is the unit of configuration in an FPGA.  
It consists of a lookup table and a flip-flop.  
In the case of Xilinx, 1 LC = 2.25 LUT ..**

# Summary on 3ES500

Table 1: Summary of Spartan-3E FPGA Attributes


Device	System Gates	Equivalent Logic Cells	CLB Array (One CLB = Four Slices)				Distributed RAM bits <sup>(1)</sup>	Block RAM bits <sup>(1)</sup>	Dedicated Multipliers	DCMs	Maximum User I/O	Maximum Differential I/O Pairs
			Rows	Columns	Total CLBs	Total Slices						
XC3S100E	100K	2,160	22	16	240	960	15K	72K	4	2	108	40
XC3S250E	250K	5,508	34	26	612	2,448	38K	216K	12	4	172	68
XC3S500E	500K	10,476	46	34	1,164	4,656	73K	360K	20	4	232	92
XC3S1000E	1000K	16,518	68	46	3,108	12,432	188K	576K	36	8	364	144
XC3S1600E	1600K	33,192	76	58	3,688	14,752	231K	648K	36	8	376	156

**Notes:**

1. By convention, one Kb is equivalent to 1,024 bits.

**XC3S500E = 500K 'system gates'**

**46 rows, 34 columns**

 

# Summary on 3ES500

Table 1: Summary of Spartan-3E FPGA Attributes

Device	System Gates	Equivalent Logic Cells	CLB Array (One CLB = Four Slices)				Distributed RAM bits <sup>(1)</sup>	Block RAM bits <sup>(1)</sup>	Dedicated Multipliers	DCMs	Maximum User I/O	Maximum Differential I/O Pairs
			Rows	Columns	Total CLBs	Total Slices						
XC3S100E	100K	2,160	22	16	240	960	15K	72K	4	2	108	40
XC3S250E	250K	5,508	34	26	612	2,448	38K	216K	12	4	172	68
XC3S500E	500K	10,476	46	34	1,164	4,656	73K	360K	20	4	232	92
XC3S1000E	1000K	18,516	68	46	2,108	8,376	138K	584K	36	8	364	144
XC3S1600E	1600K	33,192	76	58	3,688	14,752	231K	648K	36	8	376	156

**Notes:**

1. By convention, one Kb is equivalent to 1,024 bits.


**XC3S500E = 500K 'system gates'**

**46 rows, 34 columns**

**46 x 34 = 1564 positions**

**1,164 CLB's**

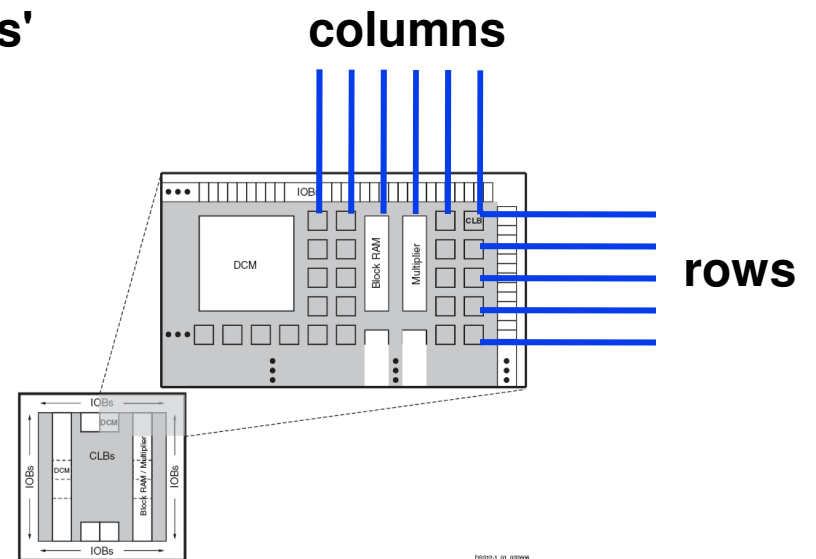**So 400 'positions' used for other things (RAM, ...)**



# Summary on 3ES500

Table 1: Summary of Spartan-3E FPGA Attributes

Device	System Gates	Equivalent Logic Cells	CLB Array (One CLB = Four Slices)				Distributed RAM bits <sup>(1)</sup>	Block RAM bits <sup>(1)</sup>	Dedicated Multipliers	DCMs	Maximum User I/O	Maximum Differential I/O Pairs
			Rows	Columns	Total CLBs	Total Slices						
XC3S100E	100K	2,160	22	16	240	960	15K	72K	4	2	108	40
XC3S250E	250K	5,508	34	26	612	2,448	38K	216K	12	4	172	68
<b>XC3S500E</b>	<b>500K</b>	<b>10,476</b>	<b>46</b>	<b>34</b>	<b>1,164</b>	<b>4,656</b>	<b>73K</b>	<b>360K</b>	<b>20</b>	<b>4</b>	<b>232</b>	<b>92</b>
XC3S1000E	1000K	18,516	68	46	2,108	8,432	138K	576K	36	8	364	144
XC3S1600E	1600K	33,192	76	58	3,688	14,752	231K	648K	36	8	376	156

**Notes:**

1. By convention, one Kb is equivalent to 1,024 bits.

**XC3S500E = 500K 'system gates'**


**1,164 CLB's**

**4,656 Slices**

**Each CLB contains 4 'Slices'**

**A Slice contains 2.25 LC's**

**2.25 x 4,656 = 10,476**

 

# Summary on 3ES500

Table 1: Summary of Spartan-3E FPGA Attributes

Device	System Gates	Equivalent Logic Cells	CLB Array (One CLB = Four Slices)				Distributed RAM bits <sup>(1)</sup>	Block RAM bits <sup>(1)</sup>	Dedicated Multipliers	DCMs	Maximum User I/O	Maximum Differential I/O Pairs
			Rows	Columns	Total CLBs	Total Slices						
XC3S100E	100K	2,160	22	16	240	960	15K	72K	4	2	108	40
XC3S250E	250K	5,508	34	26	612	2,448	38K	216K	12	4	172	68
XC3S500E	500K	10,476	46	34	1,164	4,656	73K	360K	20	4	232	92
XC3S1000E	1000K	20,952	68	46	2,328	9,312	146K	720K	40	8	464	184
XC3S1600E	1600K	33,192	76	58	3,688	14,752	231K	648K	36	8	376	156

**Notes:**

1. By convention, one Kb is equivalent to 1,024 bits.


**XC3S500E = 500K 'system gates'**

**1,164 CLB's**

**4,656 Slices**

 **73K 'Distributed RAM' Bits**

**Each Slice contains  
4 x 4 bits = 16 bits of 'RAM'  
4,656 x 16 = 74496 = 72.75K**



# Summary on 3ES500

Table 1: Summary of Spartan-3E FPGA Attributes

Device	System Gates	Equivalent Logic Cells	CLB Array (One CLB = Four Slices)				Distributed RAM bits <sup>(1)</sup>	Block RAM bits <sup>(1)</sup>	Dedicated Multipliers	DCMs	Maximum User I/O	Maximum Differential I/O Pairs
			Rows	Columns	Total CLBs	Total Slices						
XC3S100E	100K	2,160	22	16	240	960	15K	72K	4	2	108	40
XC3S250E	250K	5,508	34	26	612	2,448	38K	216K	12	4	172	68
XC3S500E	500K	10,476	46	34	1,164	4,656	73K	360K	20	4	232	92
XC3S1000E	1000K	16,518	68	46	1,808	7,232	138K	576K	36	8	364	144
XC3S1600E	1600K	33,192	76	58	3,688	14,752	231K	648K	36	8	376	156

**Notes:**

1. By convention, one Kb is equivalent to 1,024 bits.


**XC3S500E = 500K 'system gates'**

**1,164 CLB's**

**4,656 Slices**

**360K of Block RAM bits  
18 Kbit per Block RAM**

**Thus  $360/18 = 20$  Block RAM**

 

# Summary on 3ES500

Table 1: Summary of Spartan-3E FPGA Attributes

Device	System Gates	Equivalent Logic Cells	CLB Array (One CLB = Four Slices)				Distributed RAM bits <sup>(1)</sup>	Block RAM bits <sup>(1)</sup>	Dedicated Multipliers	DCMs	Maximum User I/O	Maximum Differential I/O Pairs
			Rows	Columns	Total CLBs	Total Slices						
XC3S100E	100K	2,160	22	16	240	960	15K	72K	4	2	108	40
XC3S250E	250K	5,508	34	26	612	2,448	38K	216K	12	4	172	68
XC3S500E	500K	10,476	46	34	1,164	4,656	73K	360K	20	4	232	92
XC3S1000E	1000K	20,952	68	46	2,328	9,312	146K	720K	40	8	464	184
XC3S1600E	1600K	33,192	76	58	3,688	14,752	231K	648K	36	8	376	156

**Notes:**

1. By convention, one Kb is equivalent to 1,024 bits.

**XC3S500E = 500K 'system gates'**


**1,164 CLB's**

**4,656 Slices**

**360K of Block RAM bits**

**20 Multipliers**

 **Next to each Block RAM there is a multiplier cell**





# Now, we also understand tool output

## The SHA-1 Design, revisited

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Flip Flops	503	9,312	5%	
Number of 4 input LUTs	1,676	9,312	17%	
Logic Distribution				
Number of occupied Slices	995	4,656	21%	
Number of Slices containing only related logic	995	995	100%	
Number of Slices containing unrelated logic	0	995	0%	
Total Number of 4 input LUTs	1,836	9,312	19%	
Number used as logic	1,676			
Number used as a route-thru	32			
Number used as Shift registers	128			
Number of bonded IOBs	196	232	84%	
Number of GCLKs	1	24	4%	
Total equivalent gate count for design	24,308			
Additional JTAG gate count for IOBs	9,408			

# Now, we also understand tool output

## The SHA-1 Design, revisited

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Flip Flops	503	9,312	5%	
Number of 4 input LUTs	1,676	9,312	17%	
<b>Logic Distribution</b>				
Number of occupied Slices	995	4,656	21%	
Number of Slices containing only related logic	995	995	100%	
Number of Slices containing unrelated logic	0	995	0%	
<b>Total Number of 4 input LUTs</b>	<b>1,836</b>	<b>9,312</b>	<b>19%</b>	
Number used as logic	1,676			
Number used as a route-thru	32			
Number used as Shift registers	128			
Number of bonded IOBs	196	232	84%	
Number of GCLKs	1	24	4%	
<b>Total equivalent gate count for design</b>	<b>24,308</b>			
Additional JTAG gate count for IOBs	9,408			

**Used 995 Slices ( $2 \times 995 = 1990$  LUT's at most)**

**Used 1836 LUTs of 1990 possible LUTs**

**Used 1676 of 1836 occupied LUTs for actual logic**

**Used 503 Flip Flops of ( $2 \times 995 = 1990$  Flip Flops at most)**

# Summary FPGA

---

- FPGA contains 5 elements + interconnection network
  - CLB
  - RAM
  - Multiplier
  - DCM
  - IOB
  
- A 'gate-level netlist' is mapped on an FPGA by configuring these elements
  - Choose CLB configuration (LUT, flip-flop, carry logic, ..)
  - Choose interconnections in network