
ECE 4514 Digital Design II Spring 2008

Lecture 15: FSM-based Control

A Design Lecture


Patrick Schaumont

Overview


- ❑ Finite State Machines
 - Verilog Mapping: one, two, three always blocks
- ❑ State Encoding
 - User-defined or tool-defined
 - State encoding techniques: one-hot, user-defined, gray
- ❑ Synthesis Issues
 - Default state assignment
 - Safe Implementations
 - Next-state logic: RAM or LUT
- ❑ FSM-based control of Datapath (gcd)

Finite State Machine Template

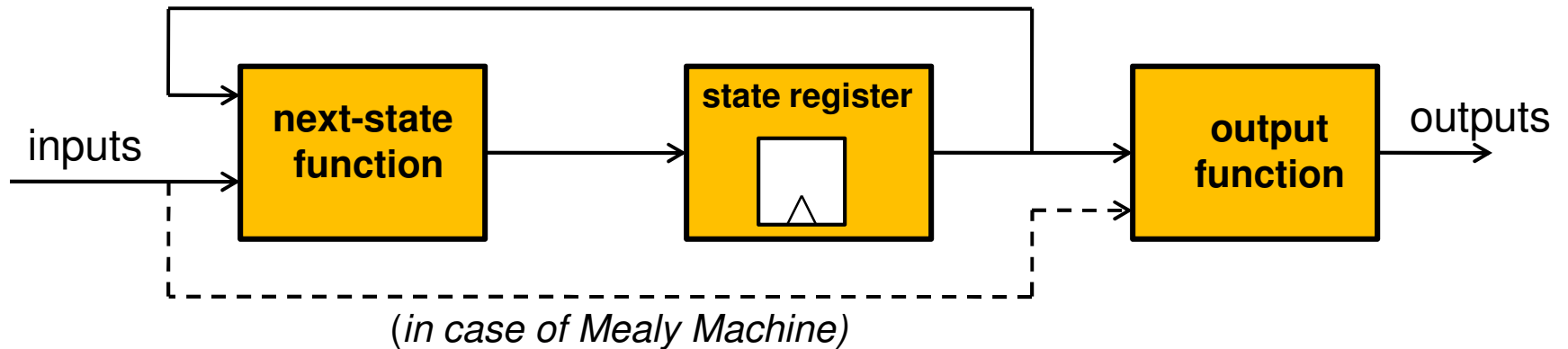
- Sequential Machine defined by
 - Set of Inputs and Outputs
 - Set of States
 - Initial State (reset function)
 - State Transitions




Design Process

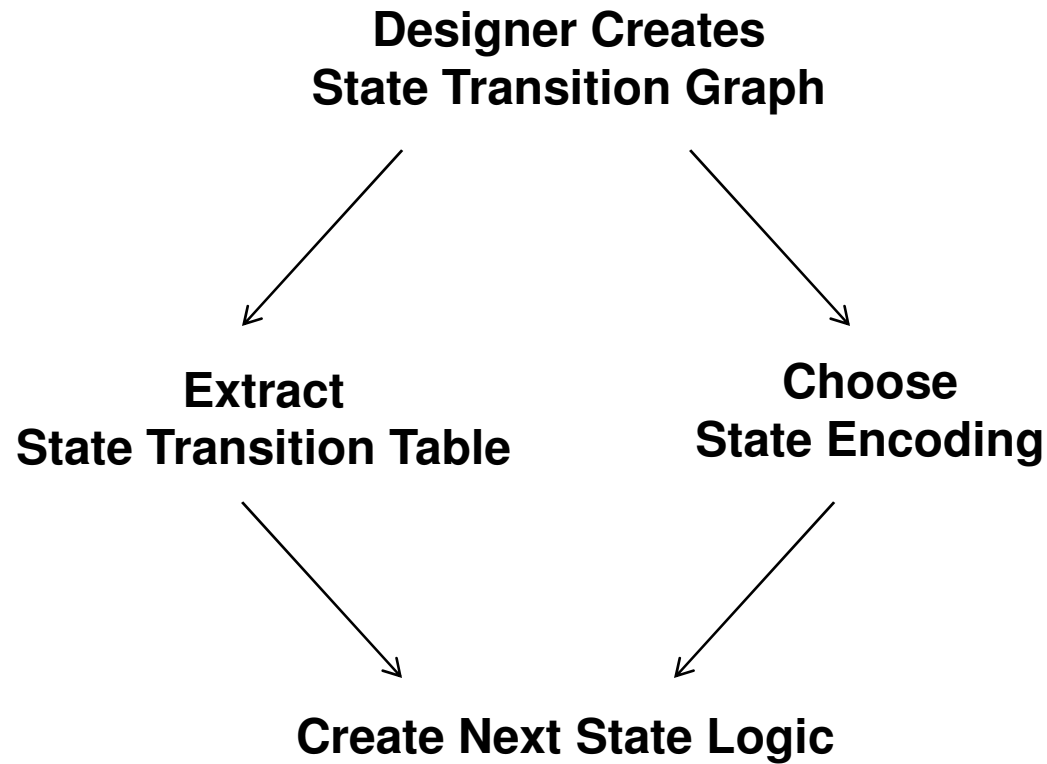

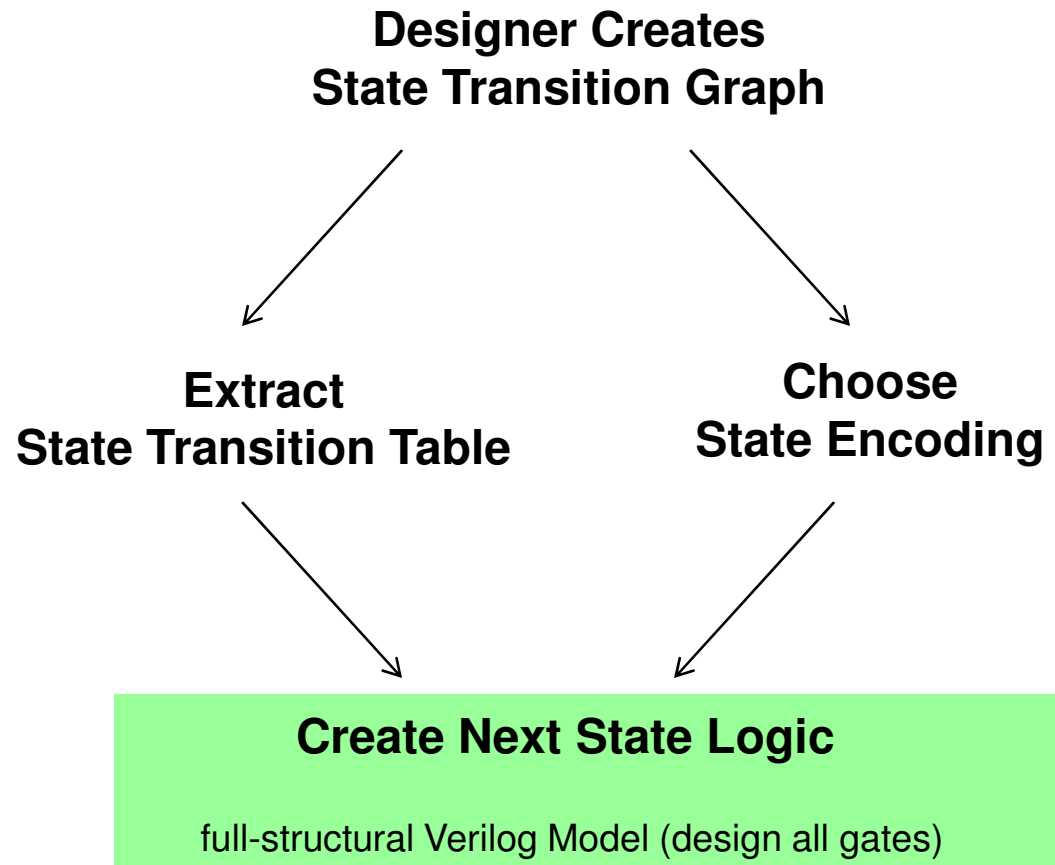

Design Process

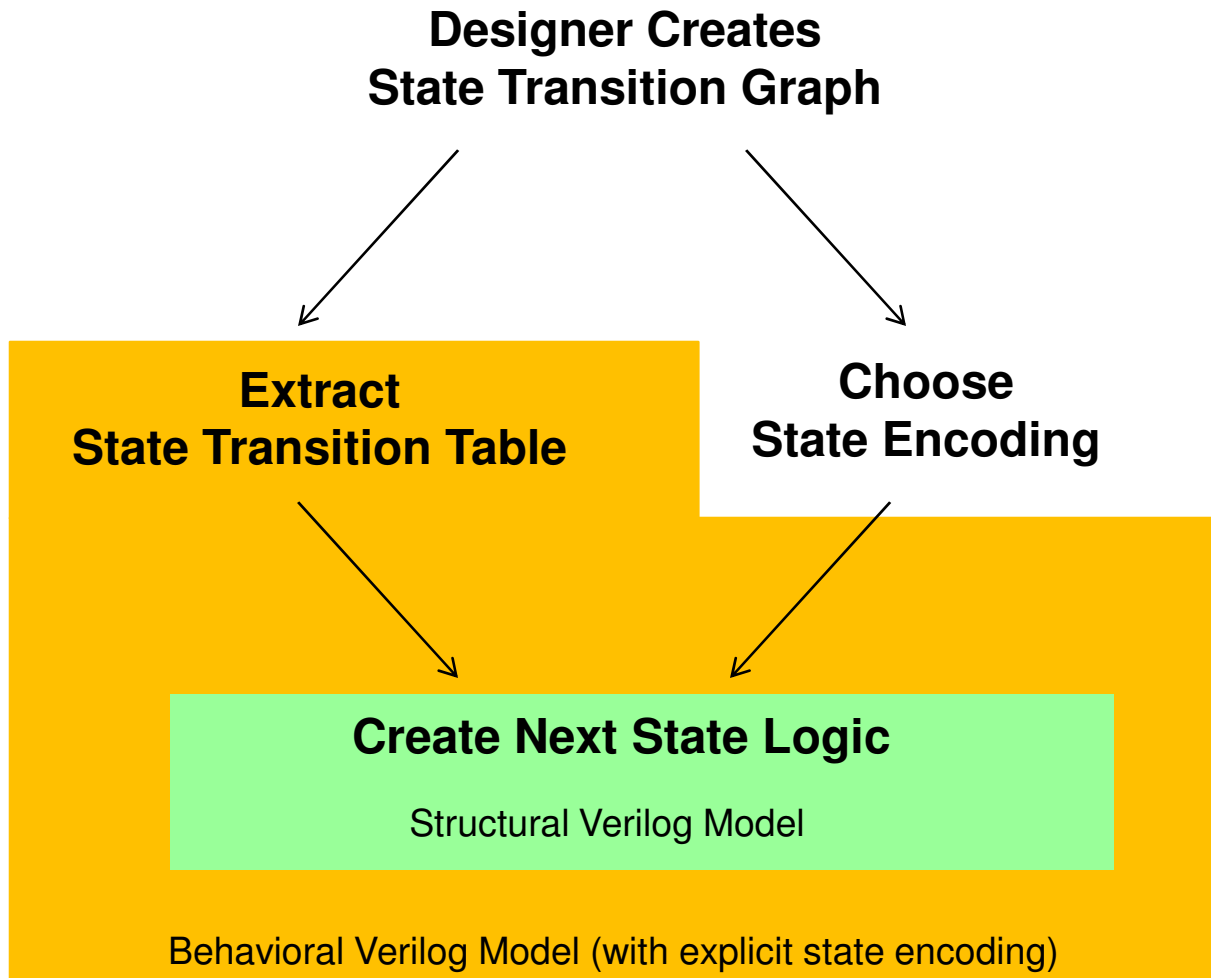


Design Process



Design Process


We will focus on  and 

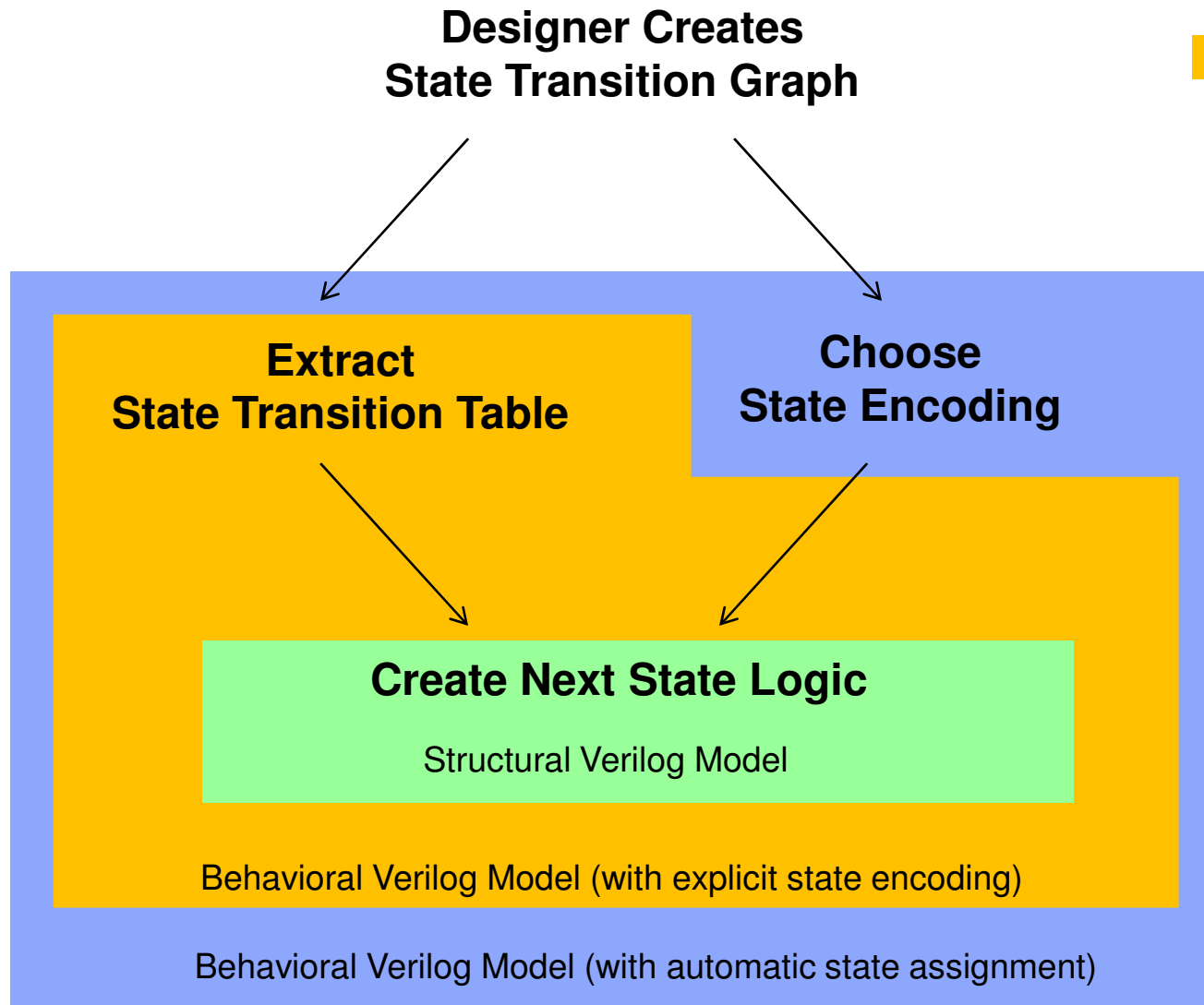

 Example FSM Design

- Create an FSM that turns the first '1' of a string of consecutive '1' into a '0'.

Each clock cycle, a new input is provided



Example FSM Design


□ How many states?

Input	1	0	1	0	0	0	1	1	1	0	0	1	1	1	1	1	1
Output	0	0	0	0	0	0	0	1	1	0	0	0	1	1	1	1	1

Example FSM Design

□ How many states?

Input	1	0	1	0	0	0	1	1	1	0	0	1	1	1	1	1	1
Output	0	0	0	0	0	0	0	1	1	0	0	0	1	1	1	1	1

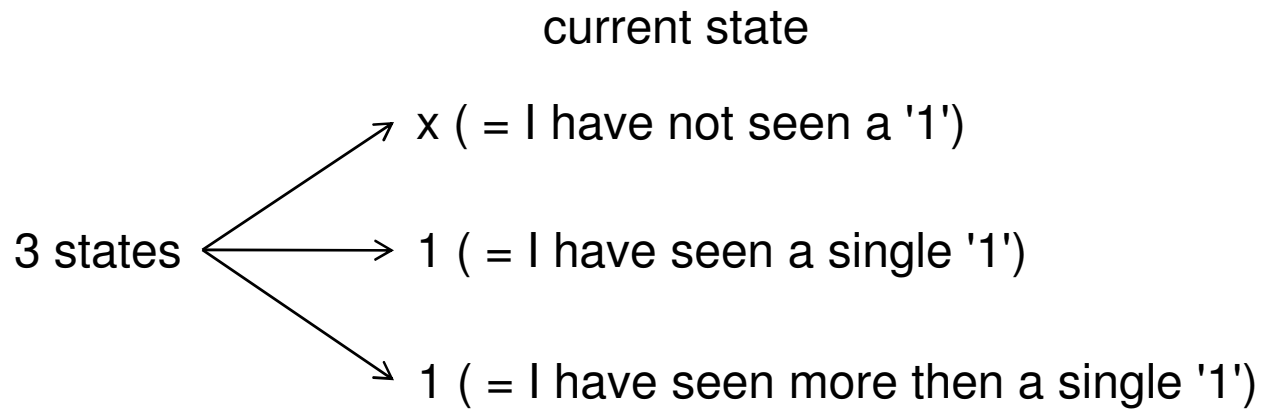

Example FSM Design

□ How many states?

Input	1	0	1	0	0	0	1	1	1	0	0	1	1	1	1	1	1
Output	0	0	0	0	0	0	0	1	1	0	0	0	1	1	1	1	1

S0


S1

S2

Example FSM Design

□ How many states?

Input	1	0	1	0	0	0	1	1	1	0	0	1	1	1	1	1	1
Output	0	0	0	0	0	0	0	1	1	0	0	0	1	1	1	1	1

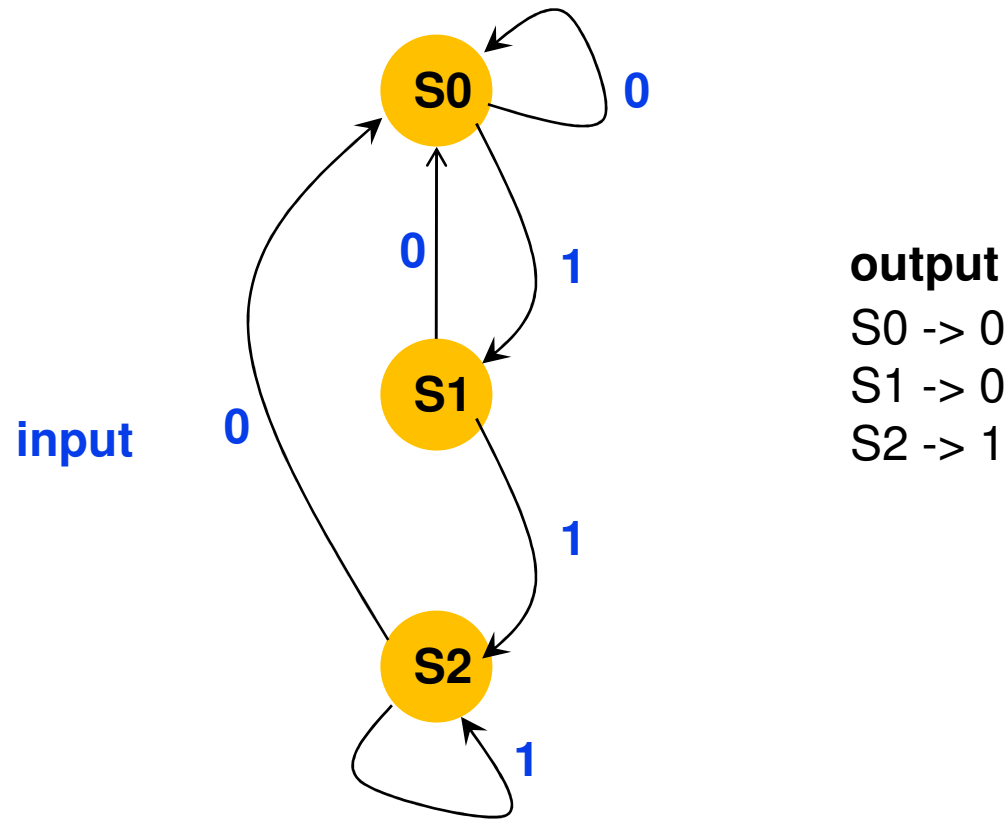

Verilog Mapping of FSM - Generic Ideas

- ❑ Use 'parameter' to express state encoding


```
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;
```

- ❑ This is a *symbolic* encoding, not necessarily the encoding that will be used by the synthesis tool
- ❑ Use standard conventions for coding logic
 - Use non-blocking <= for registers, specify correct reset and edge-triggered behavior
 - Use blocking = for combinational logic, make sure sensitivity lists are complete

 Example FSM Design - Verilog Mapping I

```
module fsm(q, i, clk, rst);
  input i, clk, rst;
  output q;
  reg q;
  reg [1:0] state;
  parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;

  always @(posedge clk or posedge rst)
    if (rst) begin
      state <= s0; q <= 1'b0;
    end else begin
      case (state)
        s0: if (i == 1'b1) begin
              state <= s1;
              q <= 1'b0;
            end else begin
              state <= s0;
              q <= 1'b0;
            end
        s1: ..
        s2: ..
      endcase
    end
endmodule
```



output


S0 -> 0

S1 -> 0

S2 -> 1

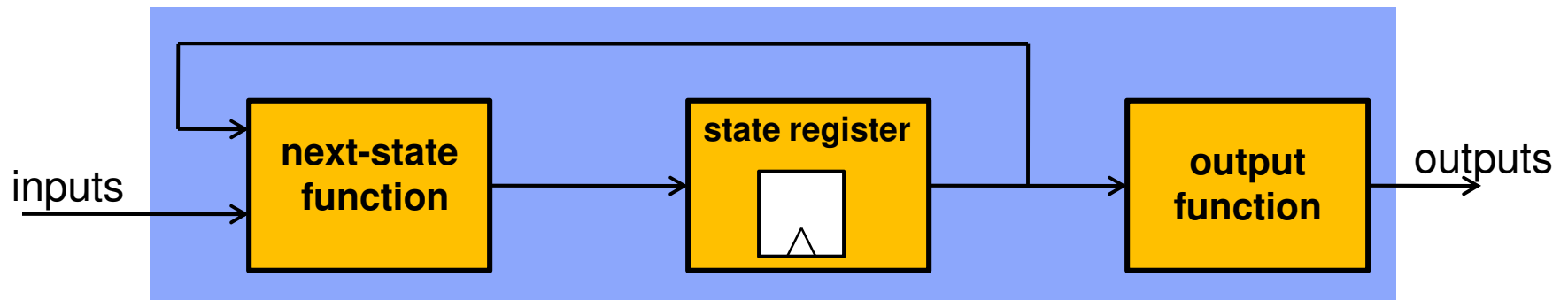Example FSM Design - Verilog Mapping I


- ❑ One single always block
 - Reset and update in same block
 - Output will always have a register (not always desired ..)



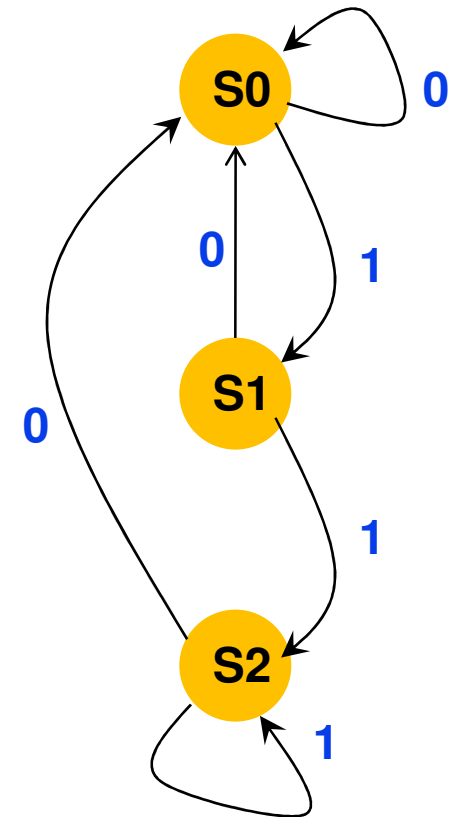Example FSM Design - Verilog Mapping II

```
reg q;  
reg [1:0] state;  
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;  
  
always @(posedge clk or posedge rst)  
  if (rst)  
    state <= s0;  
  else  
    case (state)  
      s0: if (i == 1'b1)  
          state <= s1;  
        else  
          state <= s0;  
      s1: ..  
      s2: ..  
    endcase
```

```
always @(state)  
  q = 1'b0; // default assignment  
  case (state)  
    s0: q = 1'b0;  
    s1: q = 1'b0;  
    s2: q = 1'b1;  
  endcase
```



output


S0 -> 0

S1 -> 0

S2 -> 1

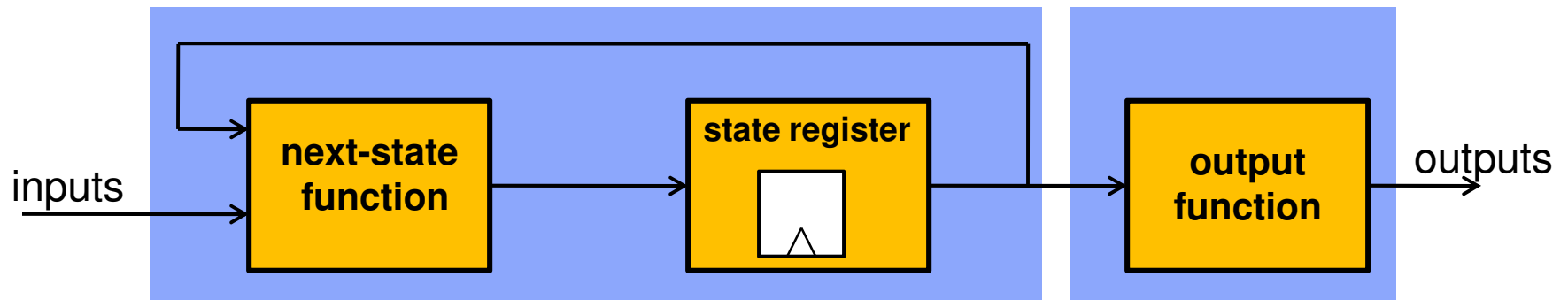Example FSM Design - Verilog Mapping II

- ❑ Two always block
 - Reset and update still in same block
 - Output can be combinational



Example FSM Design - Verilog Mapping III


```
reg q;  
reg [1:0] state, next_state;  
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;
```

```
always @(posedge clk or posedge rst)  
  if (rst)  
    state <= s0;  
  else  
    state <= next_state;
```

```
always @(state or i) begin  
  next_state = s0;  
  case (state)  
    s0: if (i == 1'b1)  
        next_state = s1;  
      else  
        next_state = s0;  
    s1: ..  
  endcase  
end
```

```
always @(state)  
  // output encoding
```

endmodule

 

output


S0 -> 0

S1 -> 0

S2 -> 1

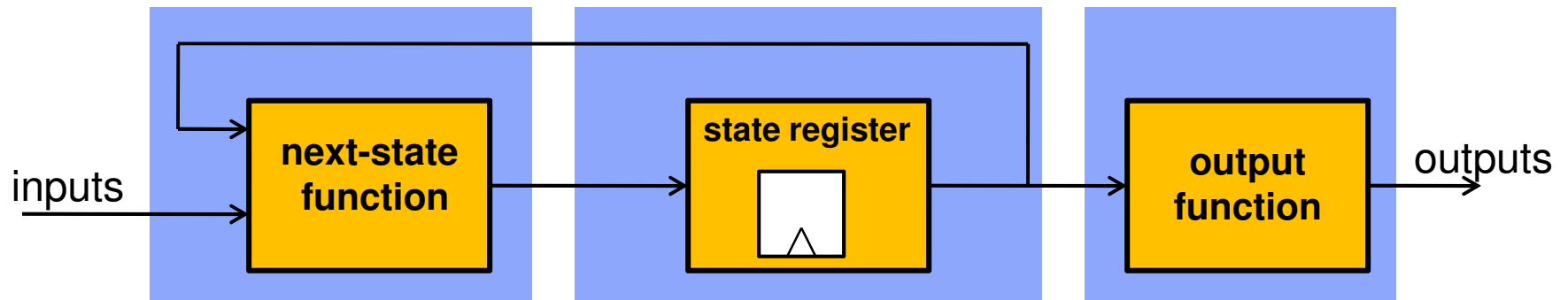Example FSM Design - Verilog Mapping III

- ❑ Three always block
 - Reset and update in different blocks
 - Output can be combinational



One, two, three always block

	1 always block	2 always block	3 always block	
Combinational Output		✓	✓	
Reset/Update separate from next-state Logic			✓	

Synthesis of FSM

□ Output of XST on Example 1 (single always block):

```
=====
*                               HDL Synthesis                               *
=====



Performing bidirectional port resolution...

Synthesizing Unit <myfsm>.
  Related source file is "myfsm.v".
  Found finite state machine <FSM_0> for signal <state>.
-----
| States           | 3 |
| Transitions     | 6 |
| Inputs          | 1 |
| Outputs         | 3 |
| Clock           | clk (rising_edge) |
| Reset           | rst (positive) |
| Reset type      | asynchronous |
| Reset State     | 00 |
| Encoding        | automatic |
| Implementation  | LUT |
-----

Found 1-bit register for signal <q>.
Summary:
  inferred 1 Finite State Machine(s).
  inferred 1 D-type flip-flop(s).
Unit <myfsm> synthesized.
```

Synthesis tool treats FSM
as a separate entity

RTL Schematic

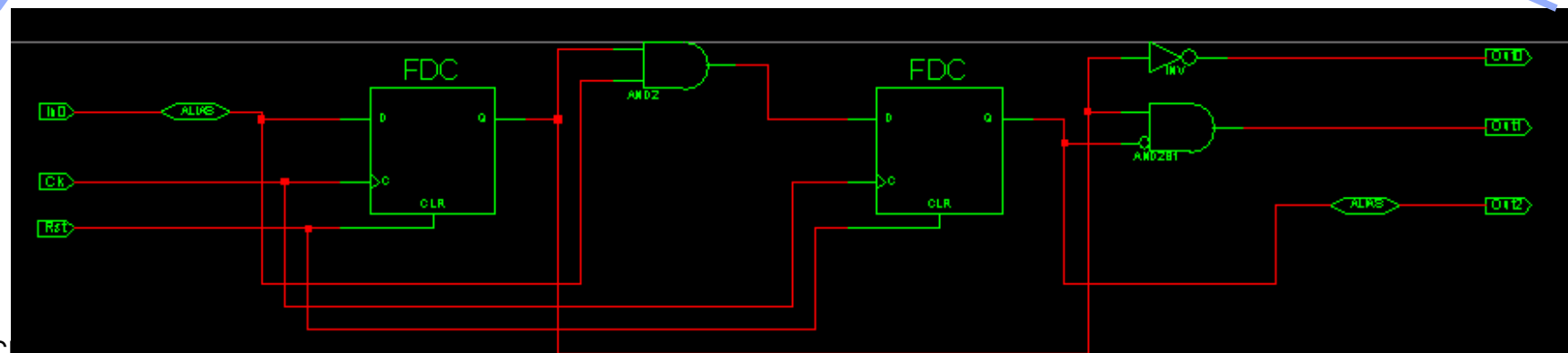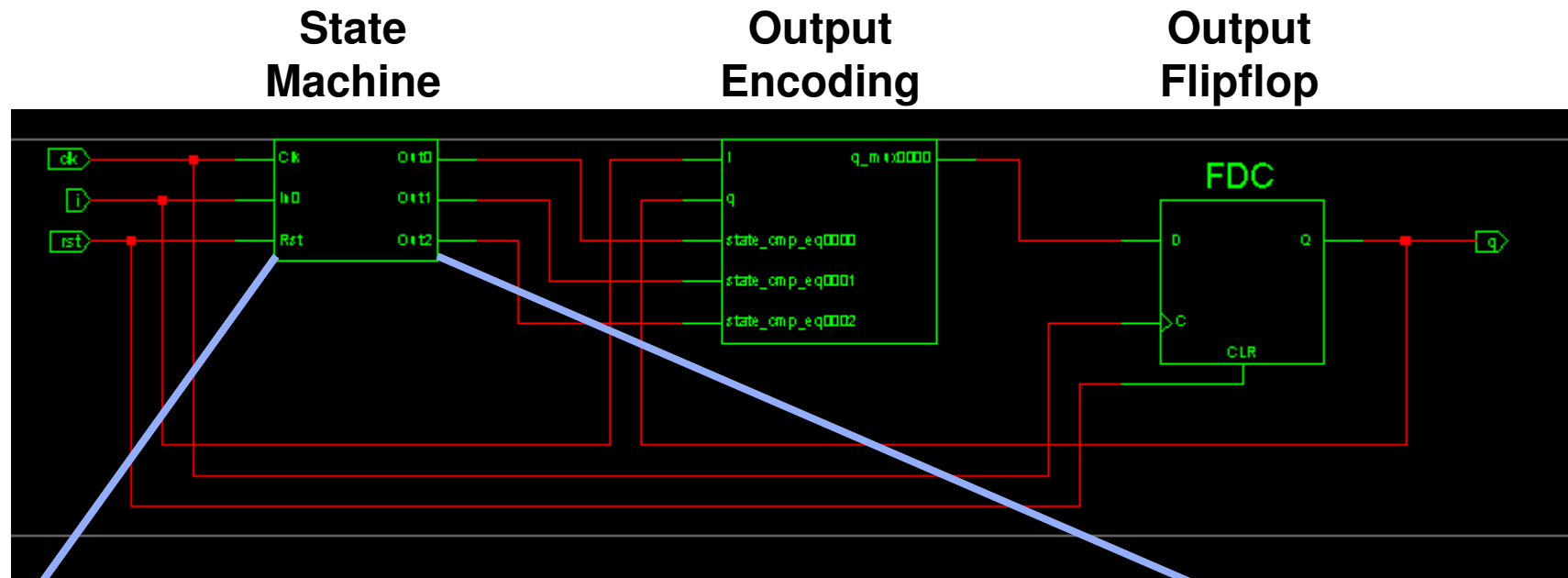

Synthesis of FSM

```
=====
*                               Advanced HDL Synthesis                               *
=====
```

```
Analyzing FSM <FSM_0> for best encoding.
Optimizing FSM <state> on signal <state[1:2]> with gray encoding.
```

State	Encoding
00	00
01	01
10	11

↓
This encoding style was chosen by the tool
(encoding is selected to be 'automatic')

↓ ↘
This encoding is used in actual implementation
This state was chosen in parameter entry

```
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;
```


Gray Encoding ?

- A binary code in which subsequent words differ by only a single bit

1-bit gray code 0
 1

2-bit gray code 00
 01
 ——— mirror
 11
 10

 3-bit gray code 000
 001
 011
 010 mirror
 ———
 110
 111
 101
 100




Gray Codes require minimal logic transitions to go from one state to the next. (= minimal power consumption, minimal risk for glitches & hazards)


What other types of encoding are common ?

□ One-hot:

 - Select one bit for each state
- Each state transition flips only two bits
- Good for FPGA (with lots of flip-flops)
- Not so efficient with large number of states or large number of state transitions, because state-decoding becomes too big



one-hot encoding
with 16 states

 


normal encoding
with 16 states

What other types of encoding are common ?

□ Sequential:

 - Encode successive states in sequence
- Simplifies next-state logic if there are long sequences



□ User-defined:

- Keeps the same encoding as specified by the designer

```
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;
```

□ Synthesis tool tries to select a good encoding automatically


- This choice is only a heuristic !

Can we enforce the encoding?

- ❑ What if we insist that the encoding should be User-defined:

```
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;
```

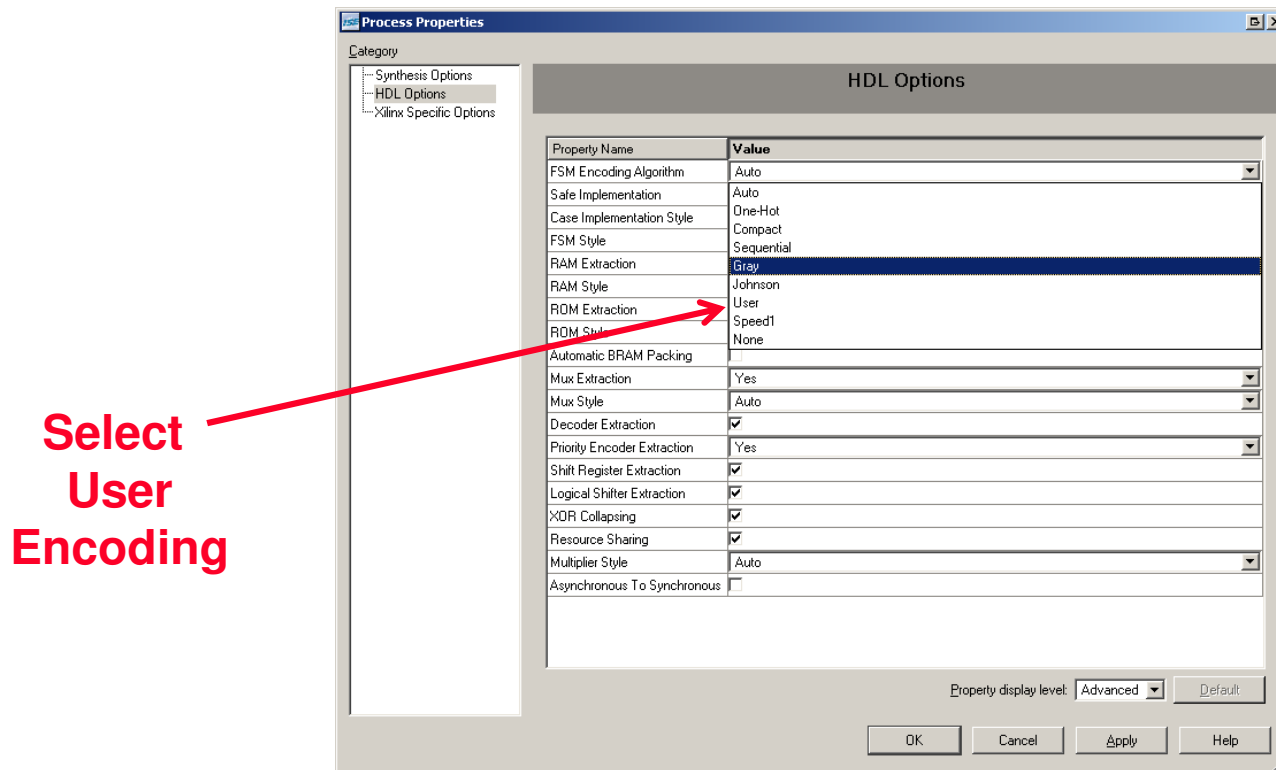- ❑ Solution 1: Change encoding option in the synthesis tool



Can we enforce the encoding?

- ❑ What if we insist that the encoding should be User-defined:

```
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;
```

- ❑ Solution 2: Provide pragma in the Verilog Code
(This is also called a *synthesis constraint*)

```
(* fsm_encoding = user *)  
  
module fsm(q, i, clk, rst);  
    input i, clk, rst;  
    output q;  
    reg q;  
    reg [1:0] state;  
    parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;  
    ...  
endmodule
```

Example 1 with one-hot encoding

```
(* fsm_encoding = one-hot *)


module fsm(q, i, clk, rst);
  input i, clk, rst;
  output q;
  reg q;
  reg [1:0] state;
  parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;
  ...
endmodule
```

```
=====
*                               Advanced HDL Synthesis                               *
```

```
=====
Optimizing FSM <state> on signal <state[1:3]> with one-hot encoding.
```

```
-----
State | Encoding
-----
00    | 001
01    | 010
10    | 100
-----
```

Example 1 with one-hot encoding

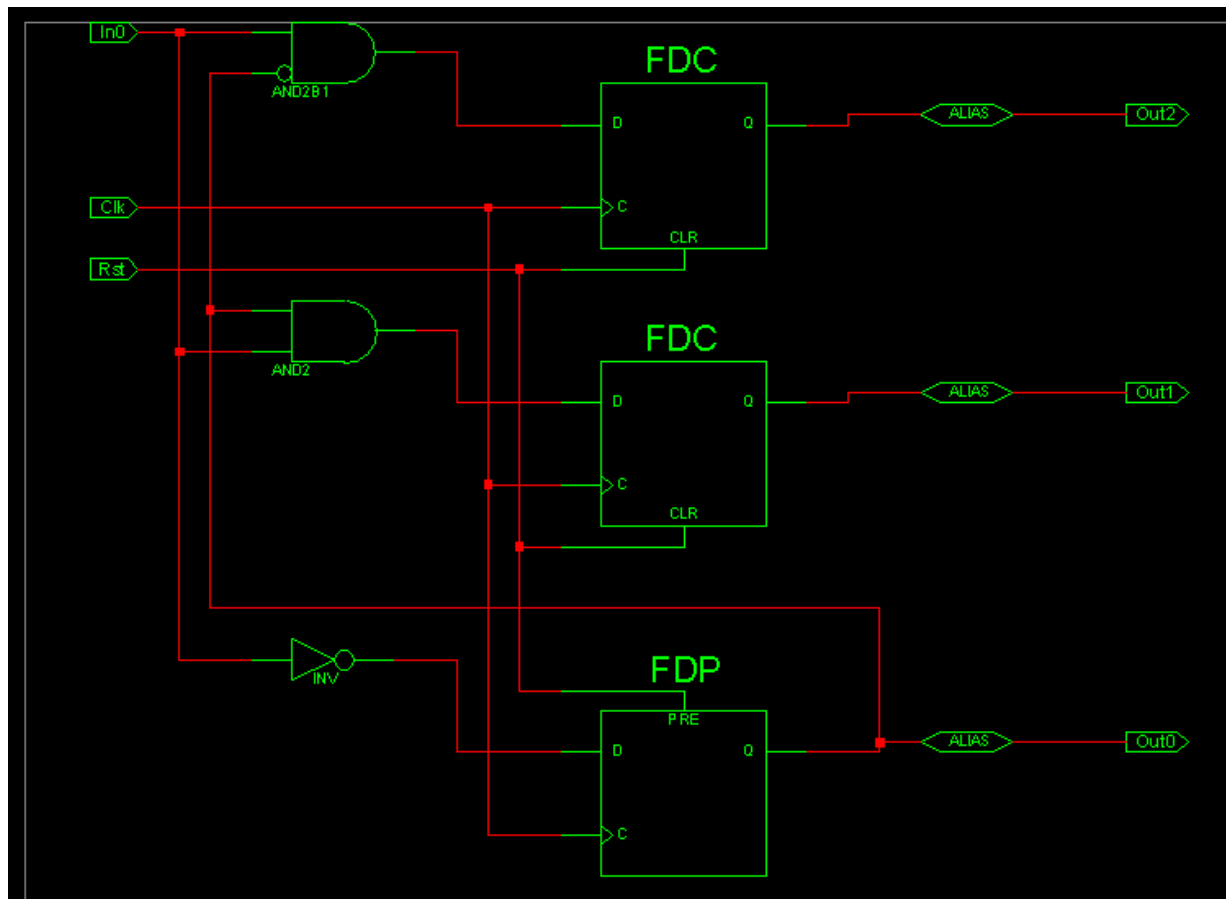

Another way of writing one-hot state encoding

```
reg q;  
reg [2:0] state, next_state;  
parameter s0 = 3'd0, s1 = 3'd1, s2 = 3'd2;
```

index into
state register

```
always @(posedge clk or posedge rst)  
  if (rst)  
    state <= 3'd1;  
  else  
    state <= next_state;
```

```
always @(state or i) begin  
  next_state = 3'd0;  
  case (1'b1)  
    state[s0]: if (i == 1'b0)  
      next_state[s1] = 1'd1;  
      else  
        next_state[s0] = 1'd1;  
    state[s1]: ..  
  endcase  
end
```

next-state
selection

*This example is not recognized as a finite state machine by XST,
so that the user-specified encoding will be used.*


Default State Assignment

```
reg q;  
reg [1:0] state, next_state;  
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;
```

```
always @(posedge clk or posedge rst)  
  if (rst)  
    state <= s0;  
  else  
    state <= next_state;
```

```
always @(state or i) begin  
  next_state = s0;  
  case (state)  
    s0: if (i == 1'b0)  
        next_state = s1;  
        else  
        next_state = s0;  
    s1: ..  
  endcase  
end
```

 
```
always @(state)  
  // output encoding
```



**Default next-state assignment
may deal with improper
initialization and faults**

Safe Implementation

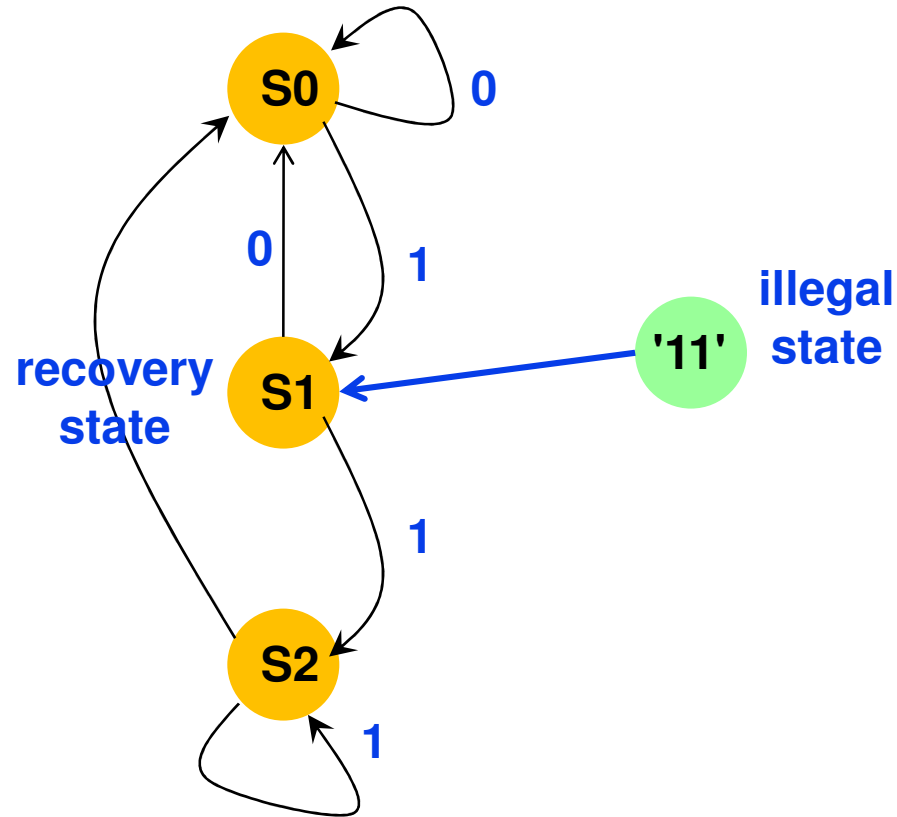
- A 'Safe FSM' is an FSM that will convert each invalid state automatically to a recovery state (usually the reset state)



Default (unsafe) implementation

```
module fsm(q, i, clk, rst);
  input i, clk, rst;
  output q;
  reg q;
  reg [1:0] state;
  parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;


 
  always @(posedge clk or posedge rst)
    if (rst) begin
      state <= s0; q <= 1'b0;
    end else begin
      case (state)
        s0: if (i == 1'b0) begin
              state <= s1;
              q <= 1'b0;
            end else begin
              state <= s0;
              q <= 1'b0;
            end
        s1: ..
        s2: ..
      endcase
    end
endmodule
```



Cannot 'escape' from state '11'

output
S0 -> 0
S1 -> 0
S2 -> 1


Default (unsafe) implementation

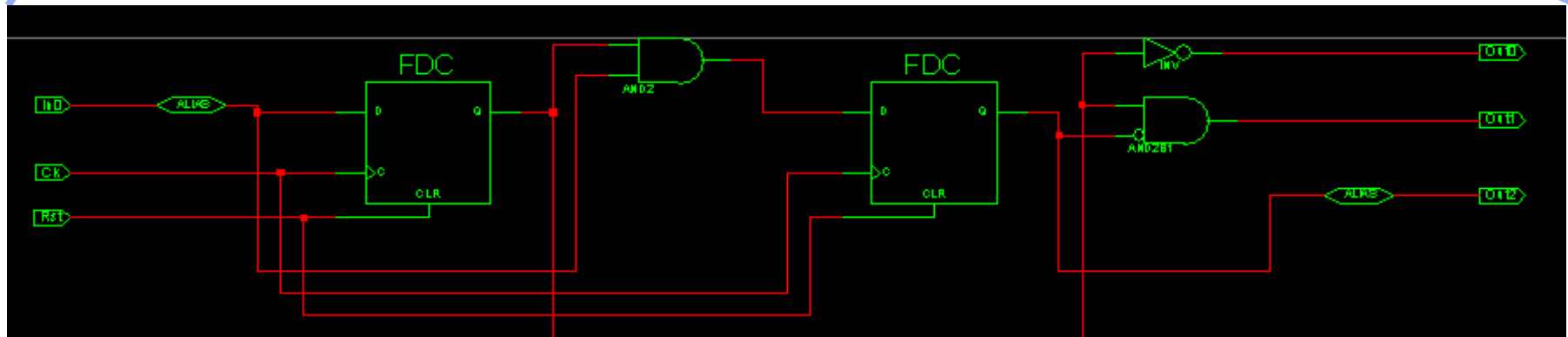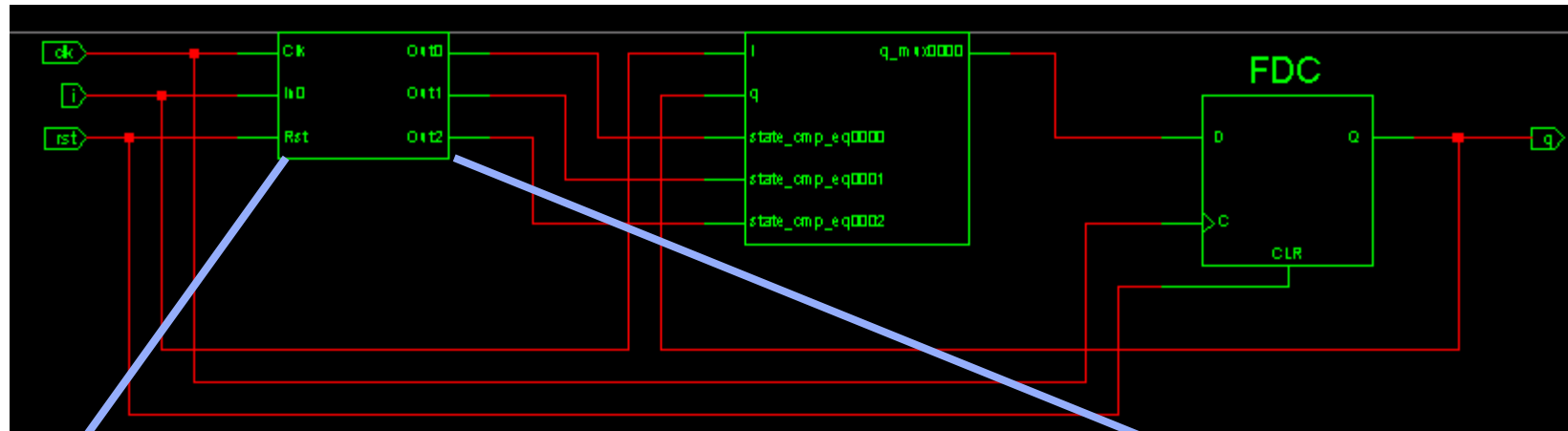


state flip-flop

state flip-flop

Default (unsafe) implementation

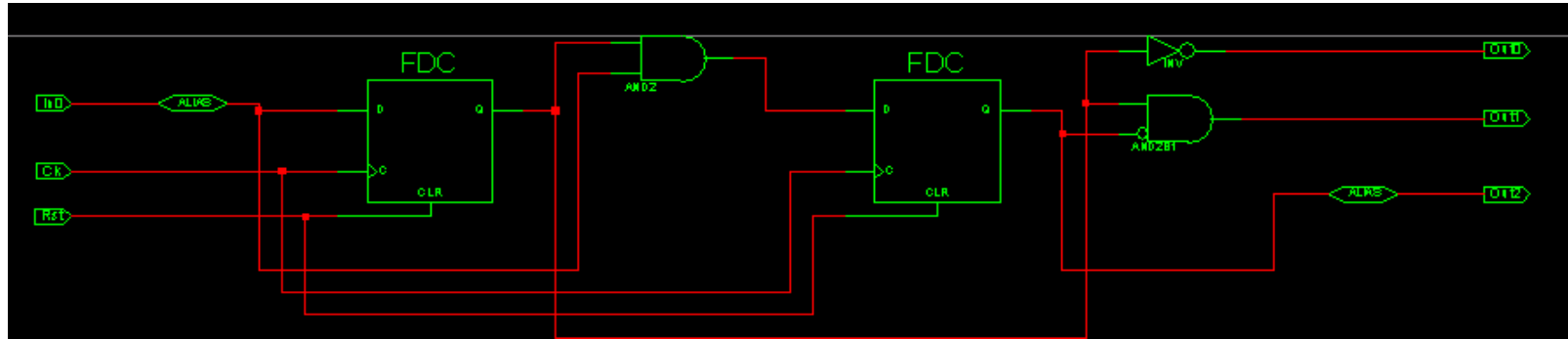


s0
s1
s2

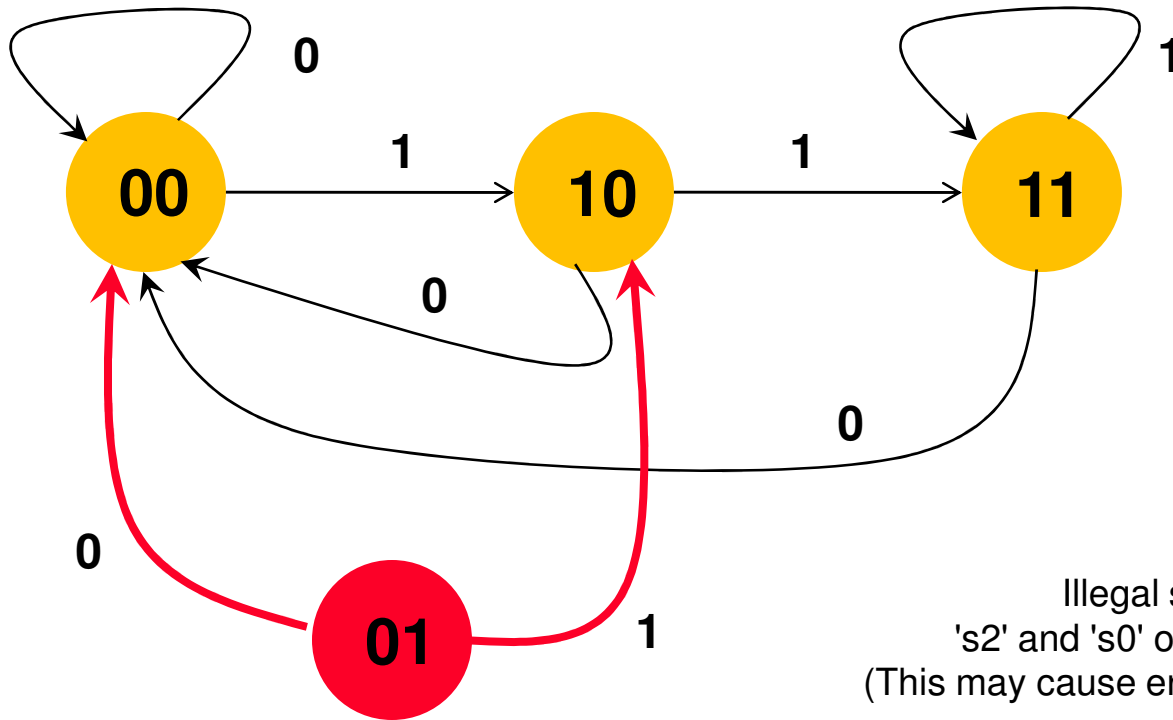


Illegal state '01' will drive 's2' and 's0' output simultaneously high (This may cause errors in output encoding block)

Safe Implementation

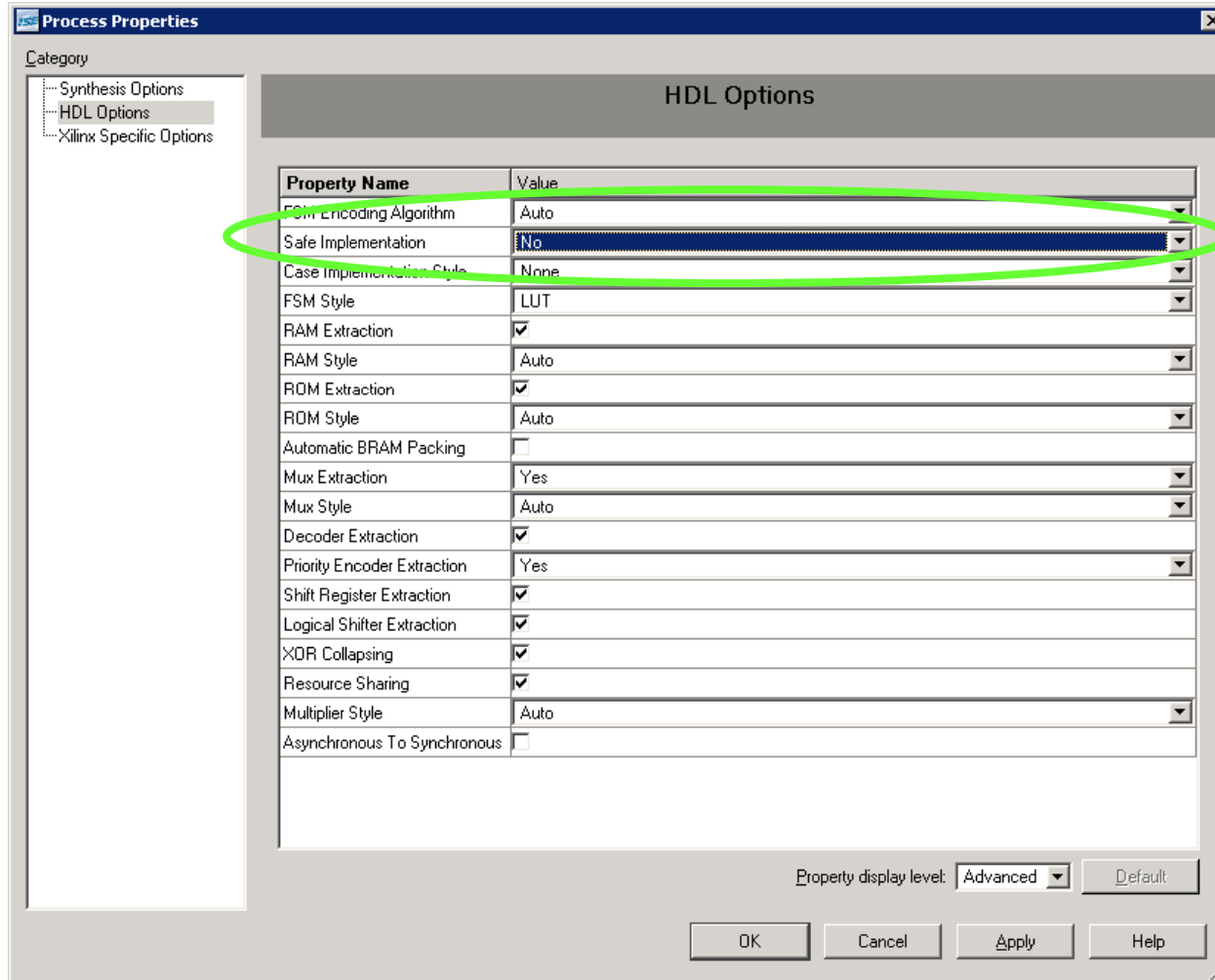- ❑ Specified with tool option or Verilog code pragma




Safe Implementation

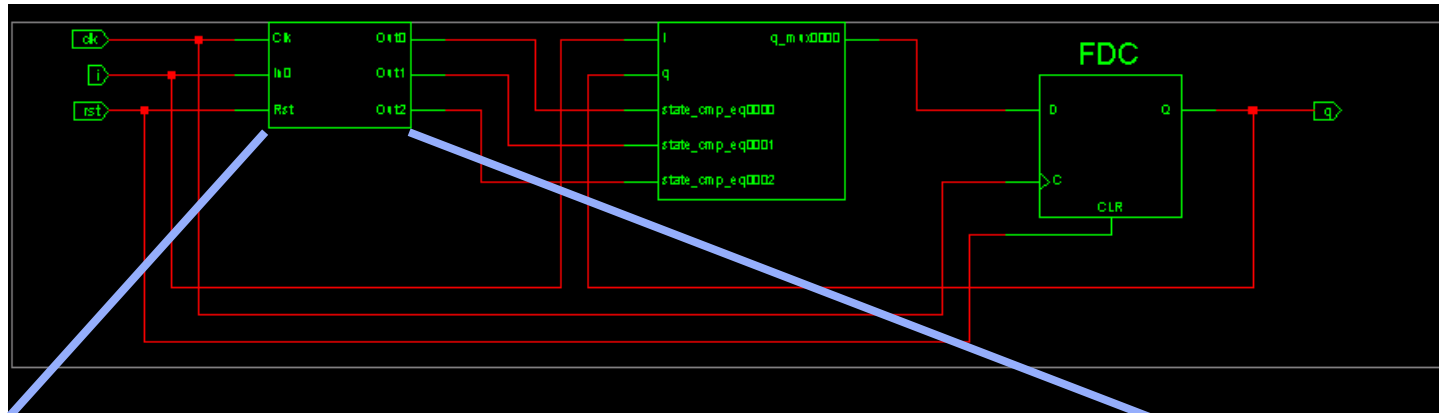

next-state logic



next-state logic

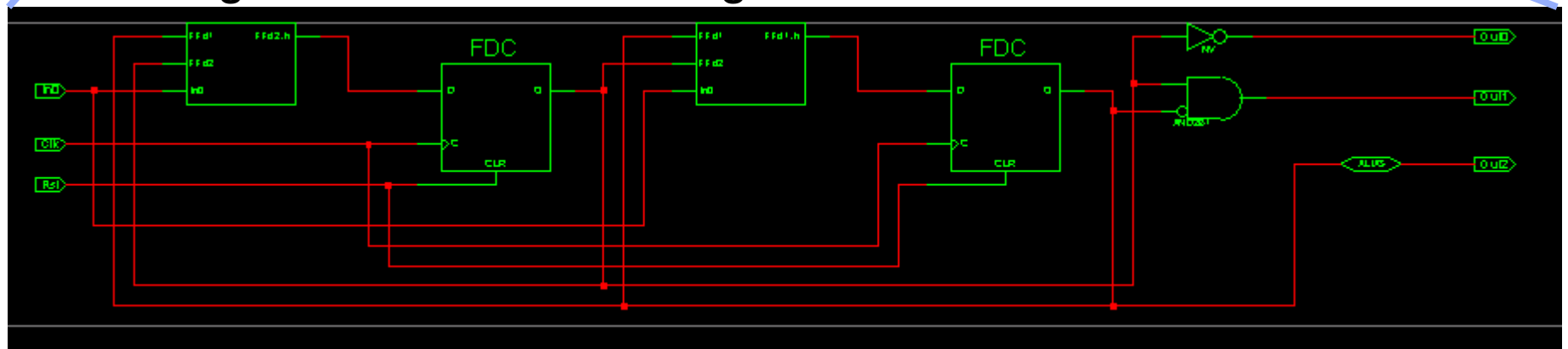

state flip-flop



state flip-flop

Safe Implementation

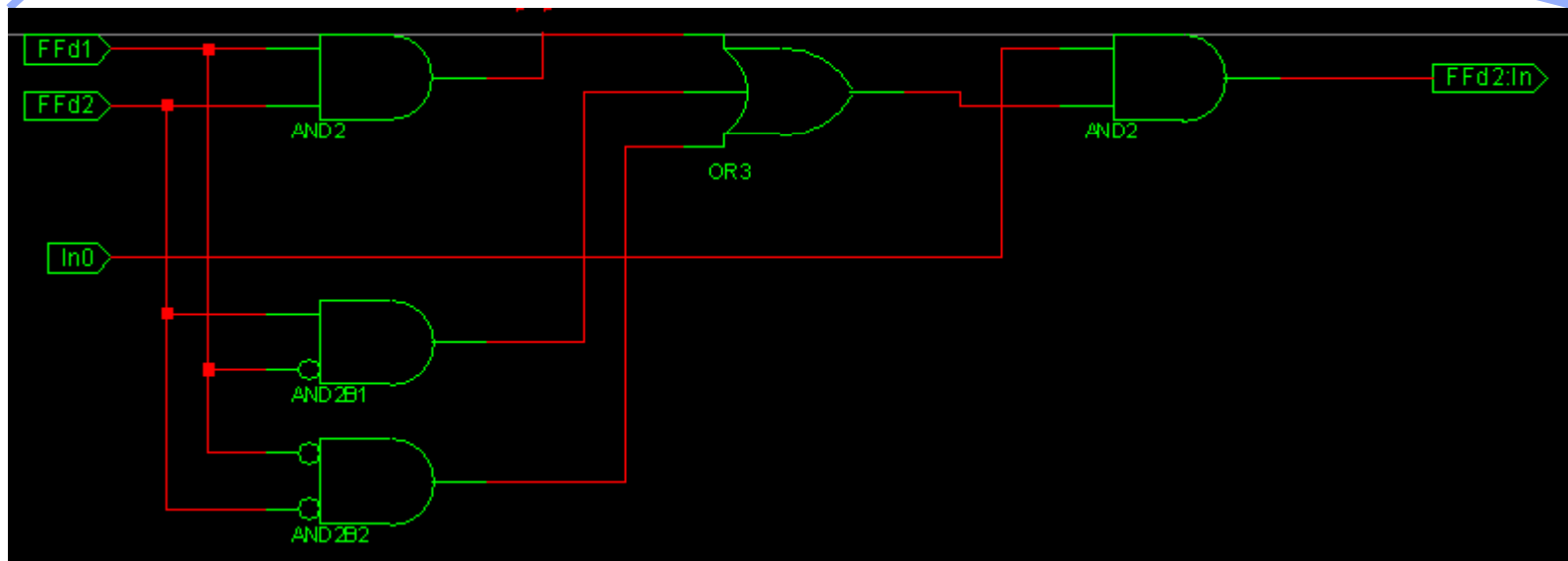 

$$f2 = (f1.f2 + !f1.f2 + !f1.!f2) . (in1)$$

Safe Implementation

  

$$f1 = (f1.f2 + !f1.f2 + !f1.!f2) . (in.f2)$$

Safe Implementation

$$f1 = (f1.f2 + !f1.f2 + !f1.!f2) . (in.f2)$$


$$f2 = (f1.f2 + !f1.f2 + !f1.!f2) . (in1)$$

—→ **f1. f2 will always be one of {00, 01, 11}.**
State 10 cannot appear (will be immediately converted into 00)

- ❑ Safe Implementations are used when proper, precisely defined operation is more important than cost (area, performance)
- ❑ Related concept: fault tolerance.
 - Design of digital architectures that can withstand the presence of faults
 - Usually implemented using redundancy (replicating functions in time or space).


RAM-based next-state logic

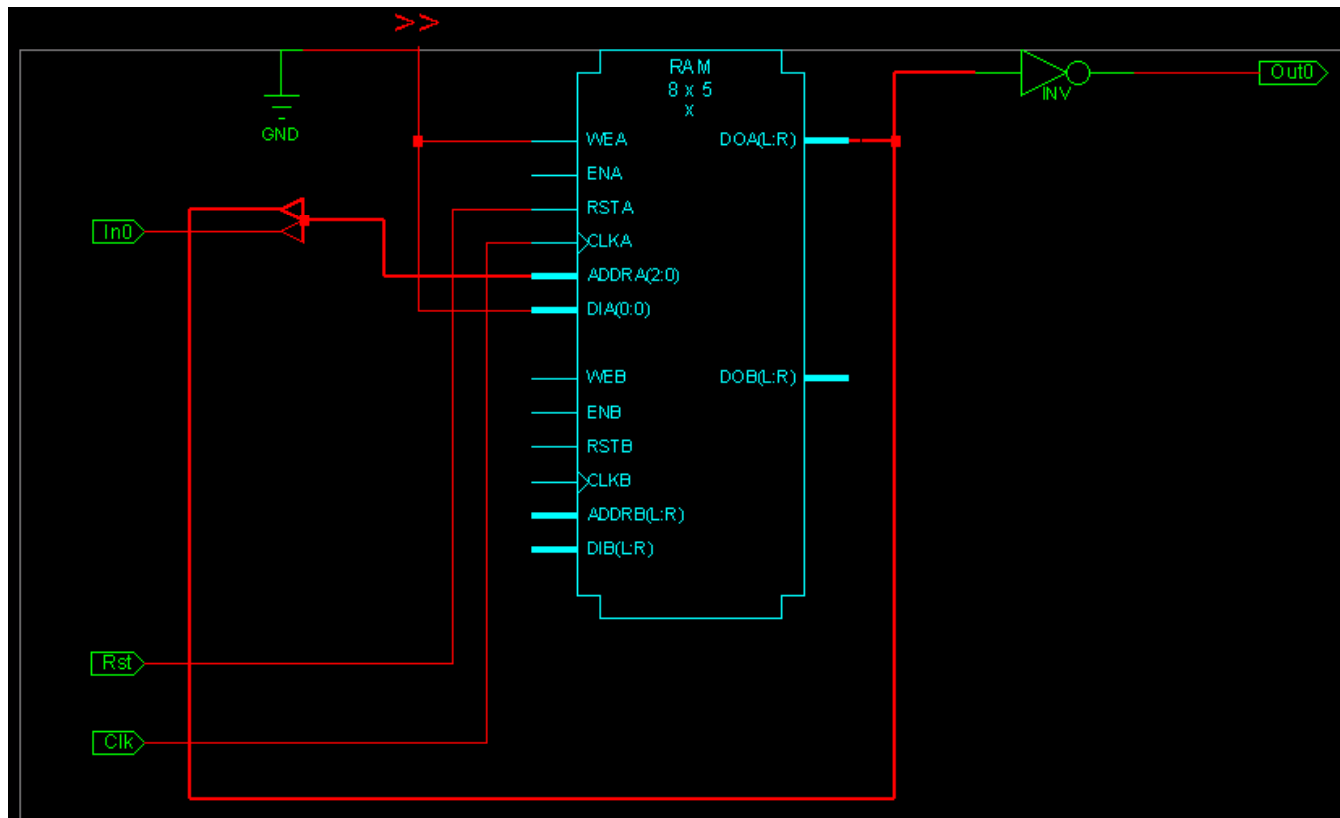- ❑ In FPGA, on-chip synchronous BRAM can be used for next-state logic and state register
- ❑ Selected as a synthesis option; default is LUT-based FSM



Mixing Datapath and FSM


□ Example - Greatest Common Divisor

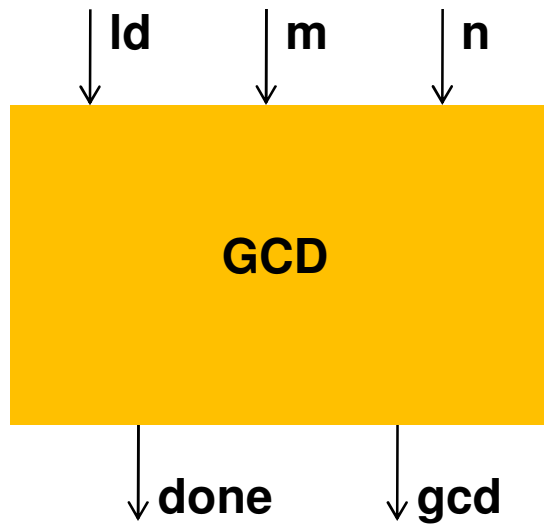

```
GCD: while (m != n) {  
    if (m > n)  
        m = m - n;  
    else  
        n = n - m;  
}  
output = m;
```


Mixing Datapath and FSM

Example - Greatest Common Divisor

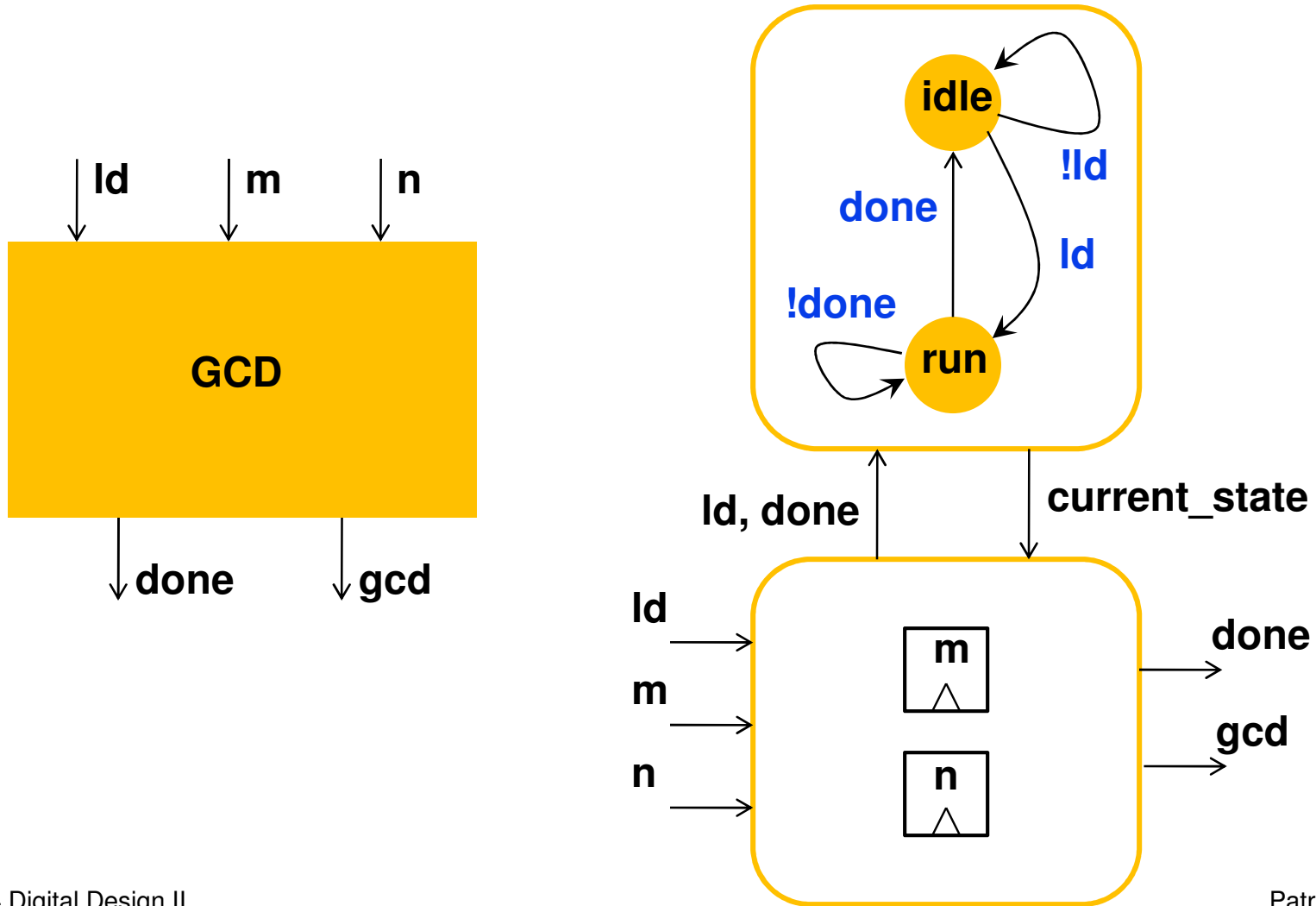


Mixing Datapath and FSM

- Example - Greatest Common Divisor

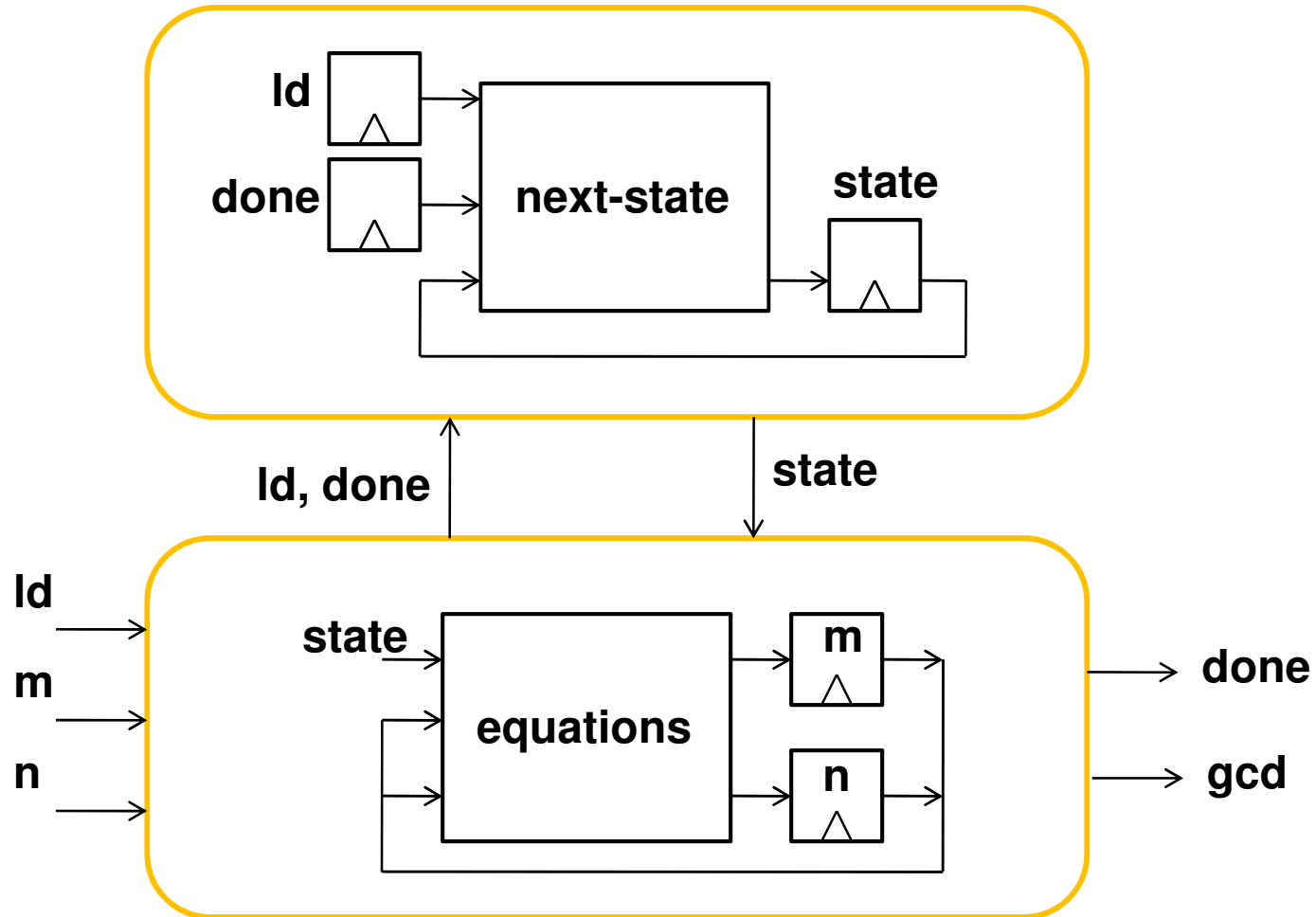

GCD I/O and State
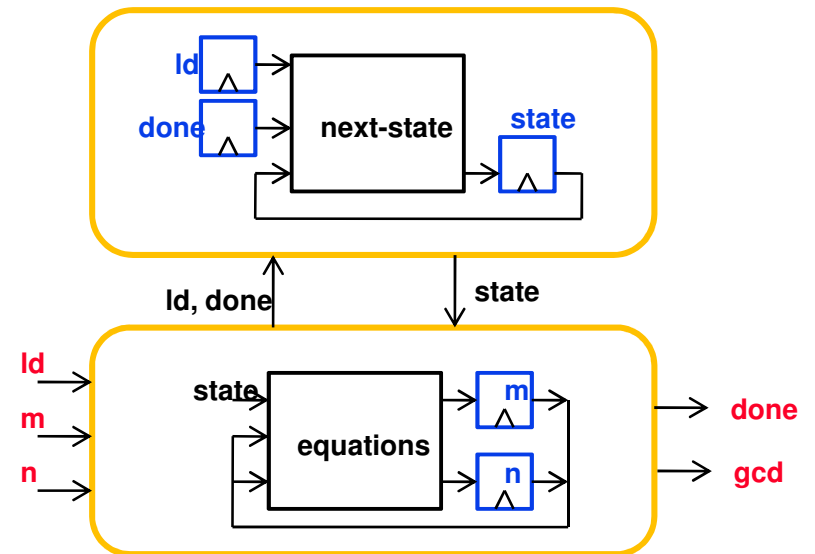
```
module gcd(q, done, m, n, ld, clk, rst);  
    output [9:0] q;  
    reg [9:0] q;  
    output done;  
    reg done;  
    input [9:0] m, n;  
    input ld;  
    input clk;  
    input rst;  
  
    reg state;  
    reg [9:0] reg_m, reg_n;  
    reg reg_ld;  
    parameter swait = 1'b0, srun = 1'b1;
```



GCD Single-case statement design

```
module gcd(q, done, m, n, ld, clk, rst);
...
always @(posedge clk) begin

    state <= swait; // default reg assignment (essential for control-related
    reg_ld <= ld; // state, optional for datapath-related state)
    done <= 1'b0;

    case (state)

        swait: begin
            if (reg_ld)
                state <= srun;
            else
                state <= swait;
            reg_m <= m; // read new input
            reg_n <= n;
            end

        srun: begin
            if (done)
                state <= swait;
            else
                state <= srun;
            reg_m <= (reg_m > reg_n) ? reg_m - reg_n : reg_m; // GCD iteration
            reg_n <= (reg_m > reg_n) ? reg_n : reg_n - reg_m;
            q <= reg_m;
            done <= (reg_m == reg_n);
            end
        endcase
    end
end
```

GCD Single-case statement design

```
module gcd(q, done, m, n, ld, clk, rst);
...
always @(posedge clk) begin

    state <= swait; // default reg assignment (essential for control-related
    reg_ld <= ld;   // state, optional for datapath-related state)
    done <= 1'b0;

    case (state)
```

```
swait: begin
    if (reg_ld)
        state <= srun;
    else
        state <= swait;
    reg_m <= m; // read new input
    reg_n <= n;
end
```

**Each state specifies
state transitions
+ datapath operations**

```
srun: begin
    if (done)
        state <= swait;
    else
        state <= srun;
    reg_m <= (reg_m > reg_n) ? reg_m - reg_n : reg_m; // GCD iteration
    reg_n <= (reg_m > reg_n) ? reg_n : reg_n - reg_m;
    q <= reg_m;
    done <= (reg_m == reg_n);
end
endcase
```

end

Synthesis


Advanced HDL Synthesis Report

Macro Statistics

```
# Adders/Subtractors           : 2
  10-bit subtractor            : 2
# Registers                     : 33
  Flip-Flops                   : 33
# Comparators                   : 2
  10-bit comparator equal      : 1
  10-bit comparator greater    : 1
```

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Flip Flops	22	9,312	1%	
Number of 4 input LUTs	78	9,312	1%	
Logic Distribution				
Number of occupied Slices	40	4,656	1%	
Number of Slices containing only related logic	40	40	100%	
Number of Slices containing unrelated logic	0	40	0%	
Total Number of 4 input LUTs	78	9,312	1%	
Number of bonded IOBs	33	92	35%	
IOB Flip Flops	11			
Number of GCLKs	1	24	4%	
Total equivalent gate count for design	948			
Additional JTAG gate count for IOBs	1,584			

GCD Single-case statement design

 

start
GCD(34, 8)

done
GCD = 2

Summary

❑ Finite State Machines

- Verilog Mapping: one, two, three always blocks

❑ State Encoding

- User-defined or tool-defined
- State encoding techniques: one-hot, user-defined, gray

❑ Synthesis Issues

- Default state assignment
- Safe Implementations
- Next-state logic: RAM or LUT

❑ FSM-based control of Datapath (gcd)