
ECE 4514

Digital Design II

Spring 2008

Lecture 16:

Synthesis of Memories

in FPGA

A Design Lecture

Patrick Schaumont


Overview

- ❑ Design flow for Datapath and Memory Elements
 - Inference and instantiation
 - Integrated synthesis and simulation

- ❑ Memory Elements
 - Register Files
 - Memory Arrays: SRAM and DRAM
 - Operation of SRAM and DRAM
 - SRAM in Spartan 3E FPGA
 - Configuration: single/dual port, read/write ordering
 - Inferring SRAM with Verilog
 - Initializing SRAM, \$readmemb and \$readmemh

- ❑ Overview of Project 4 & 5

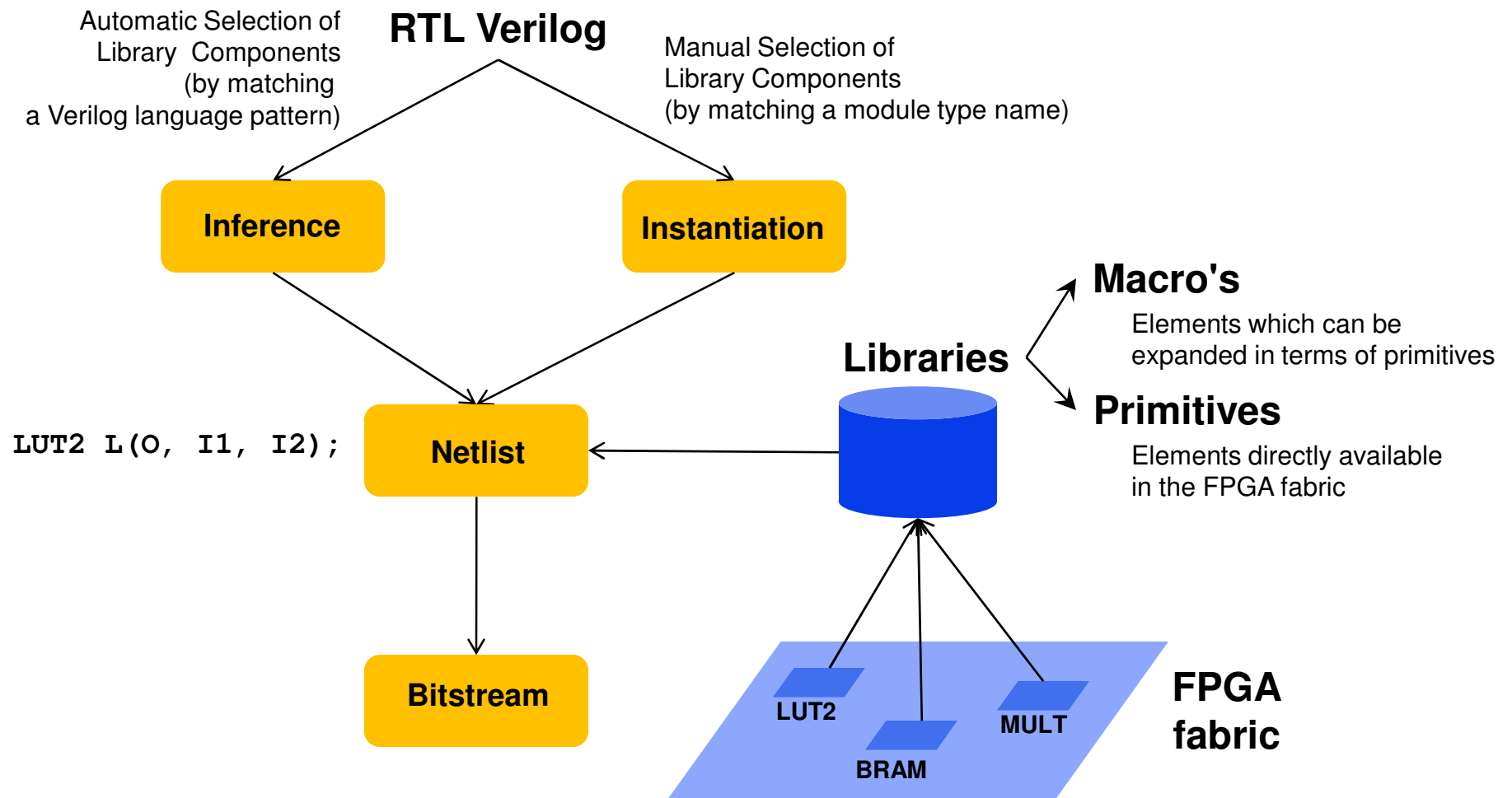
Design flow for datapath & memory elements



 Example 1 (primitive): Flip-flop

- This piece of code *infers* a flip-flop

```
module my_flipflop_i(q, c, d);  
    output q;  
    reg    q;  
    input  c;  
    input  d;  
  
    always @(posedge c)  
        q <= d;  
  
endmodule
```




This is a *primitive*
library element

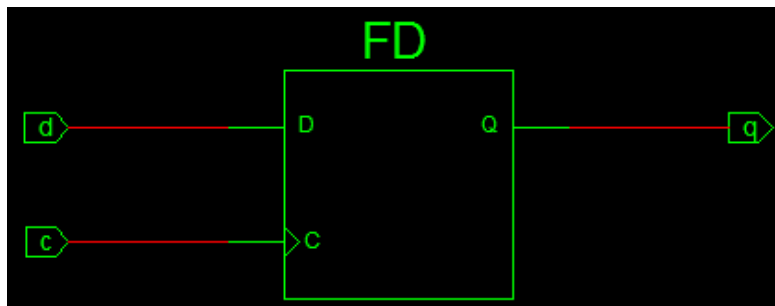Example 1 (primitive): Flip-flop

- This piece of code *instantiates* a flip-flop

```
module my_flipflop_1(q, c, d);  
    output q;  
    input  c;  
    input  d;  
  
    FD FD_instance (q, c, d);  
  
endmodule
```



This is a primitive
library element

How do we know what primitives are available?

□ "Xilinx FPGA Libraries Guide"


- lists all available primitive elements
- available parameters, availability over FPGA families, ...

FD

D Flip-Flop

Architectures Supported

FD	
Spartan-II, Spartan-IIE	Primitive
Spartan-3	Primitive
Virtex, Virtex-E	Primitive
Virtex-II, Virtex-II Pro, Virtex-II Pro X	Primitive
XC9500, XC9500XV, XC9500XL	Primitive
CoolRunner XPLA3	Primitive
CoolRunner-II	Primitive

 

FD is a single D-type flip-flop with data input (D) and data output (Q). The data on the D inputs is loaded into the flip-flop during the Low-to-High clock (C) transition.

The flip-flop is asynchronously cleared, output Low, when power is applied.

For XC9500/XV/XL, CoolRunner XPLA3, and CoolRunner-II, the power-on condition can be simulated by applying a High-level pulse on the PRLD global net.

Spartan-II, Spartan-IIE, Spartan-3, Virtex, Virtex-E, Virtex-II, Virtex-II Pro, and Virtex-II Pro X simulate power-on when global set/reset (GSR) is active.

How do we know what primitives are available?

□ "Xilinx FPGA Libraries Guide"

- FD entry shows how to instantiate it in Verilog or VHDL

Verilog Instantiation Template

```
FD FD_instance_name (.Q (user_Q),  
                    .C (user_C),  
                    .D (user_D));
```

```
defparam FD_instance_name.INIT = bit_value;
```

Commonly Used Constraints

BLKNM, HBLKNM, HU_SET, INIT, IOB, LOC, REG, RLOC, TIMEGRP, TNM, U_SET,
XBLKNM

Example 2 (macro): 4-bit adder

- This code infers a 4-bit adder

```
module a1(sum, co, a, b, ci);
    output [3:0] sum;
    reg [3:0] sum;
    output co;
    reg co;
    input [3:0] a, b;
    input ci;


    always @(a or b or ci)
    begin
        {co, sum} <= a + b + ci;
    end
endmodule
```


Example 2 (macro): 4-bit adder

- 4-bit adder synthesizes as a *macro* (not a primitive)

```
=====
Advanced HDL Synthesis Report

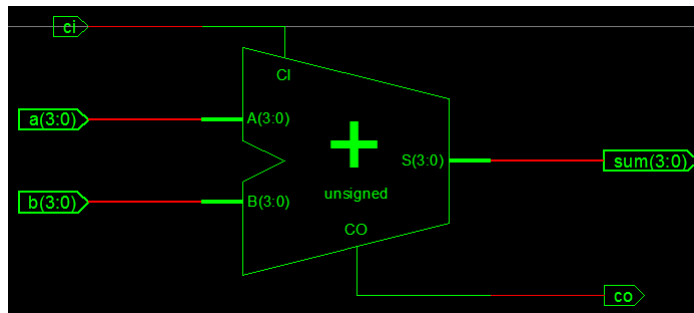Macro Statistics
# Adders/Subtractors                : 1
4-bit adder carry in/out            : 1
```



Since this is a *macro*, it will be expanded into FPGA primitives (LUTs, XORchain, registers,...)

Inference vs Instantiation

- ❑ Standard design practice (for any type of digital design: FPGA, ASIC) will *mix* inference and instantiation

- ❑ Inference:
 - Portable code which compiles on multiple targets
 - Portable code which simulates with generic simulator
 - Provides maximal freedom to synthesis tools

- ❑ Instantiation:
 - Nonportable code which makes specific assumption on target
 - Nonportable code which requires simulation library to simulate
 - Gives designer maximum control over synthesis process

Integrated Synthesis and Simulation


- ❑ Once we use design elements from a library, we need to add a simulation library specific to the target technology
 - Simulation library may provide a behavioral model of primitives and macro's, to implement the leaf cells of your design

- ❑ In addition, after synthesis, additional design details help to estimate precisely the delay incurred by each component and each net. This can also be included in the simulation.
 - Simulation library may provide detailed structural model of primitives, which are decorated with delay figures from tools.

- ❑ See lecture 20: Timing Analysis & Simulation

Memory Elements: Register Files

 
- ❑ Used when multiple registers are attached to single bus
- ❑ May be multi-ported and/or concurrent read/write



How to implement this ?

Memory Elements: Register Files

 
- Single write-port : load-enable edge-triggered reg



```
module r1(q, clk, enable, in);
  output [7:0] q;
  reg [7:0] q;
  input clk, enable;
  input [7:0] in;


  always @(posedge clk)
    if (enable)
      q <= in;

endmodule
```

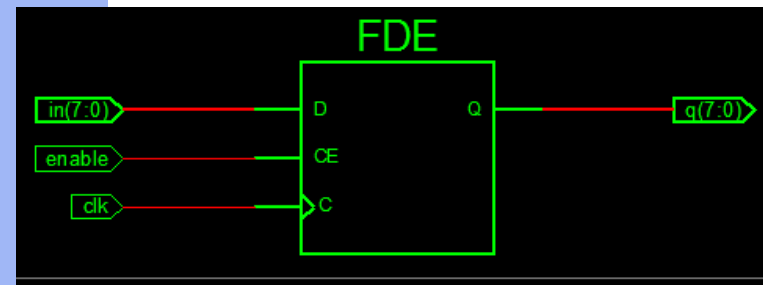


Memory Elements: Register Files

□ How to implement dual write-port ?

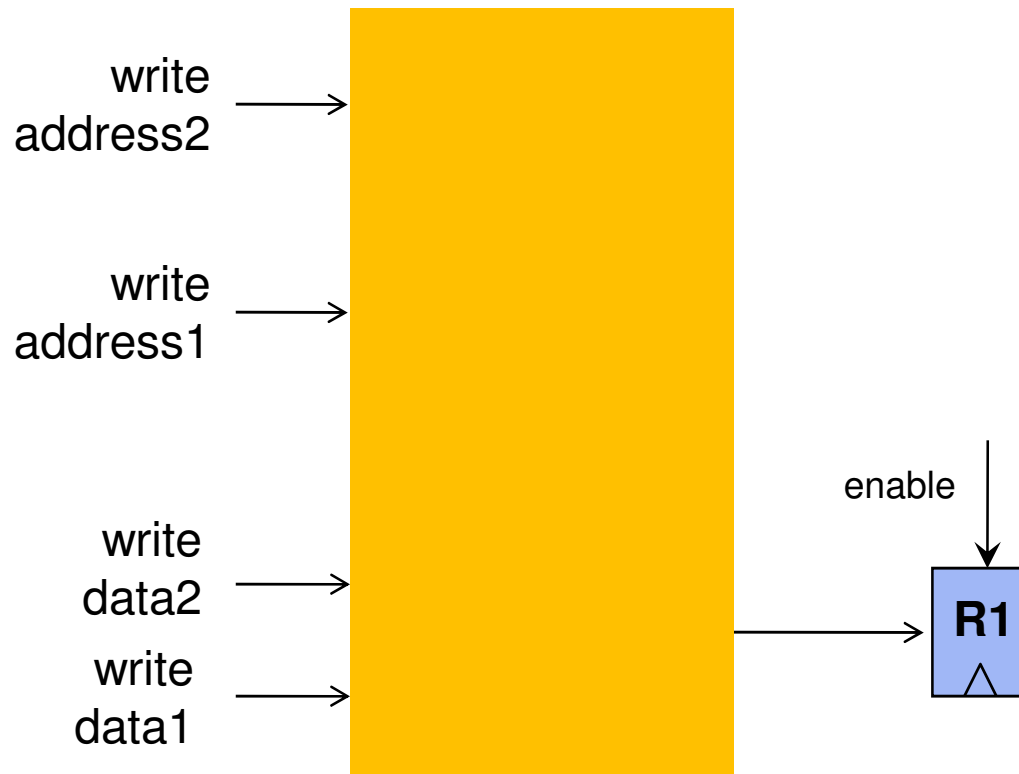

Memory Elements: Register Files

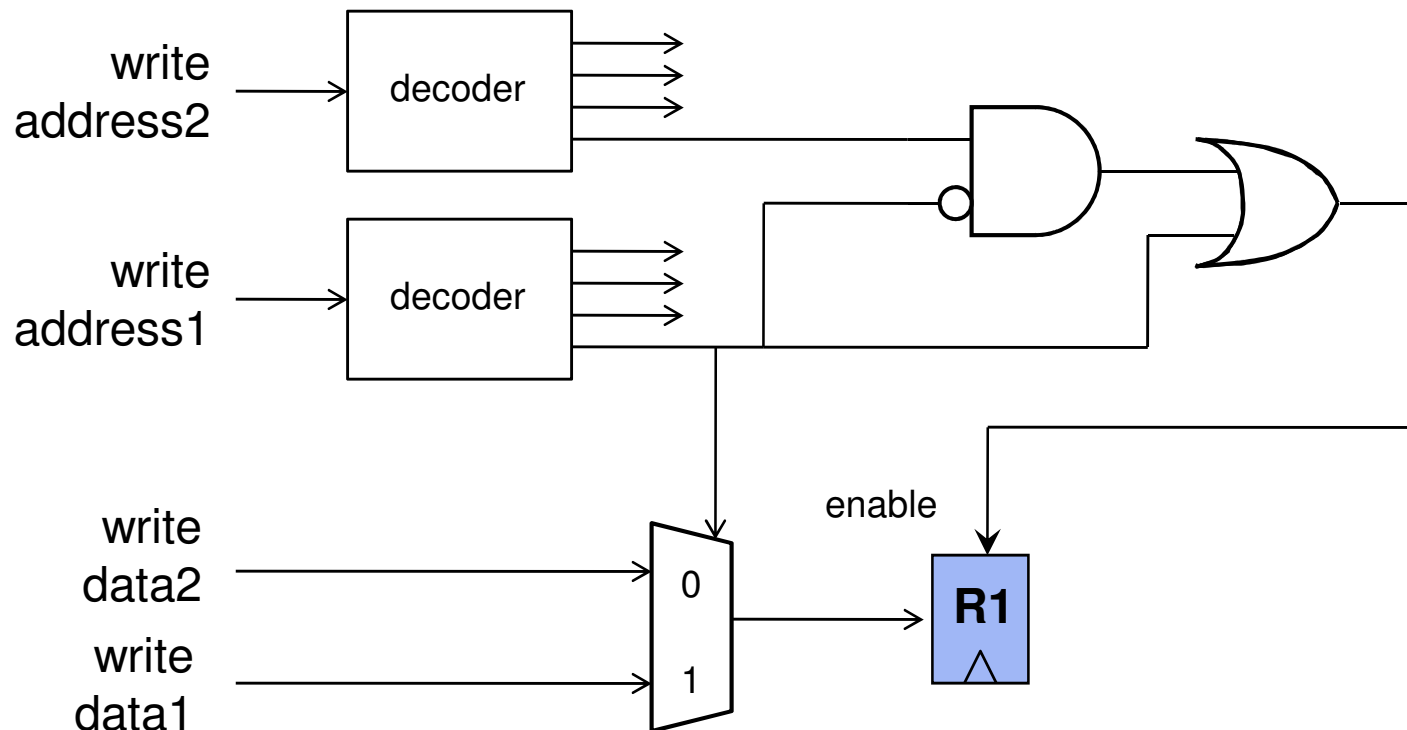
- Dual write-port : load-enable edge-triggered reg, mux and priority



What is the (most likely) critical path of this design ?

Memory Elements: Register Files

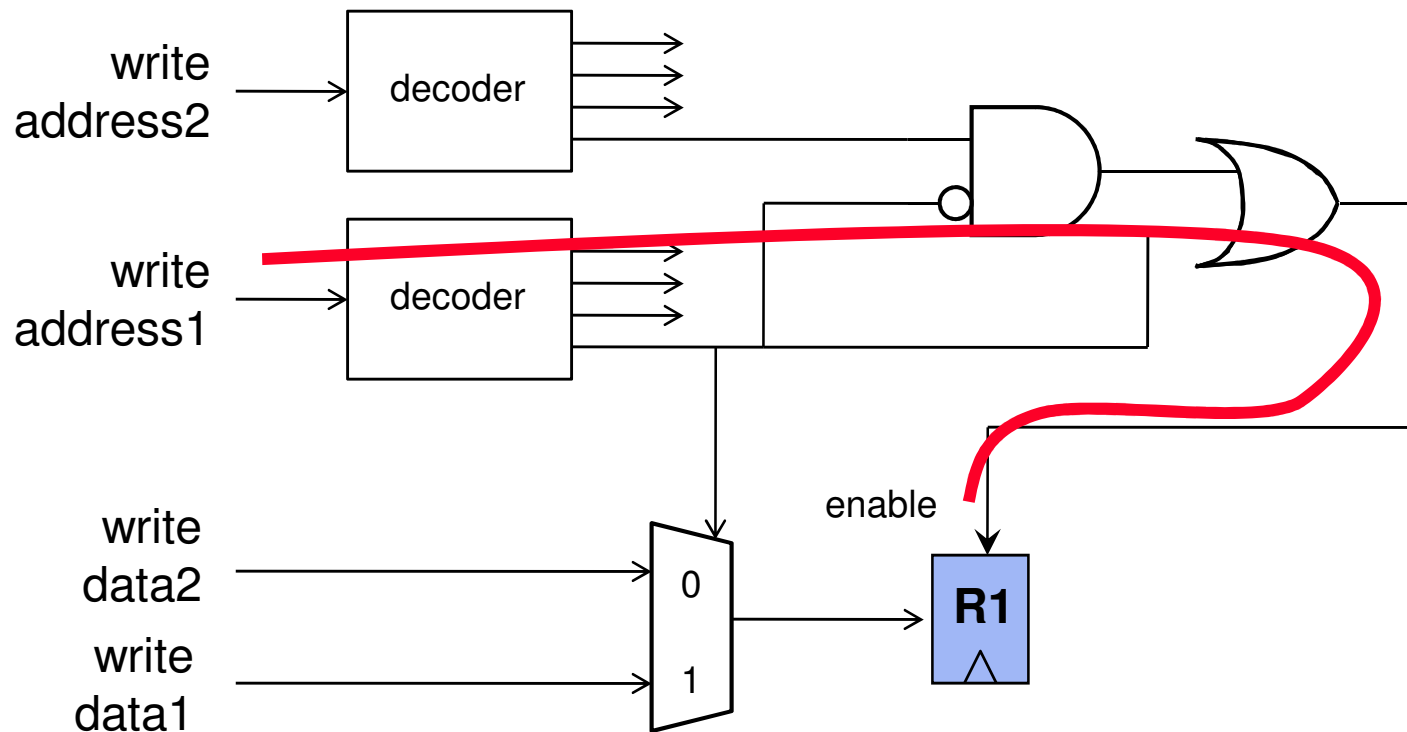- Dual write-port : load-enable edge-triggered reg, mux and priority




What is the (most likely) critical path of this design ?

Memory Arrays

- ❑ Flip-flop based on gates is area- and power-hungry
- ❑ More dense solutions arrange bit cells in an array
 - static random access memory (SRAM)
 - dynamic random access memory (DRAM)


D flip-flop

 

>20 transistors/bit


Basic SRAM Cell

[D. Harris]

 

6 transistors/bit



Basic DRAM Cell

 

1 transistor/bit


Generic SRAM Architecture

- m data bits per address, 2^n addresses

 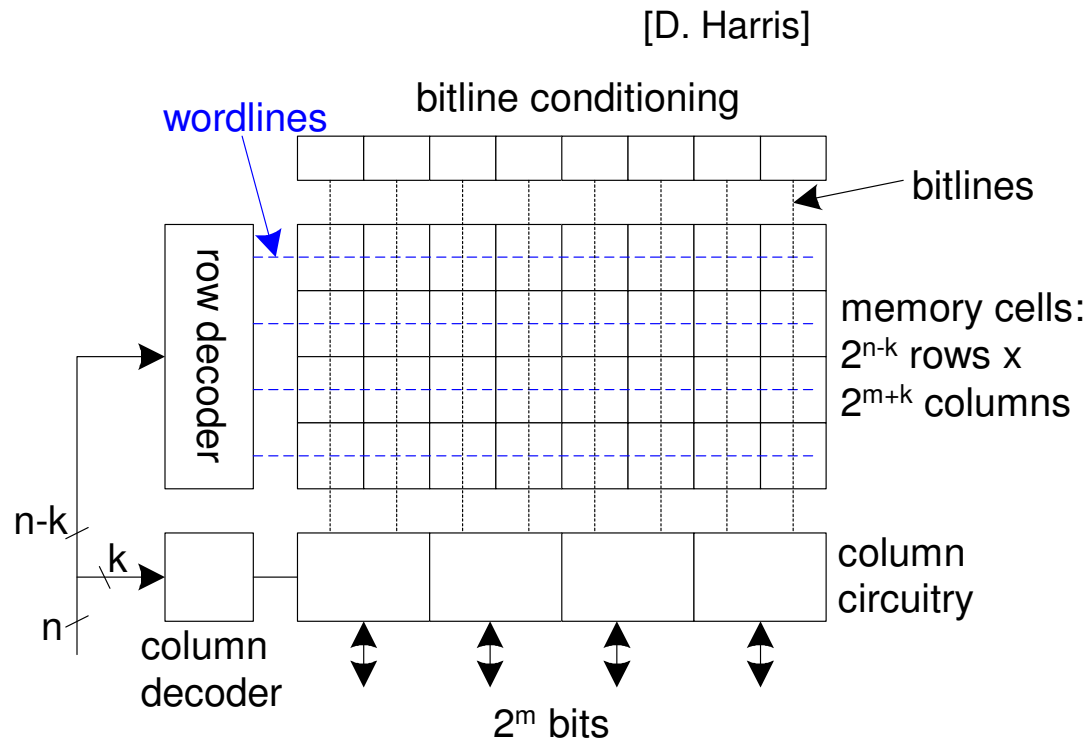



IBM Power4
(LSU, L2) Caches have regular SRAM structures, which are easy to spot

Dynamic RAM Architecture


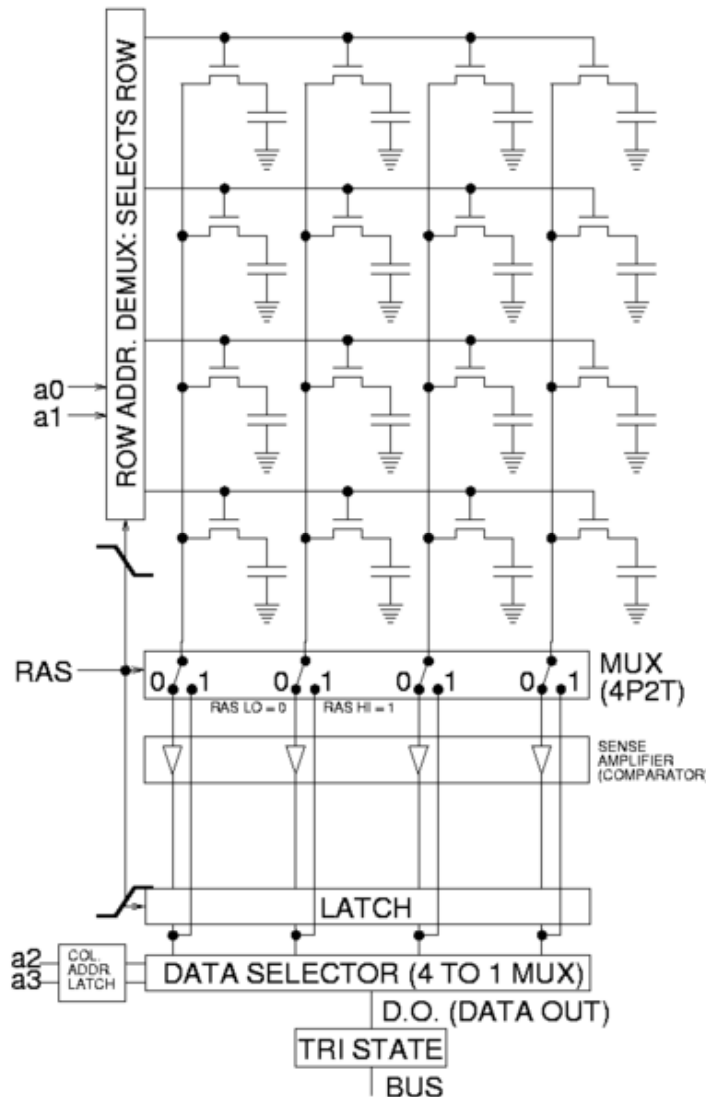


- ❑ One transistor/ capacitor per bit
- ❑ Multiplexed Address Bus
 - RAS = Row Address Select
 - CAS = Column Address Select
- ❑ Due to leakage current, capacitor discharges in a few ms
 - DRAM memory needs to be continuously rewritten. This process is called *refresh*
- ❑ Data is always read/written an *entire* row at a time

Dynamic RAM Architecture - Read

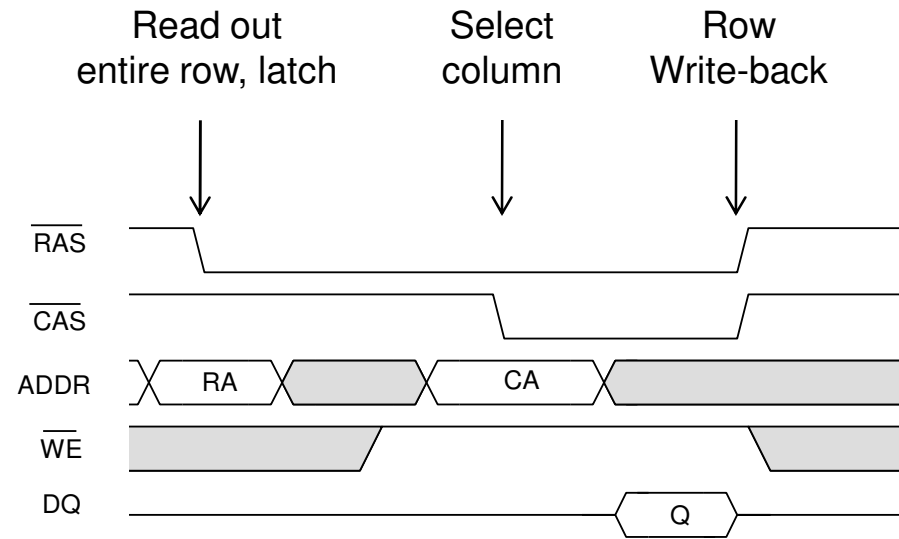 


Dynamic RAM Architecture - Write

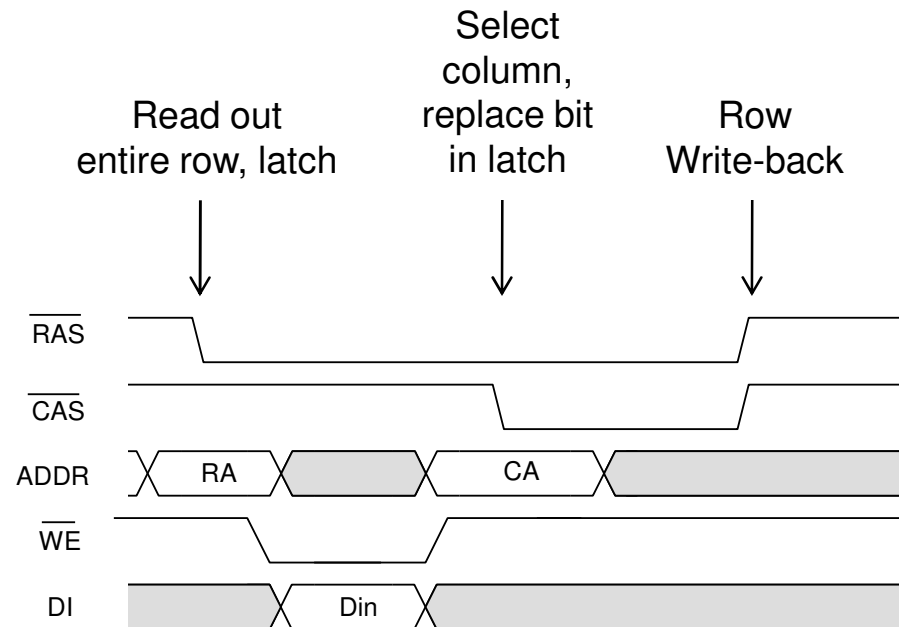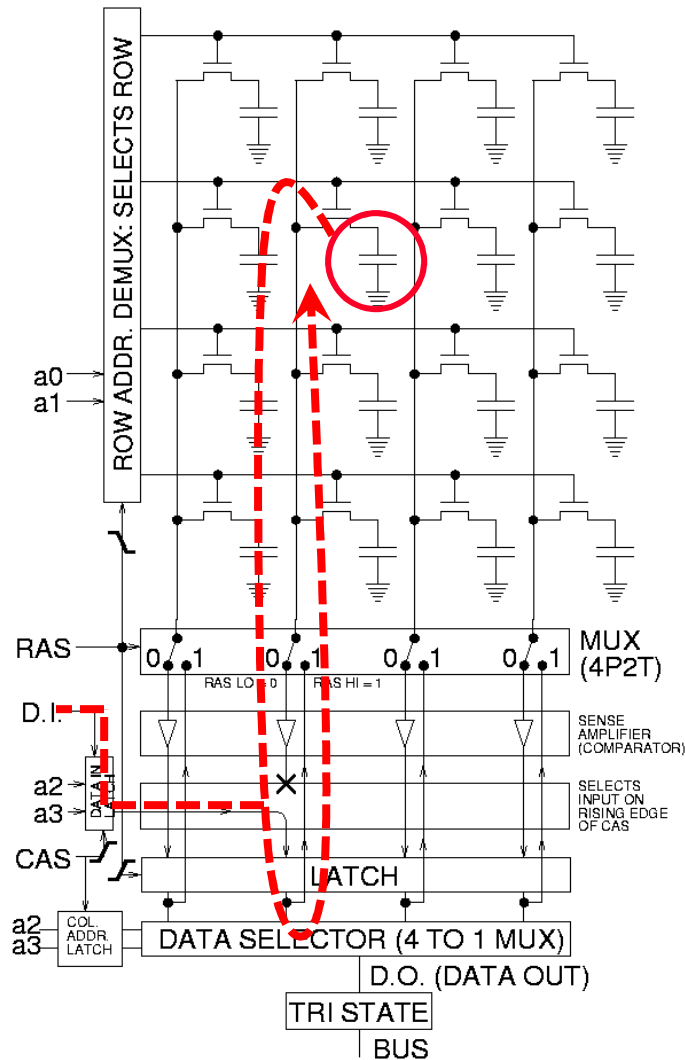


SRAM in FPGA

 - ❑ In Spartan 3ES500, 20 BlockRAM modules of 18Kbit each
- ❑ 18Kbit = (16 data + 2 parity) Kbit
- ❑ Single or Dual Port
 - a 'Port' contains a data-input port, a data-output port, an address bus, and a read/write command signal
- ❑ Reconfigurable to multiple data/address combinations
 - 16K (address) x1 (data)
 - 8Kx2
 - 4Kx4
 - ...
 - 512x36




Single Port Configuration

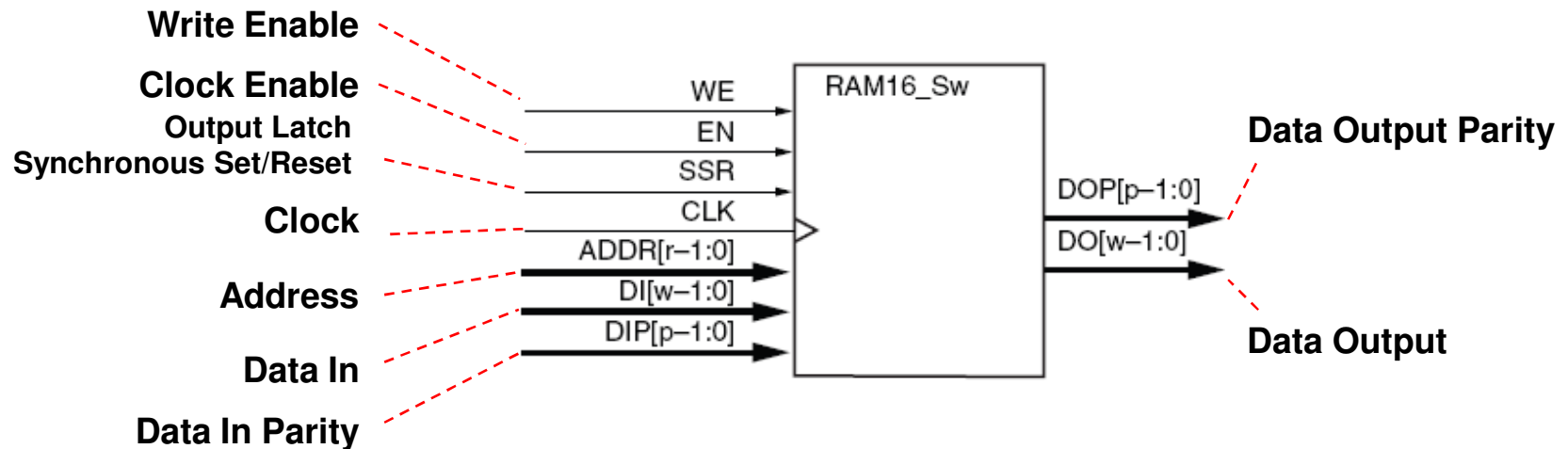

EN	WE	CLK	Function
0	X	X	Block RAM disabled. No operation.
1	0	↑	Block RAM enabled but no write operation.
1	1	↑	As appropriate for the block RAM data organization, write data from the DI and DIP input ports to the currently addressed RAM location.


Dual Port Configuration

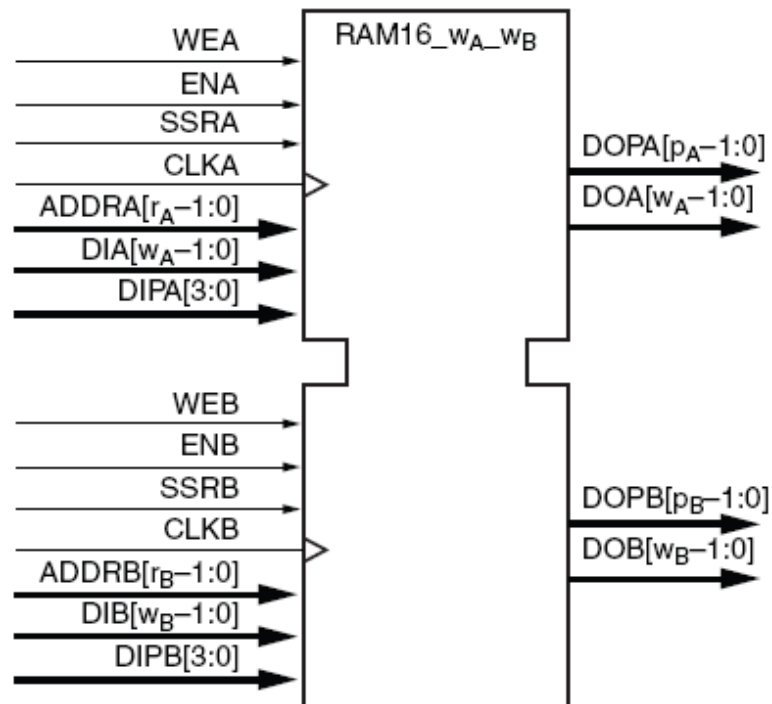- ❑ One memory array with dual write/read ports: supports two writes, two reads per clock cycle
- ❑ Dual port does not offer priority resolution
 - After write collision, memory location becomes undefined
- ❑ Each port can be configured separately to desired (Adr x Data) width



Read/write ordering on BlockRAM

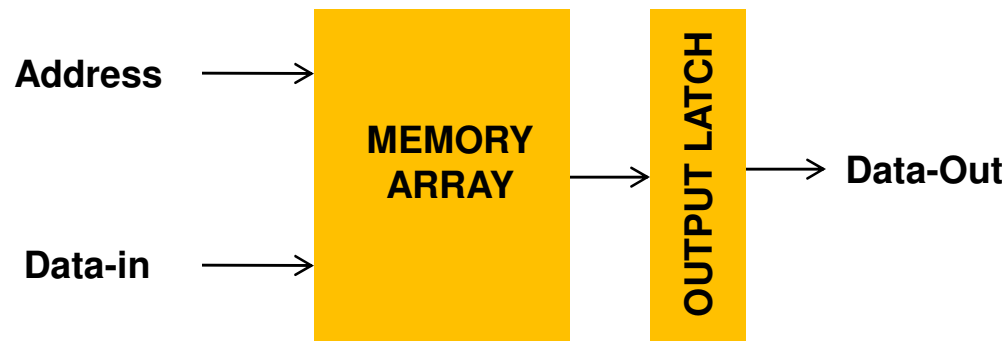- ❑ If we *write* data, what data appears on the *data-output port*?
- ❑ Three write modes: WRITE_FIRST, READ_FIRST, NO_CHANGE
 - WRITE_FIRST: `Data-out = Data-in; Mem[Addr] = Data-in`
 - READ_FIRST: `Data-out = Mem[Addr]; Mem[Addr] = Data-in`
 - NO_CHANGE: `Mem[Addr] = Data-in`



Inferring RAM in Verilog

```
module v_rams_01 (clk, en, we, addr, di, do);
    input  clk;
    input  we;
    input  en;
    input  [5:0] addr;
    input  [15:0] di;
    output [15:0] do;
    reg    [15:0] RAM [63:0]; // 16-bit, 64 locations
    reg    [15:0] do;

    always @(posedge clk)
    begin
        if (en)
        begin
            if (we)
                RAM[addr] <= di;
            do <= RAM[addr];
        end
    end

endmodule
```

← **Read First Mode
(non-blocking assignment)**

Always verify the feedback from the tools

□ Verify your assumptions

```
=====
*                               Advanced HDL Synthesis                               *
=====

Loading device for application Rf_Device from file '5vlx30.nph' in environment
C:\Xilinx91i.
INFO:Xst:2691 - Unit <v_rams_01> : The RAM <Mram_RAM> will be implemented as a BLOCK
RAM, absorbing the following register(s): <do>.
```

ram_type	Block		

Port A			
aspect ratio	64-word x 16-bit		
mode	read-first		
clkA	connected to signal <clk>	rise	
enA	connected to signal <en>	high	
weA	connected to signal <we>	high	
addrA	connected to signal <addr>		
diA	connected to signal <di>		
doA	connected to signal <do>		

```
=====
Advanced HDL Synthesis Report
```



Macro Statistics

```
# RAMs : 1
64x16-bit single-port block RAM : 1
```

Inferring RAM in Verilog

```
module v_rams_01 (clk, en, we, addr, di, do);  
    input  clk;  
    input  we;  
    input  en;  
    input  [10:0] addr;  
    input  [15:0] di;  
    output [15:0] do;  
    reg    [15:0] RAM [2047:0]; // 16-bit, 2048 locations  
    reg    [15:0] do;  
  
    always @(posedge clk)  
    begin  
        if (en)  
        begin  
            if (we)  
                RAM[addr] <= di;  
            do <= RAM[addr];  
        end  
    end  
  
endmodule
```

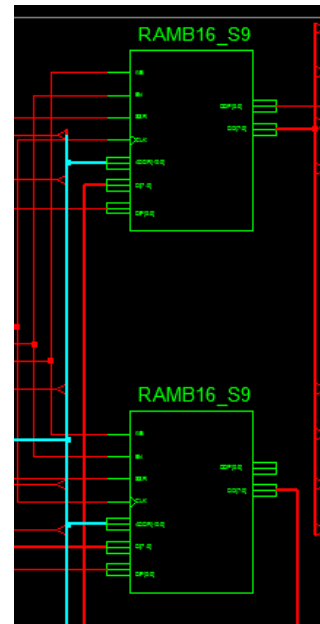 
When a single BlockRAM is too small, tools will allocate multiple BlockRAM



Inferring RAM in Verilog

```
module v_rams_01 (clk, en, we, addr, di, do);
    input  clk;
    input  we;
    input  en;
    input  [5:0] addr;
    input  [15:0] di;
    output [15:0] do;
    reg    [15:0] RAM [63:0]; // 16-bit, 64 locations
    reg    [15:0] do;

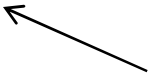    always @(posedge clk)
    begin
        if (en)
        begin
            if (we)
                RAM[addr] <= di;
            do <= di;
        end
    end
endmodule
```



Write First Mode

Always verify the feedback from the tools

□ Verify your assumptions

```
=====
*                               Advanced HDL Synthesis                               *
=====

Loading device for application Rf_Device from file '3s500e.nph' in environment
C:\Xilinx91i.
INFO:Xst:2691 - Unit <v_rams_02a> : The RAM <Mram_RAM> will be implemented as a BLOCK
RAM, absorbing the following register(s): <do>.

-----
| ram_type          | Block          |           |
-----
| Port A
|   aspect ratio   | 64-word x 16-bit |           |
|   mode           | write-first    |           |
|   clkA           | connected to signal <clk> | rise |
|   enA            | connected to signal <en> | high |
|   weA            | connected to signal <we> | high |
|   addrA          | connected to signal <addr> |           |
|   diA            | connected to signal <di> |           |
|   doA            | connected to signal <do> |           |
-----
```

Verify your assumptions - typical mistake

```
module v_rams_01 (clk, en, we, addr, di, do);
    input  clk;
    input  we;
    input  en;
    input  [5:0] addr;
    input  [15:0] di;
    output [15:0] do;
    reg    [15:0] RAM [127:0]; // 16-bit, 128 locations
    reg    [15:0] do;

    always @(posedge clk)
    begin
        if (en)
        begin
            if (we)
                RAM[addr] <= di;
            do <= di;
        end
    end

endmodule
```

**What is the problem with
this code ?**

Verify your assumptions - typical mistake

```
module v_rams_01 (clk, en, we, addr, di, do);
    input  clk;
    input  we;
    input  en;
    input  [5:0] addr;
    input  [15:0] di;
    output [15:0] do;
    reg    [15:0] RAM [127:0]; // 16-bit, 128 locations
    reg    [15:0] do;

    always @(posedge clk)
    begin
        if (en)
        begin
            if (we)
                RAM[addr] <= di;
            do <= di;
        end
    end

endmodule
```

**What is the problem with
this code ?**

**128 locations, but only
6 address bits**

Always verify the feedback from the tools

- Warnings *may* (not: *will*) suggest cause

```
=====
*                               HDL Analysis                               *
=====
Analyzing top module <v_rams_02a>.
INFO:Xst:1607 - Contents of array <RAM> may be accessed with an index that
does not cover the full array size.
INFO:Xst:1607 - Contents of array <RAM> may be accessed with an index that
does not cover the full array size.
Module <v_rams_02a> is correct for synthesis.

. . .
```

ram_type	Block		
Port A			
aspect ratio	64-word x 16-bit		
mode	write-first		
clkA	connected to signal <clk>	rise	
enA	connected to signal <en>	high	
weA	connected to signal <we>	high	
addrA	connected to signal <addr>		
diA	connected to signal <di>		
doA	connected to signal <do>		

RAM with asynchronous read port

```
module v_rams_04 (clk, we, a, di, do);  
  
    input  clk;  
    input  we;  
    input  [5:0] a;  
    input  [15:0] di;  
    output [15:0] do;  
    reg    [15:0] ram [63:0];  
  
    always @(posedge clk) begin  
        if (we)  
            ram[a] <= di;  
    end  
  
    assign do = ram[a]; ← Asynchronous Read  
  
endmodule
```

What would the synthesis tools do?
Remember: BlockRAM is a synchronous module. Address is only captured on clock edge.

EN	WE	CLK	Function
0	X	X	Block RAM disabled. No operation.
1	0	↑	Block RAM enabled but no write operation.
1	1	↑	As appropriate for the block RAM data organization, write data from the DI and DIP input ports to the currently addressed RAM location.

Asynchronous read not possible on BRAM

```
=====
*                               Advanced HDL Synthesis                               *
=====
```

```
Loading device for application Rf_Device from file '3s500e.nph' in
environment C:\Xilinx91i.
INFO:Xst:2664 - HDL ADVISOR - Unit <v_rams_04> : The RAM <Mram_ram> will be
implemented on LUTs either because you have described an asynchronous read
or because of currently unsupported block RAM features. If you have
described an asynchronous read, making it synchronous would allow you to
take advantage of available block RAM resources, for optimized device usage
and improved timings. Please refer to your documentation for coding
guidelines.
```

```
-----
| ram_type          | Distributed          |          |
-----
| Port A           |                      |          |
|   aspect ratio   | 64-word x 16-bit    |          |
|   clkA           | connected to signal <clk> | rise    |
|   weA            | connected to signal <we>  | high    |
|   addrA          | connected to signal <a>   |          |
|   diA            | connected to signal <di>  |          |
|   doA            | connected to signal <do>  |          |
-----
```

64-word x 16-bit 'Distributed RAM' occupies 82 LUTs ...

Dual-port RAM

```
module v_rams_13 (clk, en, we, addra, addrb, di, doa, dob);  
    input  clk;  
    input  en;  
    input  we;  
    input  [5:0] addra;  
    input  [5:0] addrb;  
    input  [15:0] di;  
    output [15:0] doa;  
    output [15:0] dob;  
    reg    [15:0] ram [63:0];  
    reg    [5:0] read_addra;  
    reg    [5:0] read_addrb;  
  
    always @(posedge clk) begin  
        if (en)  
            begin  
                if (we)  
                    ram[addra] <= di;  
                    read_addra <= addra;  
                    read_addrb <= addrb;  
                end  
            end  
  
        assign doa = ram[read_addra];  
        assign dob = ram[read_addrb];  
    endmodule
```

1) One write-port, two read-ports
2) write-first mode

Synchronous Read
(because address is clocked)

Instantiating RAM Library Blocks

- ❑ Previous examples illustrate how a RAM can be *inferred*
- ❑ We can also *instantiate* a RAM as a library module
- ❑ The primitive BlockRAM modules in Spartan 3E S500 are of the form RAMB16_S n , where n is a number that selects the configuration

Component	Data Cells	
	Depth	Width
RAMB16_S1	16384	1
RAMB16_S2	8192	2
RAMB16_S4	4096	4
RAMB16_S9	2048	8
RAMB16_S18	1024	16
RAMB16_S36	512	32

Example Instantiation

Selects type (address/data configuration)



```
RAMB16_S9 RAMB16_S9_inst4 (  
    .DO(ram_data_out4),          // 8-bit Data Output  
    .DOP(parity4),  
    .ADDR(ram_address[10:0]),    // 11-bit Address Input  
    .CLK(clk),                  // Clock  
    .DI(out_port),              // 8-bit Data Input  
    .DIP (1'b0),  
    .EN(cs_ram4),               // RAM Enable Input  
    .SSR(1'b0),                 // Synchronous Set/Reset Input  
    .WE(write_to_ram)           ); // Write Enable Input
```

```
defparam RAMB16_S9_inst4.WRITE_MODE = "WRITE_FIRST";  
defparam RAMB16_S9_inst4.INIT0 = 256'h00000000000000000000000000000000\  
                                     00000000000000000000000000000000\  
                                     00000000000000000;
```

↑
Selects additional synthesis parameters: mode, initial values, ...

Templates and parameters are defined as part of the 'HDL Libraries Guide'

If you can infer RAM, don't bother instantiating a specific module

Initialized RAM

- ❑ An initialized RAM can be used as a lookup table or as a ROM
- ❑ In FPGA, bitstream specifies the initial contents of the BRAM
- ❑ In Verilog, we may specify the initial contents of the RAM in different ways
 - using *initial* block (inference) or *synthesis constraints* (instantiation)
 - using \$readmemb or \$readmemh system calls
- ❑ The tools will then ensure that the RAM will be initialized to the specified state after configuration

Inferring Initialized RAM in Verilog

```
module v_rams_01 (clk, en, we, addr, di, do);
    input  clk;
    input  we;
    input  en;
    input  [5:0] addr;
    input  [15:0] di;
    output [15:0] do;
    reg    [15:0] RAM [63:0]; // 16-bit, 64 locations
    reg    [15:0] do;
    reg    [6:0] i;

    initial
        for (i=0; i<64; i++)
            RAM[i] = i;

    always @(posedge clk)
    begin
        if (en)
        begin
            if (we)
                RAM[addr] <= di;
            do <= RAM[addr];
        end
    end

endmodule
```


Result of Inferred Initialized RAM

The image displays the synthesis results for a BlockRAM library module. It includes a logic diagram, a detailed schematic of the RAM block, and two tables showing initialization attributes.

Properties of Instance Mram_RAM (Top Table)

Name	Value
INIT_00	000F000E000D000C000B000A0009000800070006000500040003000200010000
INIT_01	001F001E001D001C001B001A0019001800170016001500140013001200110010
INIT_02	002F002E002D002C002B002A0029002800270026002500240023002200210020
INIT_03	003F003E003D003C003B003A0039003800370036003500340033003200310030
InstName	Mram_RAM

Properties of Instance Mram_RAM (Bottom Table)

Name	Value
INIT_00	000F000E000D000C000B000A0009000800070006000500040003000200010000
INIT_01	001F001E001D001C001B001A0019001800170016001500140013001200110010
INIT_02	002F002E002D002C002B002A0029002800270026002500240023002200210020
INIT_03	003F003E003D003C003B003A0039003800370036003500340033003200310030
InstName	Mram_RAM
Type	ramb16_s18
WRITE_MODE	READ_FIRST


\$readmemh

```
module v_rams_01 (clk, en, we, addr, di, do);
    input  clk;
    input  we;
    input  en;
    input  [5:0] addr;
    input  [15:0] di;
    output [15:0] do;
    reg    [15:0] RAM [63:0];
    reg    [15:0] do;

    initial
        $readmemh("hex.data", RAM, 0, 63);

    always @(posedge clk)
    begin
        if (en)
            begin
                if (we)
                    RAM[addr] <= di;
                do <= RAM[addr];
            end
        end
    end

endmodule
```

 

Synthesis tools will read hex file to initialize memory

Similar command (\$readmemb) for binary radix

Summary

- ❑ Design flow for Dapath and Memory Elements
 - Inference vs Instantiation
 - Integrated synthesis and simulation

- ❑ Memory Elements
 - Register Files
 - Memory Arrays: SRAM and DRAM
 - Operation of SRAM and DRAM
 - SRAM in Spartan 3E FPGA
 - Configuration: single/dual port, read/write ordering
 - Infering SRAM with Verilog
 - Initializing SRAM, \$readmemb and \$readmemh