
ECE 4514

Digital Design II

Spring 2008

Lecture 17:

Hardware Division

A Design Lecture

Patrick Schaumont

Overview

- Division algorithms/architectures
 - Division as an 'inverted' multiplication
 - Division one digit at-a-time: digit-recurrence
 - The restoring divider algorithm
 - The non-restoring divider algorithm
 - Designing the non-restoring divider architecture

Before Division .. look at Multiplication First

- Binary multiplication using shift - and - add


$$\begin{array}{r} 15 \qquad \qquad \qquad 1 \ 1 \ 1 \ 1 \\ 12 \qquad \qquad \qquad 1 \ 1 \ 0 \ 0 \\ \qquad \qquad \times \qquad \qquad \qquad \hline \qquad \qquad \qquad \qquad \qquad 0 \ 0 \ 0 \ 0 \\ \qquad \qquad \qquad \qquad \qquad 0 \ 0 \ 0 \ 0 \\ \qquad \qquad \qquad \qquad 1 \ 1 \ 1 \ 1 \\ \qquad \qquad 1 \ 1 \ 1 \ 1 \\ \hline 180 \qquad 1 \ 0 \ 1 \ 1 \ 0 \ 1 \ 0 \ 0 \end{array}$$

Before Division .. look at Multiplication First

- ❑ Binary multiplication using shift - and - add
- ❑ $12 \times 15 =$
 - $0 \times 1 \times 15 +$
 - $0 \times 2 \times 15 +$
 - $1 \times 4 \times 15 +$
 - $1 \times 8 \times 15$
- ❑ In multiplication, we look at one bit of the multiplier at a time, and accumulate & shift the multiplicand


How does division work?

- more or less the opposite way ..

 

How does division work?

 - We subtract the shifter divider from the dividend ..



How does division work?

- We subtract the shifter divider from the dividend ..

divider
quotient




dividend

$$\begin{array}{r}
 \begin{array}{cccc}
 & & 1 & 1 & 1 & 1 \\
 & & \color{blue}{1} & 1 & 0 & 0 \\
 \times & & \hline
 & & 0 & 0 & 0 & 0 \\
 & 0 & 0 & 0 & 0 & & \\
 & 1 & 1 & 1 & 1 & & \\
 \color{red}{1} & \color{red}{1} & \color{red}{1} & \color{red}{1} & & & \\
 \hline
 1 & 0 & 1 & 1 & 0 & 1 & 0 & 0 \\
 \color{red}{1} & \color{red}{1} & \color{red}{1} & \color{red}{1} & & & & \\
 \hline
 0 & 0 & 1 & 1 & 1 & 1 & 0 & 0
 \end{array}
 \end{array}$$

How does division work?

- We subtract the shifter divider from the dividend ..

divider
quotient

 


dividend

$$\begin{array}{r}
 \begin{array}{cccc}
 & & & 1 & 1 & 1 & 1 \\
 & & & 1 & 1 & 0 & 0 \\
 \times & & & \hline
 & & & 0 & 0 & 0 & 0 \\
 & & 0 & 0 & 0 & 0 & \\
 & 1 & 1 & 1 & 1 & & \\
 & 1 & 1 & 1 & 1 & & \\
 \hline
 1 & 0 & 1 & 1 & 0 & 1 & 0 & 0 \\
 & 1 & 1 & 1 & 1 & & & \\
 \hline
 0 & 0 & 1 & 1 & 1 & 1 & 0 & 0 \\
 & & 1 & 1 & 1 & 1 & & \\
 \hline
 & & & 0 & 0 & 0 & 0 & 0
 \end{array}
 \end{array}$$

How does division work?

 - The problem is: in a real division, we don't know the quotient ..



How does division work?

- Example: Start at the MSB position

divider					1	1	1	1	
quotient					0	X	X	X	X
dividend	1	0	1	1	0	1	0	0	
	1	1	1	1					
									subtract
..111	1	1	0	0	0	1	0	0	

This is an 'overflow' (when considering this as an unsigned number).

This is a negative number (when considered as 2's complement).

This means that the q-bit for the MSB position must be 0.

How does division work?

- Example: let's try the MSB-1 position

divider				1	1	1	1	
quotient			0	1	X	X	X	
<hr style="border: 0.5px solid black;"/>								
dividend	1	0	1	1	0	1	0	0
		1	1	1	1			
<hr style="border: 0.5px solid black;"/>								
	0	0	1	1	1	1	0	0

subtract

**This is not an 'overflow':
the result is < then the dividend.**

**This means that the q-bit for the MSB-1
position must be 1.**

How does division work?

- Example: let's try the MSB-2 position

divider				1	1	1	1		
quotient				0	1	1	X	X	
<hr style="border: 0.5px solid black;"/>									
dividend	1	0	1	1	0	1	0	0	
		1	1	1	1				
<hr style="border: 0.5px solid black;"/>									
	0	0	1	1	1	1	0	0	subtract
			1	1	1	1			
<hr style="border: 0.5px solid black;"/>									
	0	0	0	0	0	0	0	0	subtract

This is 0 - we are done.

This means that the q-bit for the MSB-2 position must be 1, all other positions must be 0.

How does division work?

- Example: let's try the MSB-2 position

divider				1	1	1	1		
quotient				0	1	1	0	0	
<hr style="border: 0.5px solid black;"/>									
dividend	1	0	1	1	0	1	0	0	
		1	1	1	1				
<hr style="border: 0.5px solid black;"/>									
	0	0	1	1	1	1	0	0	subtract
			1	1	1	1			
<hr style="border: 0.5px solid black;"/>									
	0	0	0	0	0	0	0	0	subtract

This is 0 - we are done.

This means that the q-bit for the MSB-2 position must be 1, all other positions must be 0.

Dividend/Divider, Quotient, Remainder

□ Indeed

$$Y = D \times Q_n + R_n$$

1 0 1 1 0 1 0 0 = 1 1 1 1 X 0 1 0 0 0 + 0 0 1 1 1 1 0 0

180 = 15 X 8 + 60

Dividend/Divider, Quotient, Remainder

- For an n-bit Dividend Y, an n-bit Divider D, an n-bit Quotient Q, and a Remainder R we can write:

$$2^n \times Y = D \times Q + R$$

The lsb weight of Q and R
equals 1

The lsb weight of Q
equals 2^{-n}

i.e. the Q 'absorbs' the 2^n and
the lsb weight of Q needs
to decrease to keep the
expression balanced

Dividend/Divider, Quotient, Remainder

- For an n-bit Dividend Y, an n-bit Divider D, an n-bit Quotient Q, and a Remainder R we can write:

$$2^n \times Y = D \times Q + R$$

The lsb weight of Q and R equals 1

The lsb weight of Q equals 2^{-n}

Example: Find $8 / 15$ on 8 bits of precision for Q

$$Y = 8, D = 15$$
$$8 / 15 = 0.5333333...$$

$$Q = \text{int}(0.533333... \times 256) = 136$$
$$R = (8 \times 256 - 136 \times 15) = 8$$

Dividend/Divider, Quotient, Remainder

- For an n-bit Dividend Y, an n-bit Divider D, an n-bit Quotient Q, and a Remainder R we can write:

$$2^n \times Y = D \times Q + R$$

*Note that
 $0 < R < D$,
otherwise, Q would
be one higher.
Thus, R is at most n bit*

The lsb weight of Q and R
equals 1

The lsb weight of Q
equals 2^{-n}


Example: Find $8 / 15$ on 8 bits of precision for Q

$$Y = 8, D = 15$$
$$8 / 15 = 0.5333333...$$

$$Q = \text{int}(0.533333... \times 256) = 136$$
$$R = (8 \times 256 - 136 \times 15) = 8$$

Let's use this relationship for a 1-bit divider

- Assume that we are looking for a 1-bit quotient
- The 1-bit quotient q , remainder R , dividend Y and divider D are related as follows:
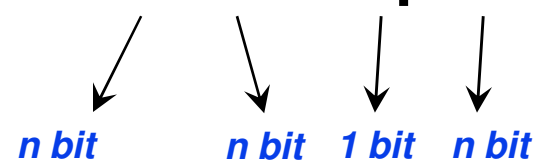
$$2 \times Y = D \times q + R$$


n bit *n bit* *1 bit* *n bit*

$q = \{0, 1\}$, corresponding to a real value of $\{0, 0.5\}$

1-bit divider: How do we choose q ?

- Since we don't know q nor R, we will just assume q is 1, and make a trial subtraction

$$2 \times Y - D = R$$

- If this relationship is correct, the subtraction should yield a positive result (since we want R to be positive). If we would work with unsigned numbers, the subtraction should not cause overflow.

$$2 \times Y - D \text{ must be } > 0$$

or

$$2 \times Y - D \text{ must not overflow}$$

1-bit divider

- After trial subtraction, if the relationship is true, then:

$$q = 1$$
$$R = 2 \times Y - D$$

- After trial subtraction, if this relationship is not true, then:

$$q = 0$$
$$R = 2 \times Y$$

Example: a 1-bit division of 4 (Y) by 6 (D):

$$2 \times 4 - 6 \times 1 = 2$$

This is > 0 , so $q = 1$ and $R = 2$

1-bit divider

- After trial subtraction, if the relationship is true, then:

$$q = 1$$
$$R = 2 \times Y - D$$

- After trial subtraction, if this relationship is not true, then:

$$q = 0$$
$$R = 2 \times Y$$

Example 2: a 1-bit division of 2 (Y) by 6 (D):

$$2 \times 2 - 6 \times 1 = -2, \text{ this is } < 0$$


In unsigned arithmetic, we would find $4 - 6 = \text{overflow}$

ECE 4514 Digital Design II
Lecture 17: Hardware Division

Thus $q = 0$ and $R = 4$

Extend to an n-bit divider

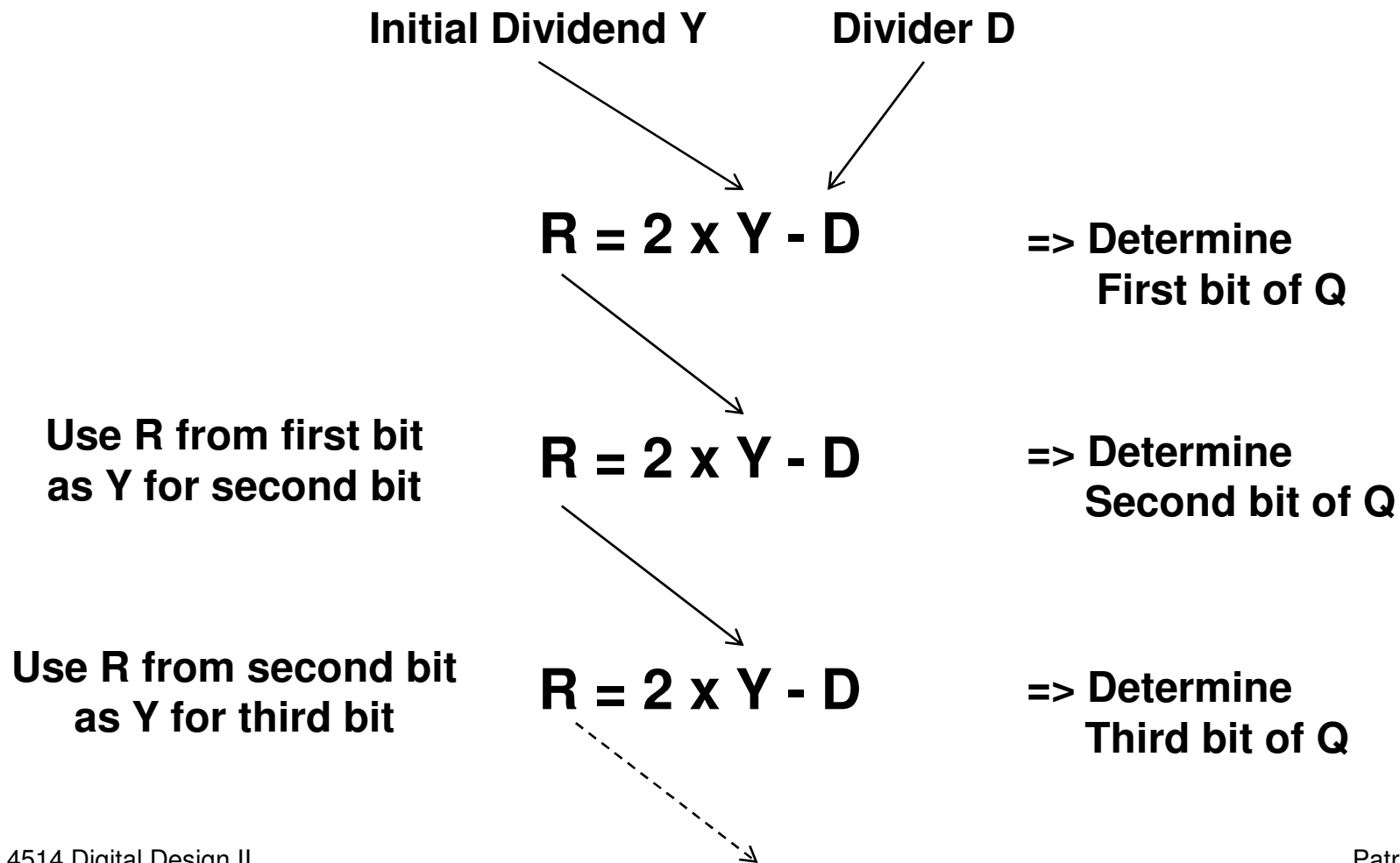- Use the 1-bit divider in a **digit-recurrence formula**



Example 2/7 on 4 bit precision ..

□ $Y = 2, D = 7$

$$2 \times 2 - 7 < 0$$

$$Q - \text{bit} = 0$$

$$2 \times 4 - 7 = 1$$

$$Q - \text{bit} = 1$$

$$2 \times 1 - 7 < 0$$

$$Q - \text{bit} = 0$$

$$2 \times 2 - 7 < 0$$

$$Q - \text{bit} = 0$$

$$R = 4$$

So

$$2^4 \times \overset{Y}{2} = \overset{D}{7} \times \overset{Q}{4} + \overset{R}{4}$$

$$32 = 28 + 4$$

Example 2/7 on 4 bit precision ..

□ $Y = 2, D = 7$

So

$$2^4 \times \overset{Y}{2} = \overset{D}{7} \times \overset{Q}{4} + \overset{R}{4}$$

The real Q (unscaled) would be: $4 / 2^4$

Indeed, $2/7 = 0.2857 \sim 0.25$

Example 23/45 on 4 bit precision ..

□ $Y = 23, D = 45$

$$2 \times 23 - 45 = 1$$

Q - bit = 1

$$2 \times 1 - 45 < 0$$

Q - bit = 0

$$2 \times 2 - 45 < 0$$

Q - bit = 0

$$2 \times 4 - 45 < 0$$

Q - bit = 0

R = 8

So

$$2^4 \times 23 = 45 \times 8 + 8$$

$$368 = 45 \times 8 + 8$$

Example 23/45 on 4 bit precision ..

□ $Y = 23, D = 45$

So

$$2^4 \times 23 = 45 \times 8 + 8$$

$$368 = 45 \times 8 + 8$$

The real Q (unscaled) would be: $8 / 2^4$

Indeed, $23/45 \sim 0.5$

Pseudocode for a *restoring* divider

- This pseudocode assumes sequential execution

input: X, Y , evaluate X/Y

output: $Q = \{q(1) \ q(2) \ q(3) \ \dots \ q(p)\}$
 R

$R = X$

for i in $1 \dots p$ **loop**

$tmp = 2 * R - Y;$

if ($tmp < 0$)

$q(i) = 0;$

$R = tmp + Y;$

else

$q(i) = 1;$

$R = tmp;$

- Each iteration does 1 bit
 $q(i)$ are each 1 bit
- The ' < 0 ' condition determines
if a q -bit is 0 or 1
- The name 'restoring' divider comes
from the fact that the loop 'restores'
the remainder after Y has been
subtracted when it shouldn't.

Pseudocode for a *restoring* divider

- This pseudocode assumes sequential execution

input: X, Y , evaluate X/Y

output: $Q = \{q(1) \ q(2) \ q(3) \ \dots \ q(p)\}$
 R

$R = X$

for i in $1 \dots p$ **loop**

tmp = $2 * R - Y;$

← trial subtraction

if ($tmp < 0$)

$q(i) = 0;$

R = $tmp + Y;$

← restore subtraction, since remainder becomes < 0

else

$q(i) = 1;$

R = $tmp;$

Pseudocode for a *restoring* divider

- This pseudocode assumes sequential execution

input: X, Y, evaluate X/Y
output: Q = {q(1) q(2) q(3) .. q(p)}
R

R = X

for i in 1 .. p **loop**

tmp = 2 * R - Y;

if (tmp < 0)

 q(i) = 0;

 R = tmp + Y;

else

 q(i) = 1;

 R = tmp;

As a further optimization,
we will rewrite
the code to overlap
the execution of this
expression with
the execution of the
if-then-else statement

This will result in the
NON-RESTORING DIVIDER

Pseudocode for a *non-restoring* divider

□ This pseudocode assumes sequential execution

input: X, Y , evaluate X/Y
output: $Q = \{q(1) \ q(2) \ q(3) \ \dots \ q(p)\}$
 R

$R = 2 * X - Y;$ ← Does already the first iteration

for i in $1 \dots p-1$ **loop**

if $(R < 0)$

$q(i) = 0;$

$R = 2 * R + Y;$ ← Restore, and prepare for the next iteration

$2 * (R + X) - X$

else

$q(i) = 1;$

$R = 2 * R - Y;$ ← Continue to the next iteration

if $(R < 0)$ ← Make sure remainder is positive

$q(p) = 0; R = R + Y;$

else

$q(p) = 1;$

Pseudocode for a *non-restoring* divider

input: X, Y, evaluate X/Y
output: Q = {q(1) q(2) q(3) .. q(p)}
R

```
R = 2 * X - Y;  
for i in 1 .. p-1 loop  
  if (R < 0)  
    q(i) = 0;  
    R = 2 * R + Y;  
  else  
    q(i) = 1;  
    R = 2 * R - Y;  
  
if (R < 0)  
  q(p) = 0; R = R + Y;  
else  
  q(p) = 1;
```

- ❑ This code is 90% equivalent to the project-3 assignment
- ❑ The algorithm used for project 3 had extra features:
 - No initial expression before the loop
 - Support for signed numbers X, Y
- ❑ For now, we stick to the algorithm shown on the left

How to map this into Verilog ?

input: X, Y, evaluate X/Y
output: Q = {q(1) q(2) q(3) .. q(p)}
R

```
R = 2 * X - Y;  
for i in 1 .. p-1 loop  
    if (R < 0)  
        q(i) = 0;  
        R = 2 * R + Y;  
    else  
        q(i) = 1;  
        R = 2 * R - Y;  
  
if (R < 0)  
    q(p) = 0; R = R + Y;  
else  
    q(p) = 1;
```

- ❑ Decide on Module Interface
- ❑ Decide on Schedule
(how to map into clock cycles)
- ❑ Choose a precision

How to map this into Verilog ?

input: X, Y, evaluate X/Y
output: Q = {q(1) q(2) q(3) .. q(p)}
R

```
R = 2 * X - Y;  
for i in 1 .. p-1 loop  
    if (R < 0)  
        q(i) = 0;  
        R = 2 * R + Y;  
    else  
        q(i) = 1;  
        R = 2 * R - Y;  
  
if (R < 0)  
    q(p) = 0; R = R + Y;  
else  
    q(p) = 1;
```

- ❑ **Decide on Module Interface**
Inputs: X, Y, start
Outputs: Z, R, done
- ❑ **Decide on Schedule**
(how to map into clock cycles)
One iteration of for-loop per clock cycle
- ❑ **Choose a precision**
X, Y, R: 16-bit
Z: 8-bit

How to map this into Verilog ?

input: X, Y, evaluate X/Y
output: Q = {q(1) q(2) q(3) .. q(p)}
R

```
R = 2 * X - Y;  
for i in 1 .. p-1 loop  
    if (R < 0)  
        q(i) = 0;  
        R = 2 * R + Y;  
    else  
        q(i) = 1;  
        R = 2 * R - Y;  
  
if (R < 0)  
    q(p) = 0; R = R + Y;  
else  
    q(p) = 1;
```

□ Start by choosing registers

What registers do you need?
(Assume inputs are stable)

How to map this into Verilog ?

input: X, Y, evaluate X/Y
output: Q = {q(1) q(2) q(3) .. q(p)}
R

```
R = 2 * X - Y;  
for i in 1 .. p-1 loop  
    if (R < 0)  
        q(i) = 0;  
        R = 2 * R + Y;  
    else  
        q(i) = 1;  
        R = 2 * R - Y;  
  
if (R < 0)  
    q(p) = 0; R = R + Y;  
else  
    q(p) = 1;
```

- Start by choosing registers

What registers do you need?
(Assume inputs are stable)

R is a 16-bit register
Q is an 8-bit register

+ additional control registers
(counters and flags)

Algorithm has three phases

input: X, Y , evaluate X/Y

output: $Q = \{q(1) \ q(2) \ q(3) \ \dots \ q(p)\}$
 R

```
R = 2 * X - Y;
```

Initialization (start=1)

```
for i in 1 .. p-1 loop
```

```
  if (R < 0)
```

```
    q(i) = 0;
```

```
    R    = 2 * R + Y;
```

```
  else
```

```
    q(i) = 1;
```

```
    R    = 2 * R - Y;
```

**Processing
in clock cycle 1 .. 7**

```
if (R < 0)
```

```
  q(p) = 0; R = R + Y;
```

```
else
```

```
  q(p) = 1;
```

**Wrap-up
clock cycle 8**

Assignments on reg in initialization

input: X, Y, evaluate X/Y

output: Q = {q(1) q(2) q(3) ...} **2 * X - Y** **0**
 R ↓ ↓

```
R = 2 * X - Y;
```

```
for i in 1 .. p-1 loop
```

```
  if (R < 0)
```

```
    q(i) = 0;
```

```
    R = 2 * R + Y;
```

```
  else
```

```
    q(i) = 1;
```

```
    R = 2 * R - Y;
```

```
if (R < 0)
```

```
  q(p) = 0; R = R + Y;
```

```
else
```

```
  q(p) = 1;
```

Assignments on reg during processing

input: X, Y , evaluate X/Y

output: $Q = \{q(1) \ q(2) \ q(3) \ \dots \ q(p)\}$
 R

```
R = 2 * X - Y;
```

```
for i in 1 .. p-1 loop
```

```
  if (R < 0)
```


```
    q(i) = 0;
```

```
    R = 2 * R + Y;
```

```
  else
```

```
    q(i) = 1;
```

```
    R = 2 * R - Y;
```

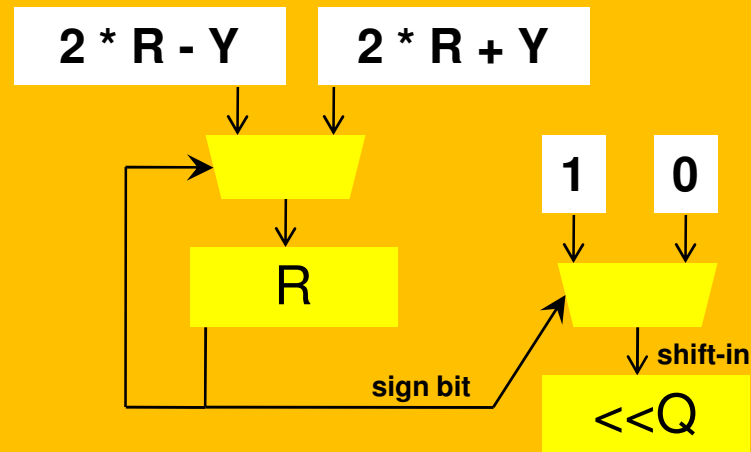

```
if (R < 0)
```

```
  q(p) = 0; R = R + Y;
```

```
else
```

```
  q(p) = 1;
```


Assignments on reg at wrap-up

input: X, Y , evaluate X/Y

output: $Q = \{q(1) \ q(2) \ q(3) \ \dots \ q(p)\}$
 R

```
R = 2 * X - Y;
```

```
for i in 1 .. p-1 loop
```

```
  if (R < 0)
```

```
    q(i) = 0;
```

```
    R = 2 * R + Y;
```

```
  else
```

```
    q(i) = 1;
```


```
    R = 2 * R - Y;
```

```
if (R < 0)
```

```
  q(p) = 0; R = R + Y;
```

```
else
```

```
  q(p) = 1;
```

 

Birds-eye view on module structure

input: X, Y , evaluate X/Y
output: $Q = \{q(1) \ q(2) \ q(3) \ \dots \ q(p)\}$
 R


```
R = 2 * X - Y;
```

```
for i in 1 .. p-1 loop  
  if (R < 0)  
    q(i) = 0;  
    R = 2 * R + Y;  
  else  
    q(i) = 1;  
    R = 2 * R - Y;
```

```
if (R < 0)  
  q(p) = 0; R = R + Y;  
else  
  q(p) = 1;
```

Datapath Design:

Old Q, R + Inputs X, Y

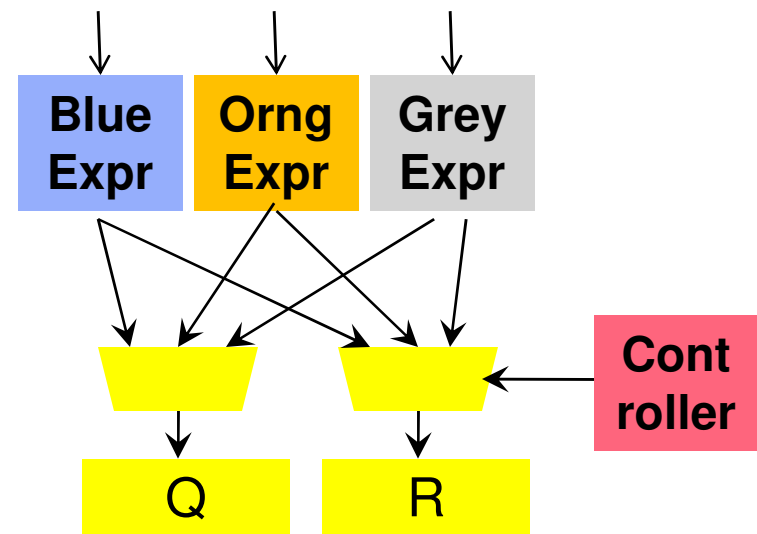

Verilog for R register assignments

input: X, Y, evaluate X/Y

output: Q = {q(1) q(2) q(3) .. q(p)}
R

```
R = 2 * X - Y; start
```

```
for i in 1 .. p-1 loop  
  if (R < 0)  
    q(i) = 0;  
    R = 2 * R + Y;  
  else  
    q(i) = 1;  
    R = 2 * R - Y;
```

```
if (R < 0) last  
  q(p) = 0; R = R + Y;  
else  
  q(p) = 1;
```

Assignments on R Register:

```
always @(posedge clk)  
  if (start)  
    R <= 2 * X - Y;  
  else if (~last & R[15])  
    R <= (R << 1) + Y;  
  else if (~last)  
    R <= (R << 1) - Y;  
  else if (last & R[15])  
    R <= R + Y;  
  else  
    R <= R;
```

Verilog for Q Register Assignments

input: X, Y, evaluate X/Y
output: Q = {q(1) q(2) q(3) .. q(p)}
R

```
R = 2 * X - Y; start
```

```
for i in 1 .. p-1 loop  
  if (R < 0)  
    q(i) = 0;  
    R = 2 * R + Y;  
  else  
    q(i) = 1;  
    R = 2 * R - Y;
```

```
if (R < 0) last  
  q(p) = 0; R = R + Y;  
else  
  q(p) = 1;
```

Assignments on Q Register:

```
always @(posedge clk)  
  if (start)  
    Q <= 0;  
  else if (~last)  
    Q <= R[15] ?  
      {Q[6:0], 1'b0} :  
      {Q[6:0], 1'b1};  
  else if (last & R[15])  
    Q <= {Q[6:0], 1'b0};  
  else if (last & ~R[15])  
    Q <= {Q[6:0], 1'b1};  
  else  
    Q <= Q;
```

Controller

input: X, Y, evaluate X/Y

output: Q = {q(1) q(2) q(3) .. q(p)}
R

```
R = 2 * X - Y;
```

Wait for Start Pulse

Reset Counter

```
for i in 1 .. p-1 loop
```

Start Pulse

```
  if (R < 0)
```

```
    q(i) = 0;
```

```
    R = 2 * R + Y;
```

Increment Counter

Counter =
0 .. 6

```
  else
```

```
    q(i) = 1;
```

```
    R = 2 * R - Y;
```

Last-flag

```
if (R < 0)
```

```
  q(p) = 0; R = R + Y;
```

Increment Counter

Counter = 7

```
else
```

```
  q(p) = 1;
```

Done-flag

Verilog for controller

input: X, Y, evaluate X/Y
output: Q = {q(1) q(2) q(3) .. q(p)}
R

```
R = 2 * X - Y;
```

```
for i in 1 .. p-1 loop  
  if (R < 0)  
    q(i) = 0;  
    R = 2 * R + Y;  
  else  
    q(i) = 1;  
    R = 2 * R - Y;
```

```
if (R < 0)  
  q(p) = 0; R = R + Y;  
else  
  q(p) = 1;
```

Controller:

```
reg done;  
reg last;
```

```
always @(posedge clk) begin  
  done <= 0;  
  last <= 0;  
  if (start)  
    cnt <= 0;  
  else  
    cnt <= cnt + 1;  
  if (cnt == 6'd6)  
    last <= 1;  
  else if (cnt == 6'd7)  
    done <= 1;  
end
```

Entire Design

```
module divider(Z, R, done, X, Y, start, clk);
    output [7:0] Z;
    output [15:0] R;
    output done;
    input [15:0] X;
    input [15:0] Y;
    input start;
    input clk;

    reg [7:0] Q;
    reg [15:0] R;

    reg [5:0] cnt;
    reg done;
    reg last;

    always @(posedge clk) begin
        done <= 0;
        last <= 0;
        if (start)
            cnt <= 0;
        else
            cnt <= cnt + 1;
        if (cnt == 6'd6)
            last <= 1;
        else if (cnt == 6'd7)
            done <= 1;
    end

    always @(posedge clk)
        if (start)
            R <= 2 * X - Y;
        else if (~last & R[15])
            R <= (R << 1) + Y;
        else if (~last)
            R <= (R << 1) - Y;
        else if (last & R[15])
            R <= R + Y;
        else
            R <= R;


    always @(posedge clk)
        if (start)
            Q <= 0;
        else if (~last)
            Q <= R[15] ? {Q[6:0], 1'b0} :
                {Q[6:0], 1'b1};
        else if (last & R[15])
            Q <= {Q[6:0], 1'b0};
        else if (last & ~R[15])
            Q <= {Q[6:0], 1'b1};
        else
            Q <= Q;

    assign Z = Q;
endmodule
```

Simulation Output

start

stop

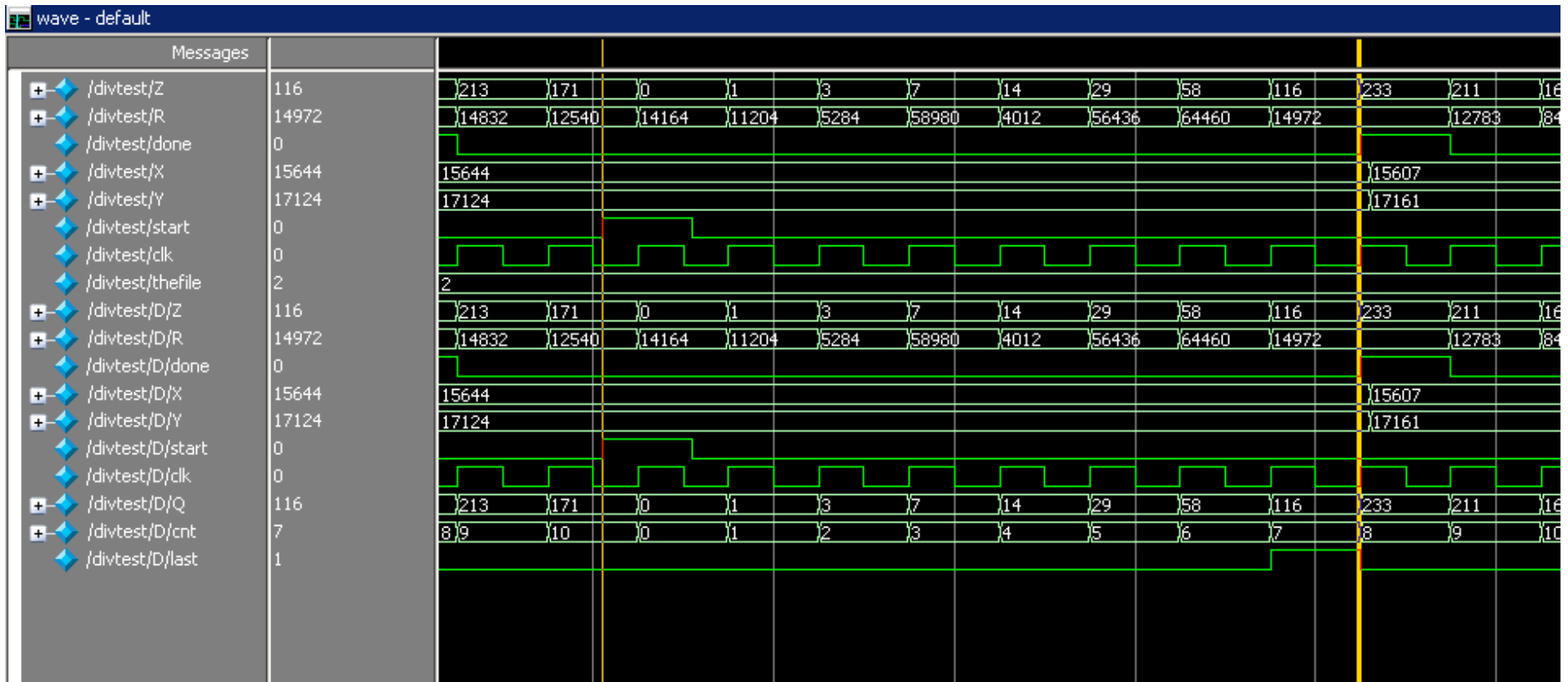


X = 15644
Y = 17124

Z = 233
R = 14972

check: $15644 * 256 - 233 * 17124 = 14972$

Simulation Output

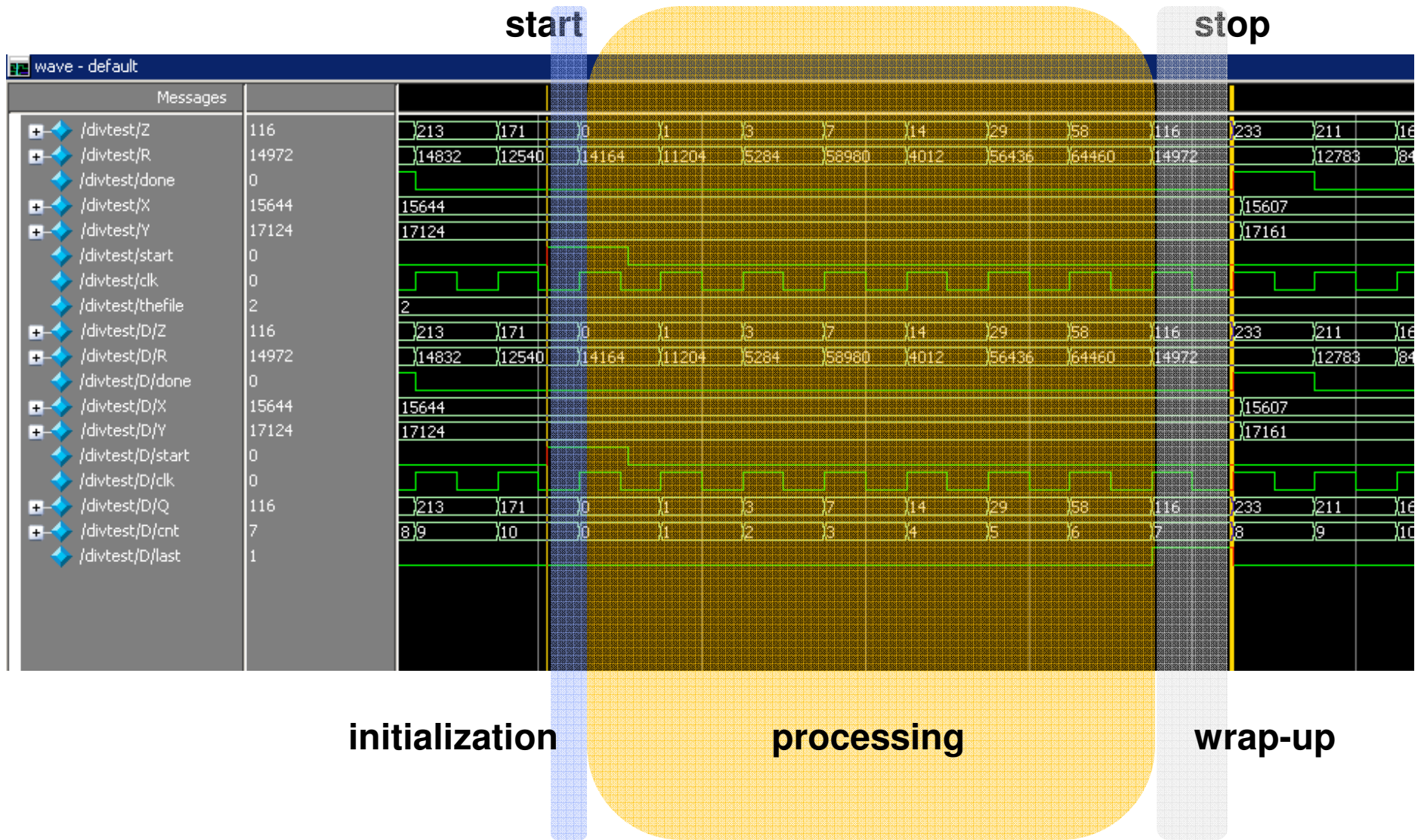

Synthesis Output

```
=====
*                               HDL Synthesis                               *
=====
```

Performing bidirectional port resolution...

Synthesizing Unit <divider>.

Related source file is "div2.v".

WARNING:Xst:647 - Input <X<15>> is never used.

WARNING:Xst - Property "use_dsp48" is not applicable for this technology.

Found 16-bit register for signal <R>.

Found 1-bit register for signal <done>.

Found 6-bit up counter for signal <cnt>.

Found 1-bit register for signal <last>.

Found 8-bit register for signal <Q>.

Found 16-bit addsub for signal <R\$mux0000>.

Summary:

inferred 1 Counter(s).

inferred 26 D-type flip-flop(s).

inferred 1 Adder/Subtractor(s).

Unit <divider> synthesized.

Expected

Indeed

INFO:Xst:1767 - HDL ADVISOR - Resource sharing has identified that some arithmetic operations in this design can share the same physical resources for reduced device utilization. For improved clock frequency you may try to disable resource sharing.

Resource Sharing

input: X, Y, evaluate X/Y

output: Q = {q(1) q(2) q(3) .. q(p)}
R

```
R = 2 * X - Y;
```

```
for i in 1 .. p-1 loop
  if (R < 0)
    q(i) = 0;
    R = 2 * R + Y;
  else
    q(i) = 1;
    R = 2 * R - Y;
```

```
if (R < 0)
  q(p) = 0; R = R + Y;
else
  q(p) = 1;
```

4 Expressions, 1 Adder/Sub

```
always @(posedge clk)
  if (start)
    R <= 2 * X - Y;
  else if (~last & R[15])
    R <= (R << 1) + Y;
  else if (~last)
    R <= (R << 1) - Y;
  else if (last & R[15])
    R <= R + Y;
  else
    R <= R;
```

Summary

- Division algorithms/architectures
 - Division as an 'inverted' multiplication
 - Division one digit at-a-time: digit-recurrence
 - The restoring divider algorithm
 - The non-restoring divider algorithm
 - Designing an architecture for a non-restoring divider