
ECE 4514 Digital Design II Spring 2007

Lecture 2: Hierarchical Design

Patrick Schaumont


Abstraction in Hardware Design

- ❑ Remember from last lecture that HDLs offer a textual description of a netlist.
- ❑ Through *abstraction* in the HDL, we can capture more than a single transistor or gate at a time.
 - Similar to a function call in C that abstracts a large collection of expressions
 - Similar to a Lego[®] castle that abstracts a large collection of Lego[®] bricks
- ❑ Verilog offers three types of abstraction
 - Structural
 - Dataflow
 - Behavioral

← These two are related, we call both of them just 'behavioral' for now

Structural Modeling

 - Describe a module in terms of components



- Netlist

- two modules: NAND_1 and NAND_2
- net 1: Rbar to NAND_1, input_1
- net 2: Sbar to NAND_2, input_2
- net 3: NAND_1, output_1 to NAND_2, input_1
- etc ..


Behavioral Modeling

- Describe a module in terms of input-output behavior

```
input S, R;  
output Q, QB;
```

```
if ( S == '1') and (R == '0') then  
    Set Q to '1', set QB to '0'  
else if ( S == '1') and (R == '1') then  
    Set Q to '1', set QB to '1'  
else if ( S == '0') and (R == '0') then  
    *Hold current state*  
else if ( S == '0') and (R == '1') then  
    Set Q to '0', set QB to '1'
```

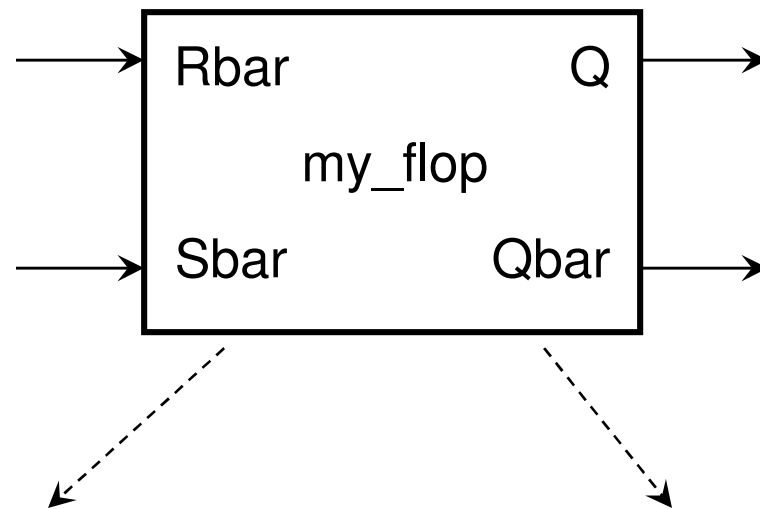Behavioral and Structural are dual mechanisms




Structural Description
explains what happens
to Q and Qbar in terms of
a netlist of lower-level
components

Behavioral Description
explains what happens
to Q and Qbar in terms of
Rbar and Sbar


Structural and Behavioral are related

- A model can be expressed as behavior or structure (of lower-level models)


Level 1

 


Level 2

 

Top-down design

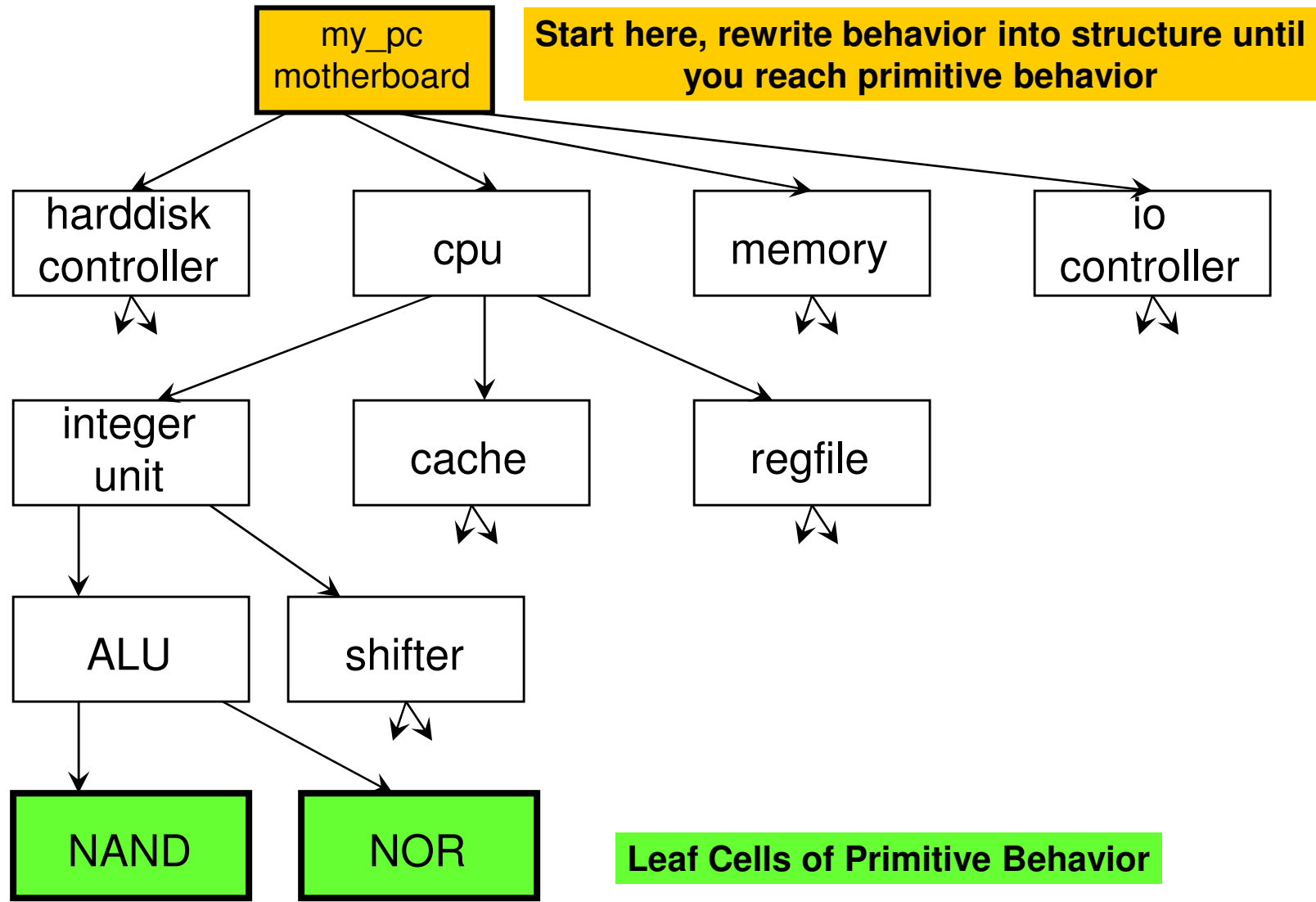

Bottom-up design

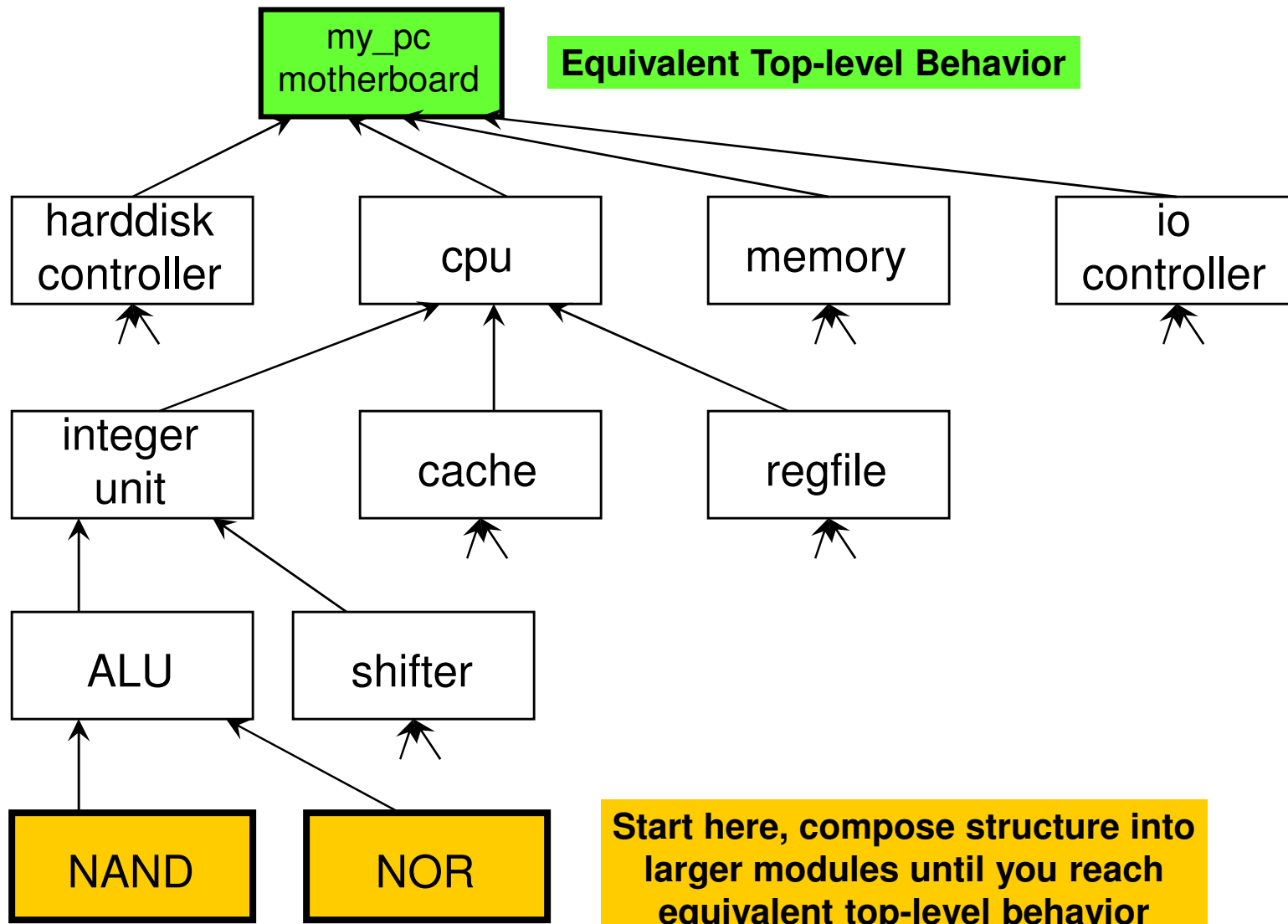


Bottom-up, Top-down are both useful

- ❑ When re-using modules from one design to the next: bottom-up
- ❑ When developing new modules from scratch: top-down
- ❑ In practice, top-down and bottom-up techniques are combined.

- ❑ In Verilog, a given module can be expressed as structure or else as behavior.
- ❑ There are two flavors of 'behavior' in Verilog
 - *Behavioral*: similar to a sequential description in C
 - *Dataflow*: a collection of concurrent expressions


Example of a hierarchical model

□ 4-bit counter

 

□ Top-level structure contains 4 interconnected T flip-flops



T flip-flop, behavior

 

Behavior can be captured in three rules:

- (1) at each negative clock edge:
 $\text{old_state} = \text{new_state}$
- (2) any time you see a change on old_state:
 $\text{new_state} = \text{not old_state}$
 $q = \text{old_state}$
- (3) any time you see a change on reset:
 $\text{new_state} = 0$

T flip-flop, structure

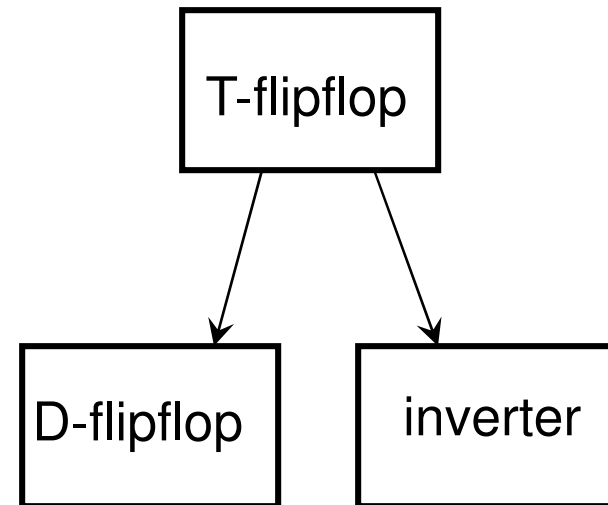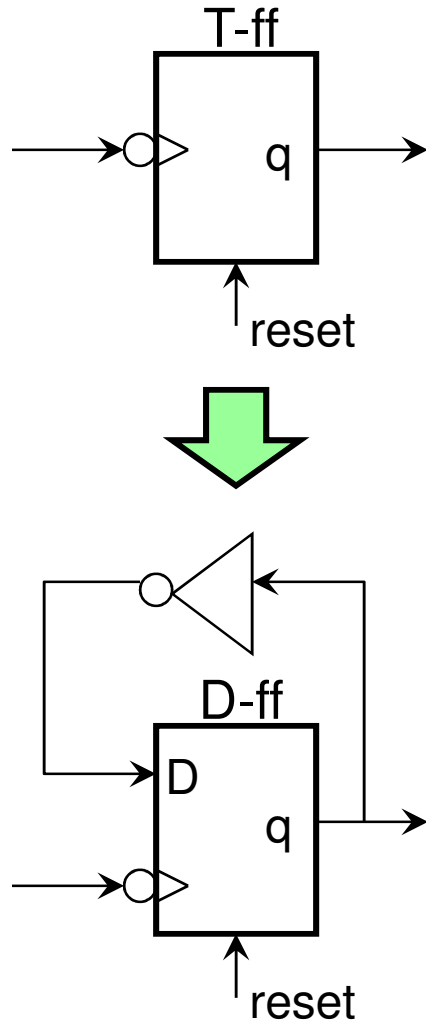

□ Thus, we can build a 4-bit counter with inverters and D flipflops

D flipflop in Verilog

```
module D_FF(q, d, clk, reset);  
    output q;  
    input d, clk, reset;  
    reg q;  
  
    always @(posedge reset or negedge clk)  
        if (reset)  
            q <= 1'b0;  
        else  
            q <= d;  
  
endmodule
```

D flipflop in Verilog

```
module D_FF(q, d, clk, reset);  
  output q;  one output port, three input ports  
  input d, clk, reset;  
  reg q;     'reg' means that q is a variable  
  
  always @(posedge reset or negedge clk)  
  if (reset)  always @(condition) means: whenever  
    q <= 1'b0;  (condition) is true, proceed.  
  else  
    q <= d;     The '<=' is called a dataflow assignment,  
               in this case the effect is similar to  
               assigning d to q  
  
endmodule
```

This is a behavioral description in dataflow format

T flipflop in Verilog

```
module T_FF(q, clk, reset);  
    output q;  
    input clk, reset;  
    wire d;  
  
    D_FF dff0(q, d, clk, reset);  
    not n1(d, q);  
  
endmodule
```

T flipflop in Verilog

```
module T_FF(q, clk, reset);  
  output q;  
  input  clk, reset;  
  wire  d;
```

```
  D_FF dff0(q, d, clk, reset);  
  not n1(d, q);
```

```
endmodule
```

connect corresponding terminals
of module

```
module D_FF(q, d, clk, reset);
```


T flipflop in Verilog

```
module T_FF (q, clk, reset);  
  output q;   
  input clk, reset;  
  wire d;  
  D_FF dff0 (q, d, clk, reset);  
  not n1 (d, q);  
endmodule
```

one output port, two input ports

a wire d has no storage: its value is always determined in terms of other variables

'not' is a *primitive* in Verilog: the simulator understands what this module does.

This is a structural description

4-bit counter in Verilog

```
module ripple_carry_counter(q, clk, reset);  
  output [3:0] q;  
  input clk, reset;  
  
  T_FF tff0(q[0], clk, reset);  
  T_FF tff1(q[1], q[0], reset);  
  T_FF tff2(q[2], q[1], reset);  
  T_FF tff3(q[3], q[2], reset);  
  
endmodule
```

4-bit counter in Verilog

```
module ripple_carry_counter(q, clk, reset);  
  output [3:0] q;      four output ports, two input ports  
  input  clk, reset;
```


```
  T_FF tff0(q[0], clk, reset);  
  T_FF tff1(q[1], q[0], reset);  
  T_FF tff2(q[2], q[1], reset);  
  T_FF tff3(q[3], q[2], reset);
```

```
endmodule
```

This is a structural description

Simulation

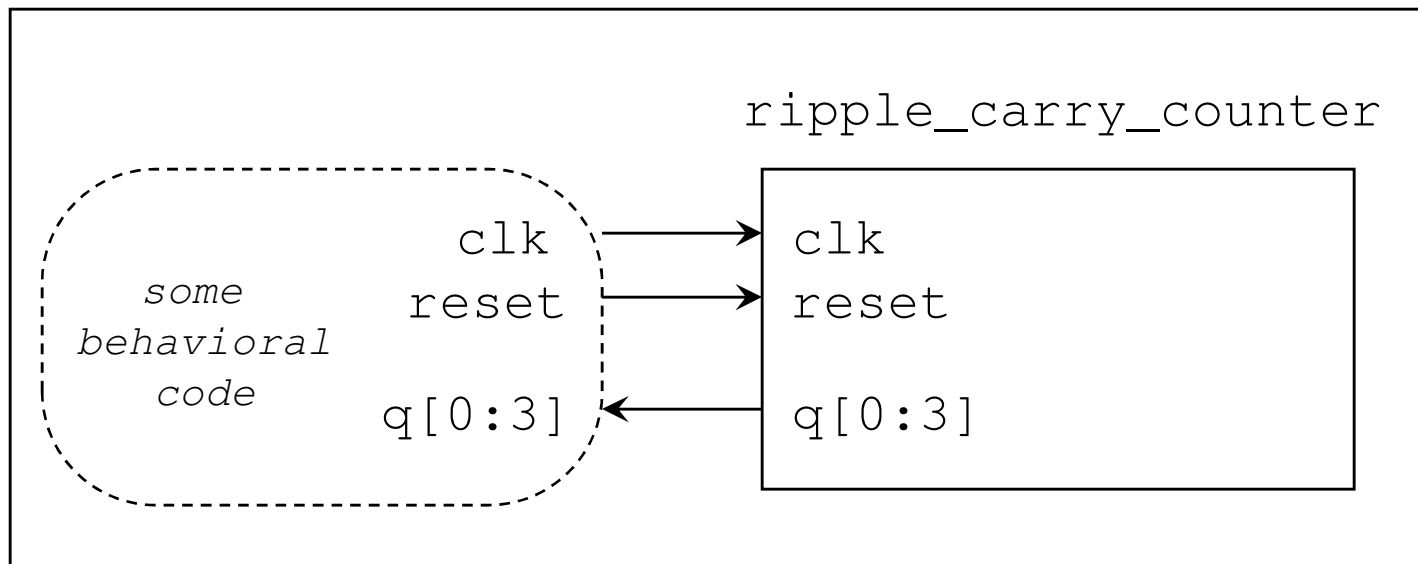- ❑ In order to test the 4-bit counter, we need a clock signal and a reset signal. We also need to monitor the counter's output.
- ❑ These activities can be implemented in a testbench.



Testbench

```
module stimulus;
  reg clk;
  reg reset;
  wire [3:0] q;

  ripple_carry_counter(q, clk, reset);

  initial
    clk = 1'b0;

  always
    #5 clk = ~clk;

  initial
  begin
    reset = 1'b1;
    #15 reset = 1'b0;
    #180 reset = 1'b1;
    #10 reset = 1'b0;
    #20 $finish;
  end

  initial
    $monitor($time, " Output q = %d", q);
endmodule
```

Testbench

```
module stimulus;  
  reg clk;  
  reg reset;  
  wire [3:0] q;
```

```
  ripple_carry_counter(q, clk, reset);
```

```
  initial
```

```
    clk = 1'b0;
```

when simulation starts, clk is low

```
  always
```

```
    #5 clk = ~clk;
```

each 5 time units, clk will flip value

```
  initial
```

```
  begin
```

```
    reset = 1'b1;
```

```
    #15 reset = 1'b0;
```

```
    #180 reset = 1'b1;
```

```
    #10 reset = 1'b0;
```

```
    #20 $finish;
```

```
  end
```

when simulation starts, reset is high.

after 15 time units, reset is low.

after 180 time units, reset is high.

after 10 time units, reset is low.


after 20 time units, stop simulation.

```
  initial
```

```
    $monitor($time, " Output q = %d", q);
```

each time q changes, print its value

Modelsim

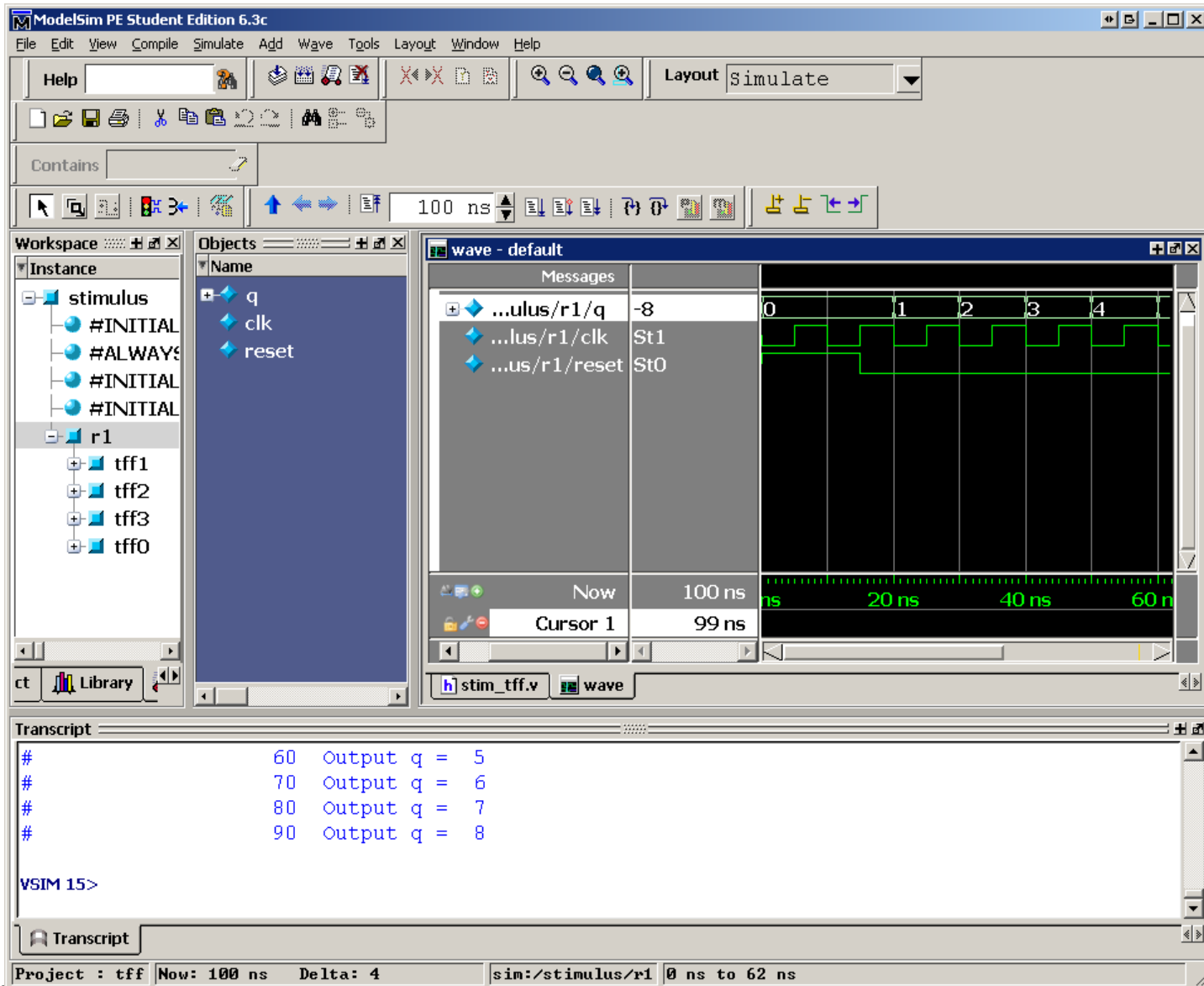

Summary

- Behavioral and Structural Modeling are two complementary forms for Hardware Description
 - They are linked with top-down (behavior into structure) or bottom-up (structure into behavior) design
 - 4-bit counter as an example of bottom-up design
 - Check design files on Blackboard