
ECE 4514 Digital Design II Spring 2007

Lecture 4: Gate Level Modeling

Patrick Schaumont

Gate-level Modeling

- ❑ In this lecture we focus on modeling and simulation of gate networks
- ❑ We will use structural modeling techniques
- ❑ We will use delay modeling to estimate the delay of a circuit

- ❑ We will discuss several examples:
 - bit comparator
 - byte comparator
 - latch
 - master/slave flip-flop


Outline

- ❑ Logic Primitive Gates
- ❑ Instantiation, Fanout, Fanin, Arrays of gates
- ❑ Truth Tables (X, Z)
- ❑ Delay Models
 - Signal propagation in gates
 - Delay modeling
- ❑ Example Models:
 - Bit-comparator, Word-comparator
 - Latches and Flip-flops


Primitive Gates

- ❑ A *primitive* is a module which you do not have to describe as the simulator already knows it
- ❑ There are 14 different primitive gates in Verilog
 - 8 of them are for logic functions (focus of this class)
 - 4 of them are for modeling tri-state signals
 - 2 of them are enhance signal strength
- ❑ New primitive gates can be added
 - User Defined Primitives (Chapter 12 Palnitkar)


Standard Logic Functions

 


and(out, in1, in2)

 


nand(out, in1, in2)

 


or(out, in1, in2)

 


nor(out, in1, in2)

 


xor(out, in1, in2)

 

xnor(out, in1, in2)

 


buf(out, in)

 


not(out, in)


More than two inputs, still a primitive

 

`and(out, in1, in2)`

 


`and(out, in1, in2, in3)`

 

`and(out, in1, in2, in3, in4, in5)`

NAND Truth Table

 
- ❑ Must deal with 'Z' and 'X' input (4-valued logic)
- ❑ Z is undefined (floating), X is unknown



		in2			
		0	1	X	Z
in1	0	1	1		
	1	1	0		
	X				
	Z				

NAND Truth Table

 
- ❑ Must deal with 'Z' and 'X' input (4-valued logic)
- ❑ Z is undefined (floating), X is unknown



With any input '0', output MUST be '1'.

NAND Truth Table

 
- ❑ Must deal with 'Z' and 'X' input (4-valued logic)
- ❑ Z is undefined (floating), X is unknown



**With an input '1', the output may be either '1' or '0',
(we don't know unless we know the value of the other input)**


NAND Truth Table

 - ❑ Must deal with 'Z' and 'X' input (4-valued logic)
- ❑ Z is undefined (floating), X is unknown




With an input unknown, we have no clue what the output may be (even if we know the other input)

NOR Truth Table

 

		in2			
		0	1	X	Z
in1	0	1	0		
	1	0	0		
	X				
	Z				


NOR Truth Table

 

		in2			
		0	1	X	Z
in1	0	1	0		
	1	0	0	0	0
	X		0		
	Z		0		

If an input is '1', the output MUST be 0.


NOR Truth Table

 

		in2			
		0	1	X	Z
in1	0	1	0	X	X
	1	0	0	0	0
	X	X	0	X	X
	Z	X	0	X	X

In all other cases, we don't know.

XOR Truth Table

 


		in2			
		0	1	X	Z
in1	0	0	1	X	X
	1	1	0	X	X
	X	X	X	<input type="text"/>	X
	Z	X	X	X	<input type="text"/>

Two arrows point from the empty circles in the table to the text below.

What should go here ? 0 or X ?

XOR Truth Table

 


	in2			
	0	1	X	Z
0	0	1	X	X
1	1	0	X	X
X	X	X	X	X
Z	X	X	X	X

The table shows the output of an XOR gate for various combinations of inputs. The inputs are labeled 'in1' and 'in2'. The outputs are labeled '0', '1', 'X', and 'Z'. The 'X' and 'Z' outputs are circled in the original image, and arrows point from them to the text below.

The simulator says 'X'. Shouldn't this be '0'?
After all, $(1 \text{ XOR } 1) = 0$ and $(0 \text{ XOR } 0) = 0$..


What would Verilog do?

 - If you answered 'it should be X', then what is the output of the following circuit ?




What would Verilog do?

 - If you answered 'it should be X', then what is the output of the following circuit ?



What would Verilog do?

 
- If you answered 'it should be X', then what is the output of the following circuit ?



4-valued logic is an abstraction,
sometimes it may be more abstract than
what you had intended ...

Gate Instantiation: Bit Comparator Example

 - Bit comparator: Q indicates if $A > B$
G is a cascading input





Pseudocode:

```
if (A = 1) and (B = 0)
  then Q is 1
else if (A=B) and (G = 1)
  then Q is 1
else Q is 0
```

		AB			
		00	01	11	10
G	0				
	1				

Gate Instantiation: Bit Comparator Example

  
- Bit comparator: Q indicates if $A > B$
G is a cascading input




Gate Instantiation: Bit Comparator Example

- Bit comparator: Q indicates if $A > B$
G is a cascading input

		AB			
		00	01	11	10
G	0				1
	1	1		1	1

 


$$Q = A.B' + G.B' + G.A$$

 

On the side - Fan-in, Fan-out

 - ❑ Fan-in = number of inputs on a logic gate
- ❑ Fan-out = max number of gates that can be driven by an output




Fan-in = 1
Fan-out = 2

Fan-in = 2
Fan-out = 1

Fan-in = 3
Fan-out = ?


Gate Instantiation: Bit Comparator Example

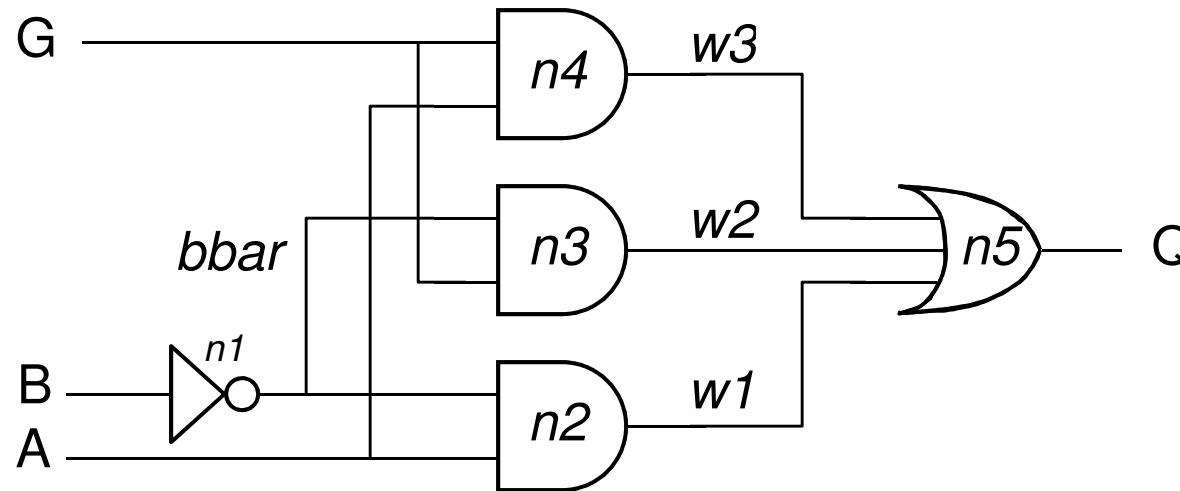- ❑ To convert to Structural Verilog
 - Label all nets. Create `wires` for intermediate signals.
 - Label all gate instances
 - Write out netlist in text format



Gate Instantiation: Bit Comparator Example

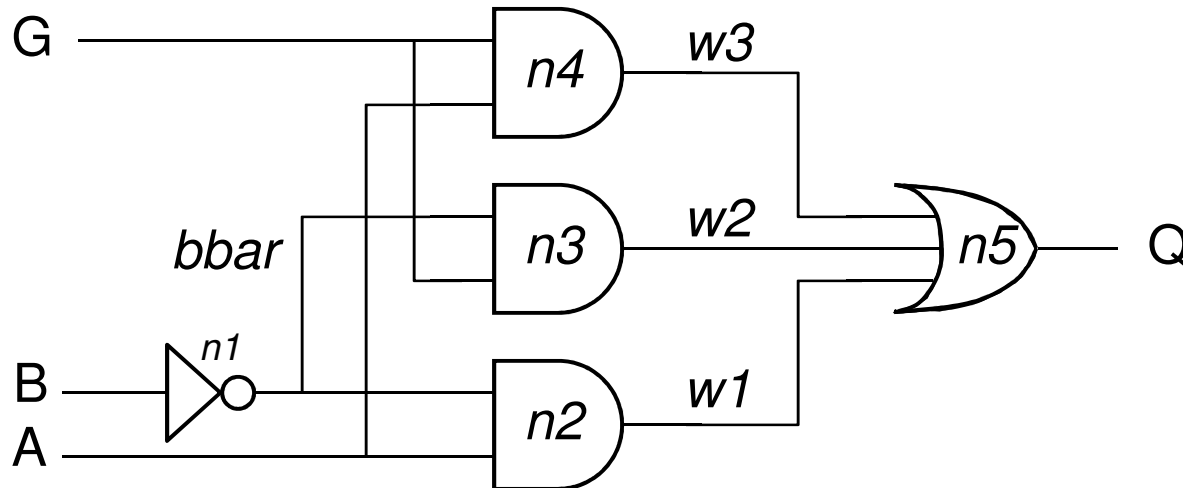
```
module bitcomp(q, a, b, g);  
  output q;  
  input a, b, g;  
  wire bbar, w1, w2, w3;  
  not n1(bbar, b);  
  and n2(w1, bbar, a);  
  and n3(w2, bbar, g);  
  and n4(w3, a, g);  
  or n5(q, w1, w2, w3);  
endmodule
```



Gate Instantiation: Bit Comparator Example


```
module bitcomp(q, a, b, g);  
  output q;  
  input a, b, g;  
  wire bbar, w1, w2, w3;  
  not (bbar, b);  
  and (w1, bbar, a);  
  and (w2, bbar, g);  
  and (w3, a, g);  
  or (q, w1, w2, w3);  
endmodule
```

Gate instance name
is optional




 


Gate Array Instantiation


```
wire q, a, b;  
and (q, a, b);
```

 
    
```
wire [0:3] q, a, b;  
and [0:3] (q, a, b);
```



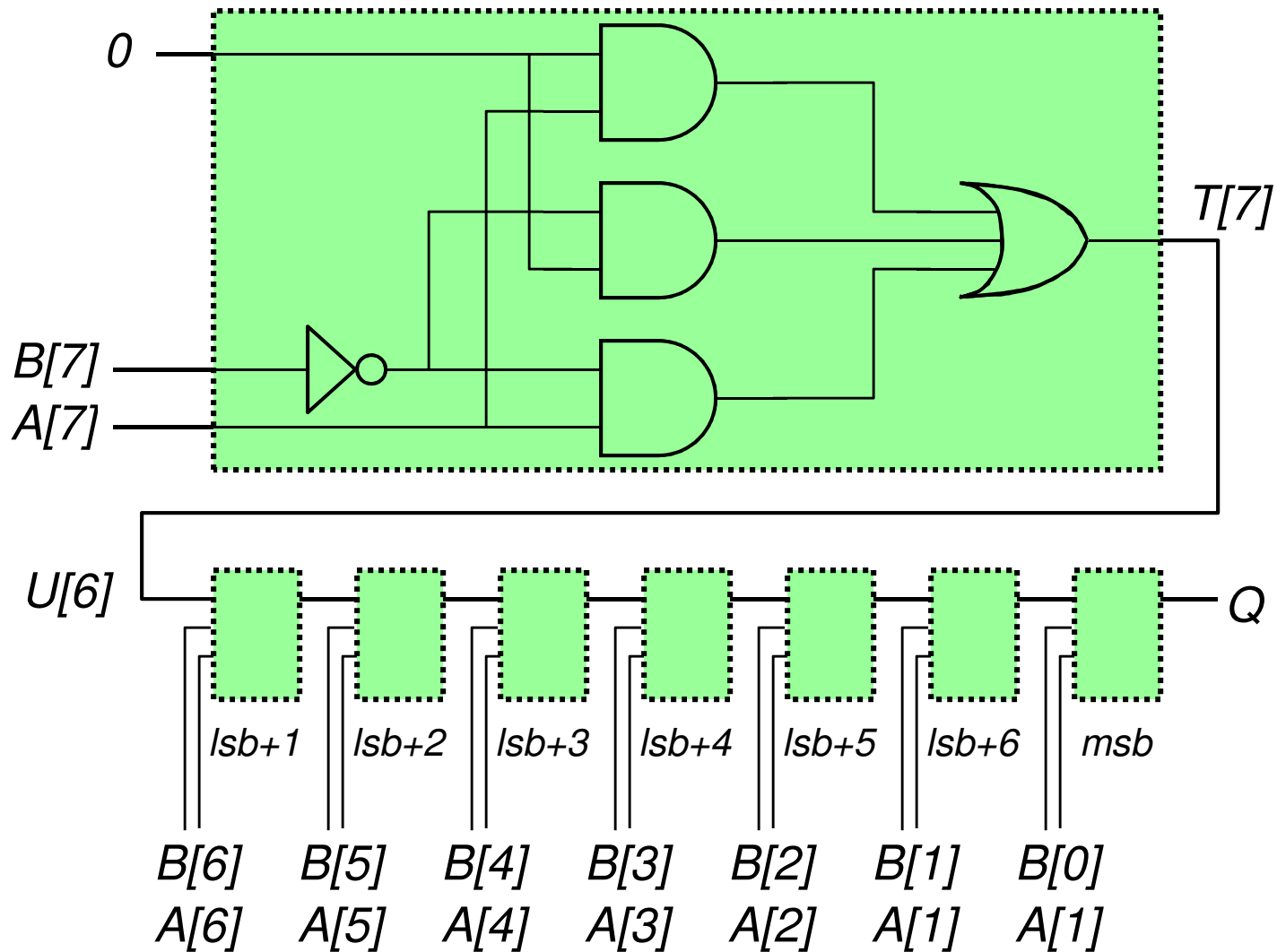Gate Array Instantiation: Byte Comparator



Gate Instantiation: Bit Comparator Example

```
module bytecomp(q, a, b);
    output q;
    input [0:7] a, b;
    wire [0:7] t, u, bbar, w1, w2, w3;

    not n1[0:7] (bbar, b);           // 8 not gates
    and n2[0:7] (w1, bbar, a);      // 8 and gates
    and n3[0:7] (w2, bbar, u);     // ...
    and n4[0:7] (w3, a, u);
    or n5[0:7] (t, w1, w2, w3);

    assign u[7] = 0;               // wire-to-wire
    assign u[0:6] = t[1:7];       // connection
    assign q = t[0];
endmodule
```

Alternate Description of Byte Comparator

```
module bytecomp(q, a, b);
    output q;
    input [0:7] a, b;
    wire [0:7] t, u;

    bitcomp n1[0:7] (t, a, b, u);

    assign u[7] = 0; // wire-to-wire
    assign u[0:6] = t[1:7]; // connection
    assign q = t[0];
endmodule
```

- ❑ In the above description there are 3 levels of hierarchy.
- ❑ In the description on the previous slide, there are only two levels of hierarchy.

Bytecomp Testbench Example

```

module tbytecomp;
    reg [0:7] a, b;           // reg at input
    wire q;                 // only wire at output
    bytecomp y(q, a, b);


    initial begin
        a = 0;
        b = 0;
    end

    always begin
        #10
        a = a + 1;
        b = b + 3;
    end
endmodule


```

Messages					
◆ /tbytecomp/a	50	54	55	56	57
◆ /tbytecomp/b	f0	fc	ff	02	05
◆ /tbytecomp/q	0				
◆ ...comp/y/q	0				
◆ ...comp/y/a	50	54	55	56	57

Gate Level Timing - The Big Idea

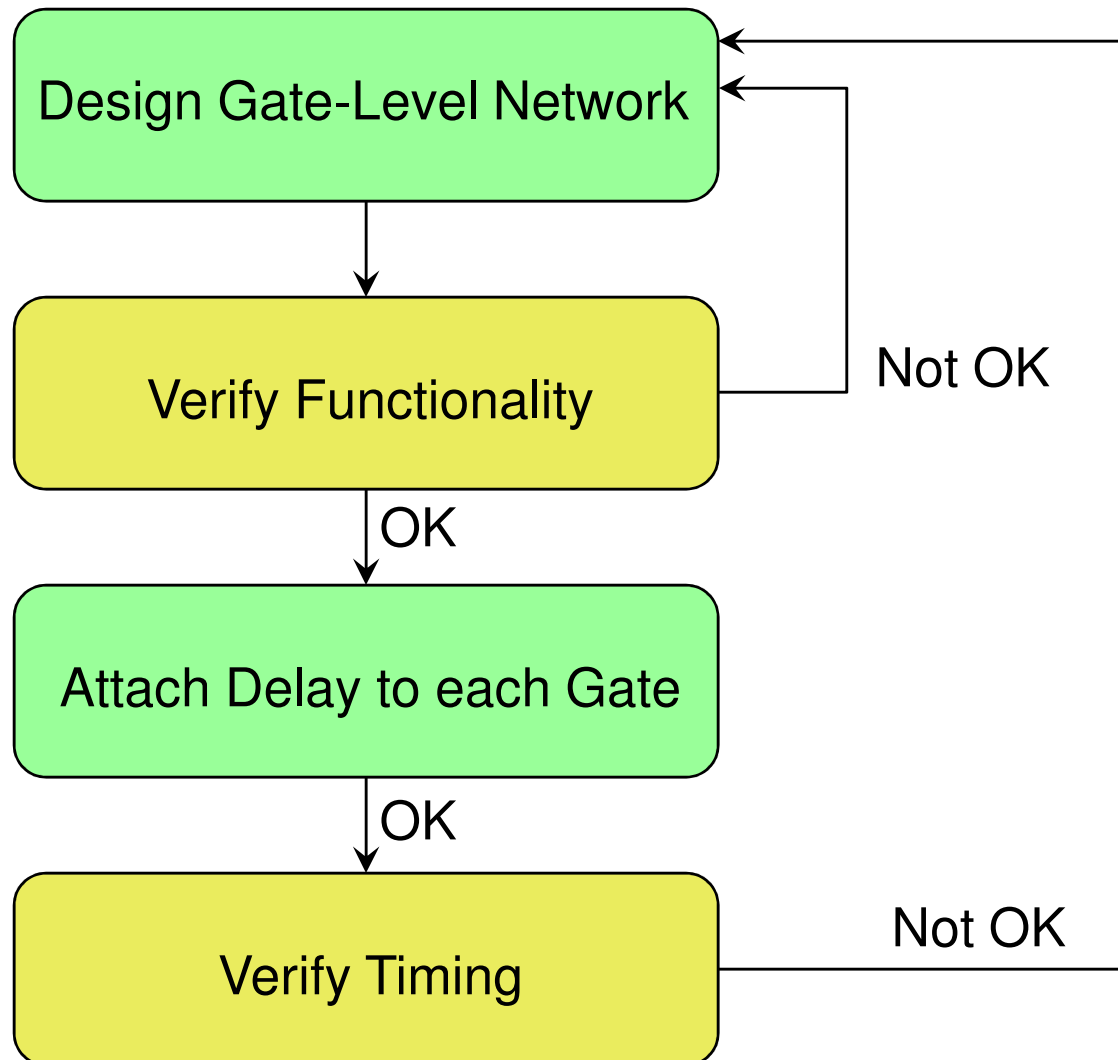


Gate Level Timing - The Big Idea

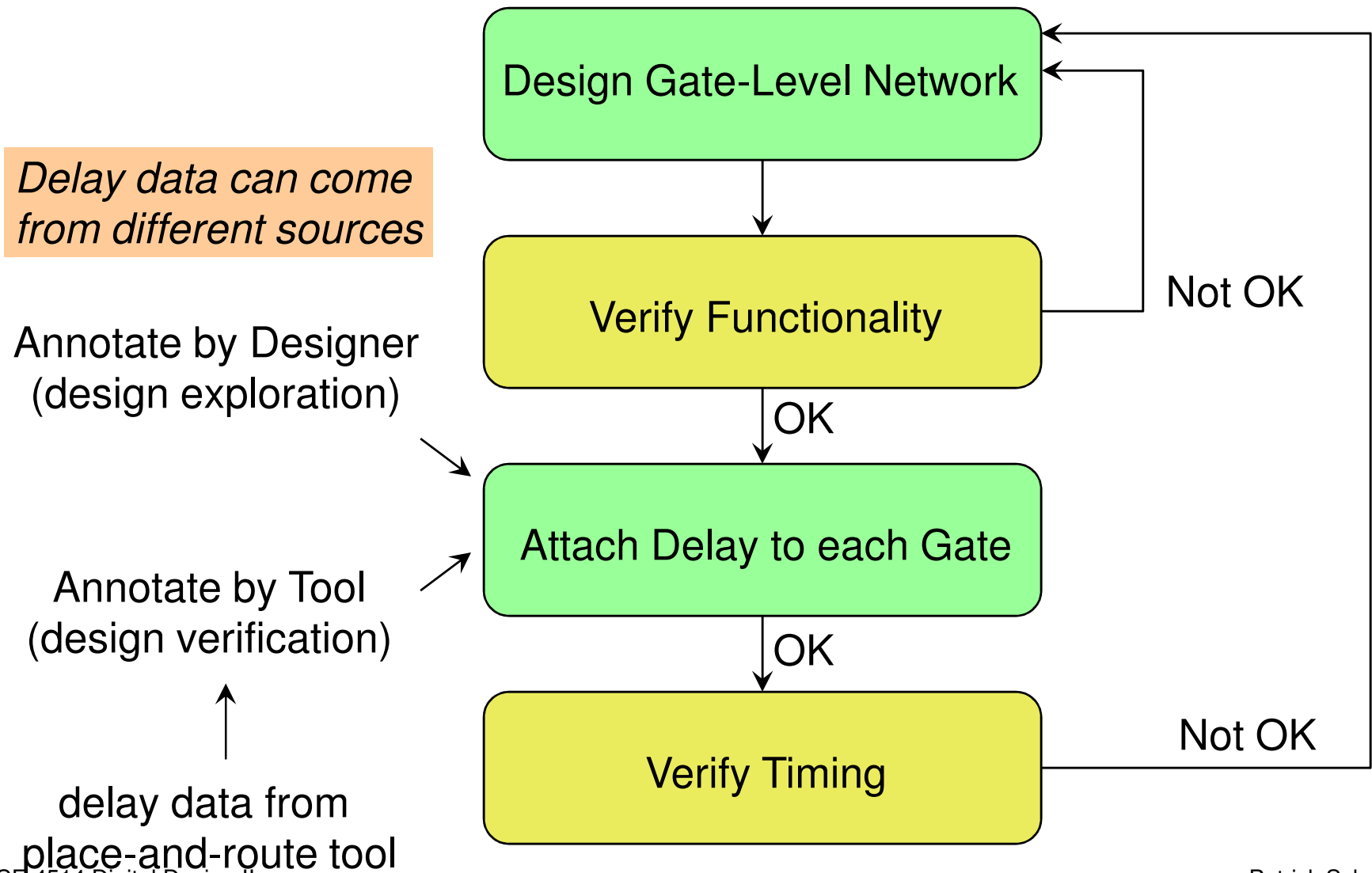


Gate-level timing

 - Default model for gates does not have delay




```
and n1 (q, a, b) ;
```

 


Gate-level timing

 - Standard delay model specifies propagation delay




```
and #(8) n1(q, a, b);
```

 

Gate-level timing

- Propagation Delay for gates really specifies two things:
 - Delay from input to output
 - Minimum width of pulses to affect the output


```
and # (8) n1 (q, a, b) ;
```

 

**Pulses smaller than 8
do not propagate to the output**


Delay Propagation Models

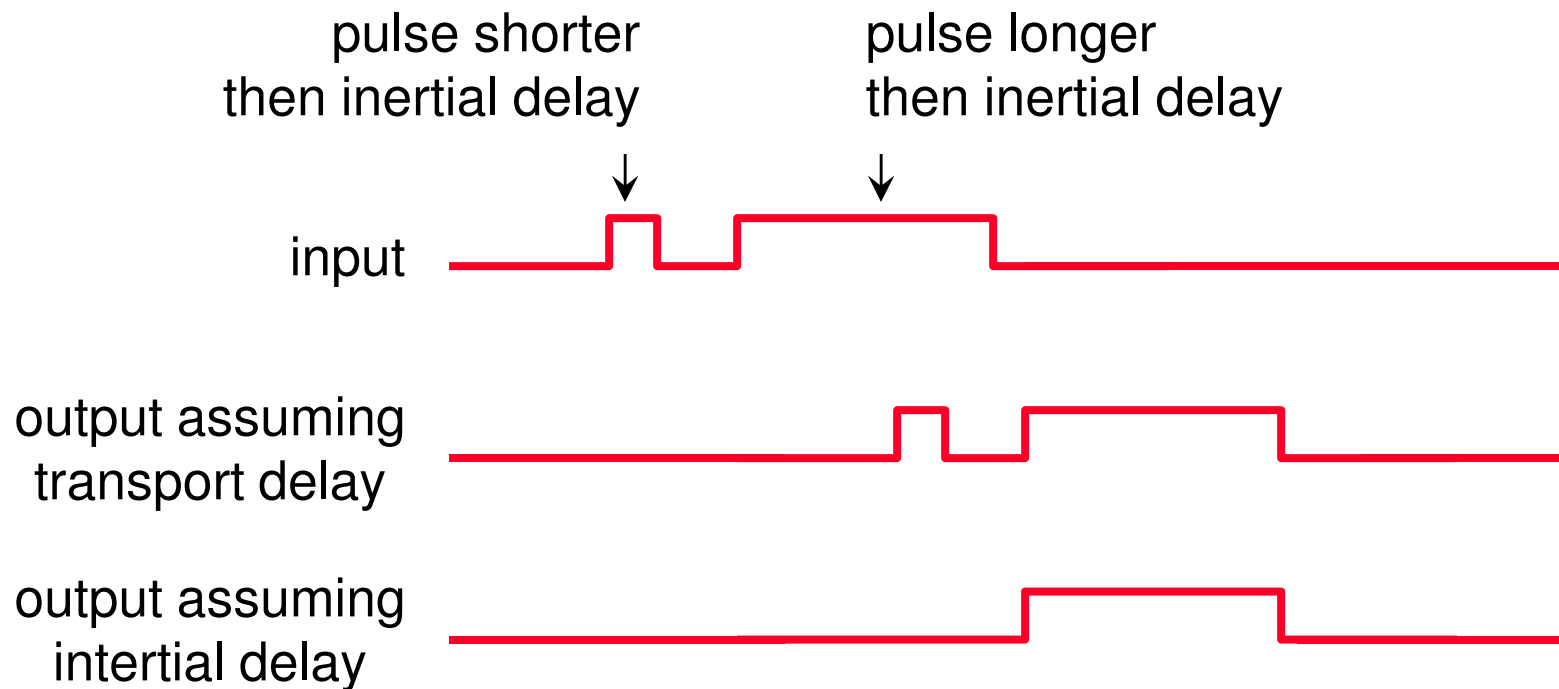- ❑ Gates use *inertial delay*
- ❑ Designers may also want to use *transport delay* (for example to model slow wires).




Gate-level timing

 - Advanced model specifies propagation delay for up- and down-transitions separately




```
and #(8, 6) n1(q, a, b);
```

 

Gate-level timing

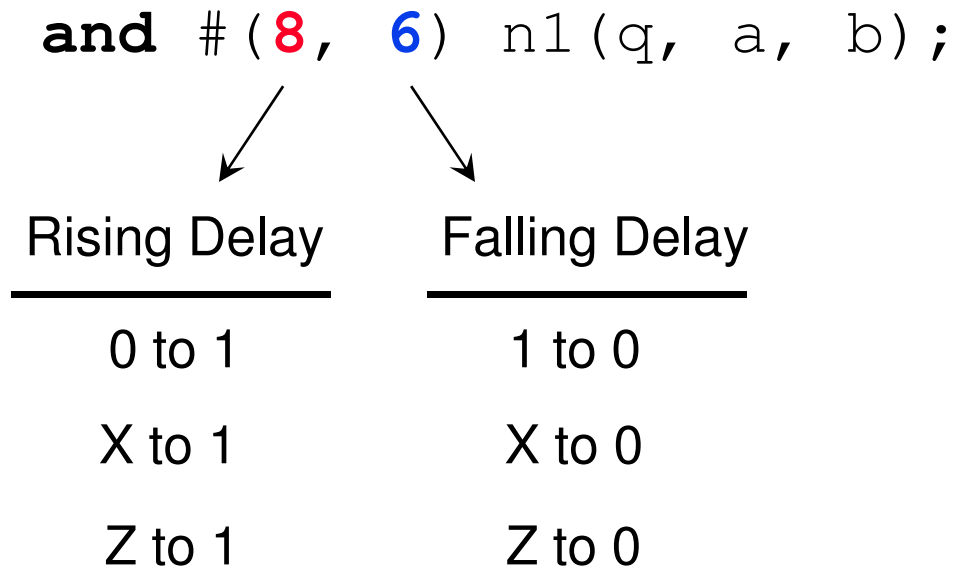- Other delays follow automatically, for example



In all other cases: Delay = min(Rise, Fall)

E.g. 1 to X ? Take min(8,6) = 6

Min:Typ:Max Delays

- ❑ Circuits show delay variations
 - Due to implementation & process parameters
 - Due to voltage and temperature


- ❑ Designers create circuits to work within an operation-range, corresponding to a domain (military, commercial, ..)

- ❑ Verilog allows to capture the effect of these variations by supporting multiple delay specifications for a gate
 - 'Typical': room temperature, normal voltage
 - 'Max': high temperature, low voltage, [slow circuit]
 - 'Min': low temperature, high voltage, [fast circuit]


Where are the time units?

- ❑ Verilog specifies relative delay in *units*
- ❑ The simulation timescale is provided through a directive at the top of the Verilog file (or modelsim.ini)

```
`timescale 10ns / 100ps
```

 

Time Unit
#33 equals 330 ns

 

Simulation Precision
#45.1355 equals 451 ns
#66.97 equals 670 ns


Gate Level Timing Example

```
module bytecomp(q, a, b);
    output q;
    input [0:7] a, b;
    wire [0:7] t, u, bbar, w1, w2, w3;

    not #5 n1[0:7] (bbar, b); // 8 not gates
    and #7 n2[0:7] (w1, bbar, a); // 8 and gates
    and #7 n3[0:7] (w2, bbar, u); // ...
    and #7 n4[0:7] (w3, a, u);
    or #7 n5[0:7] (t, w1, w2, w3);


    assign u[7] = 0; // wire-to-wire
    assign u[0:6] = t[1:7]; // connection
    assign q = t[0];
endmodule
```

Estimating worst-case timing of bytecomp

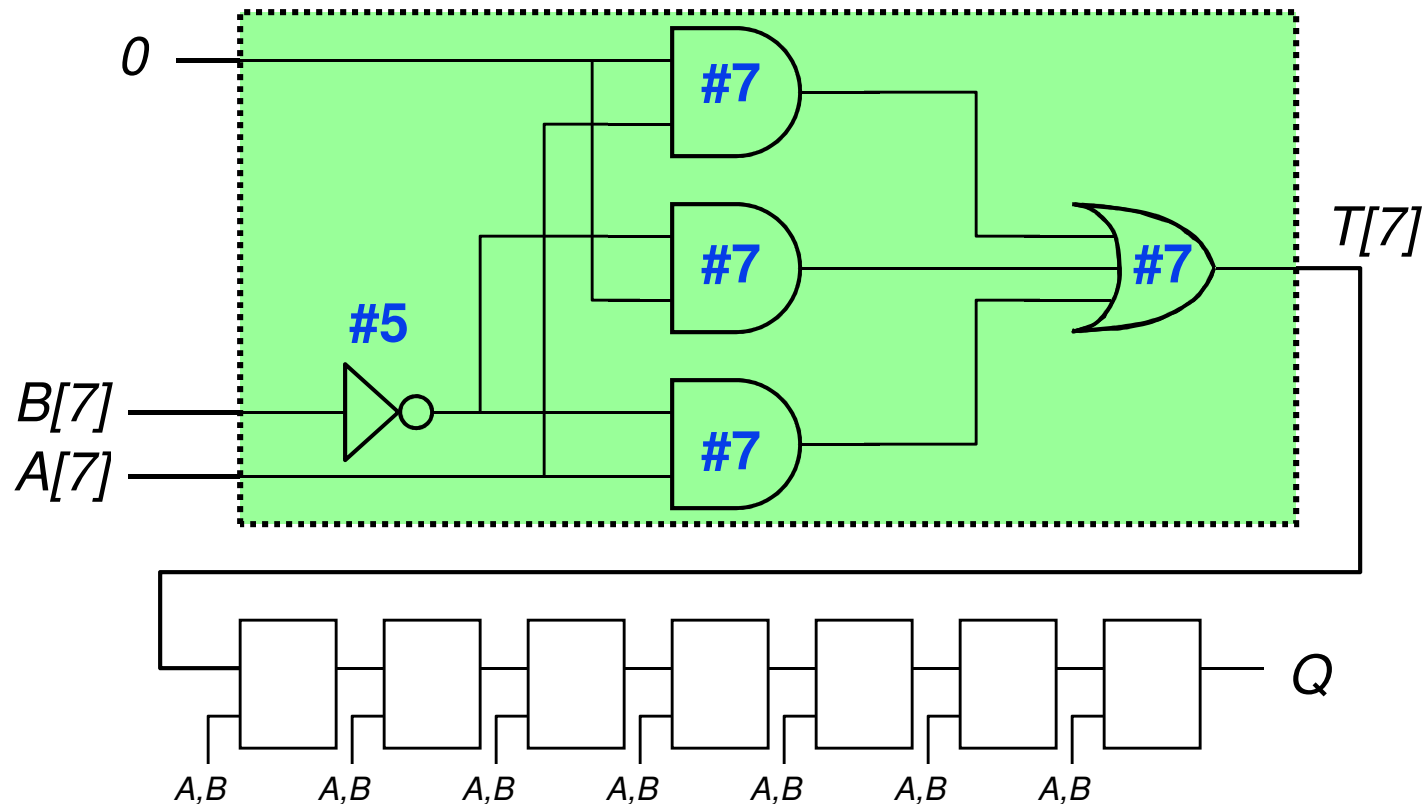

1. What is the worst possible path through the byte comparator ?
2. How can you trigger it ?


Estimating worst-case timing

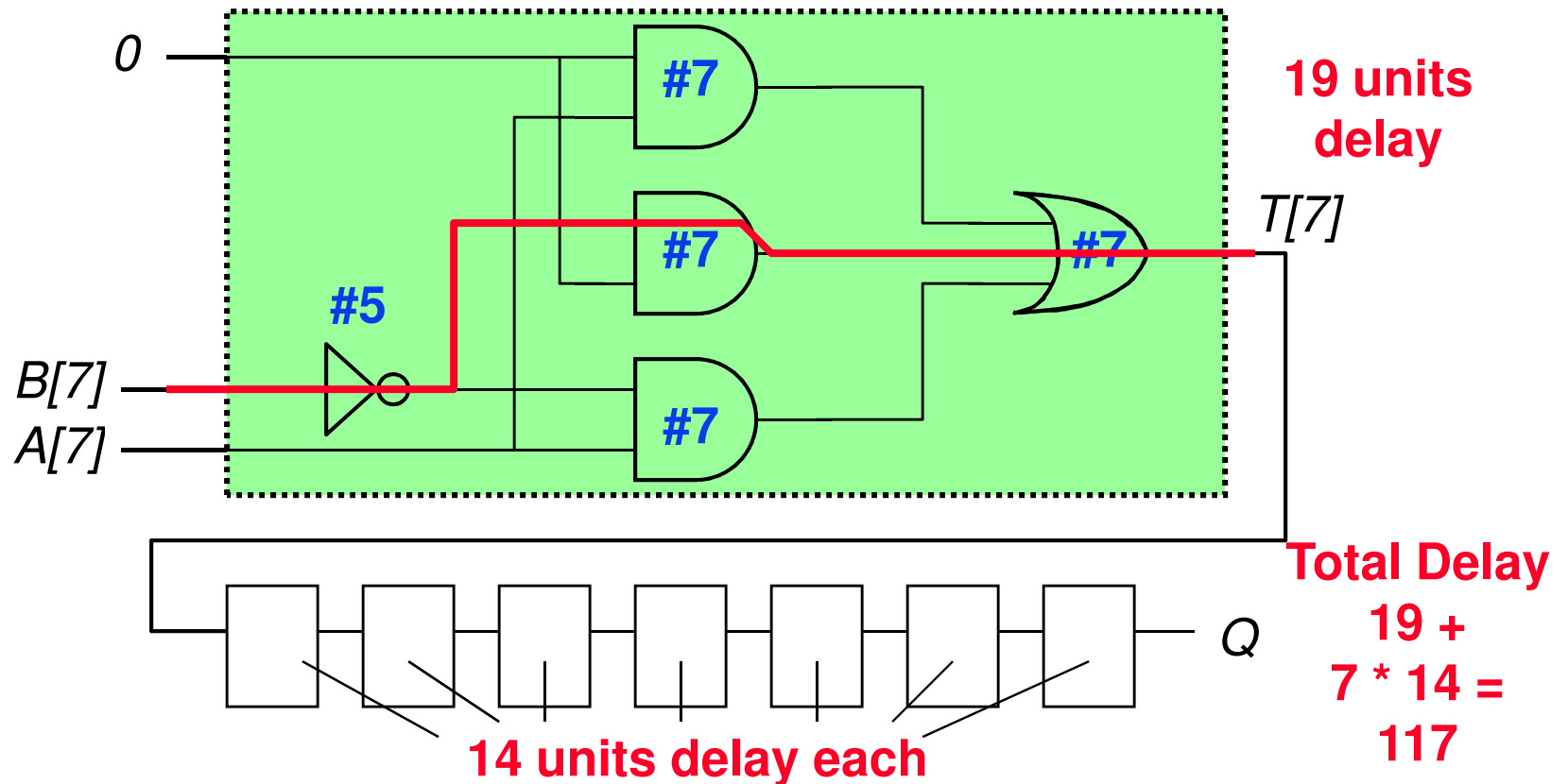

1. What is the worst possible path through the byte comparator ?
2. How can you trigger it ?

**Apply 1 to A and 0 to B -> Q is high
then set B to 1 -> Q falls to low after 117**

Simulating worst-case timing

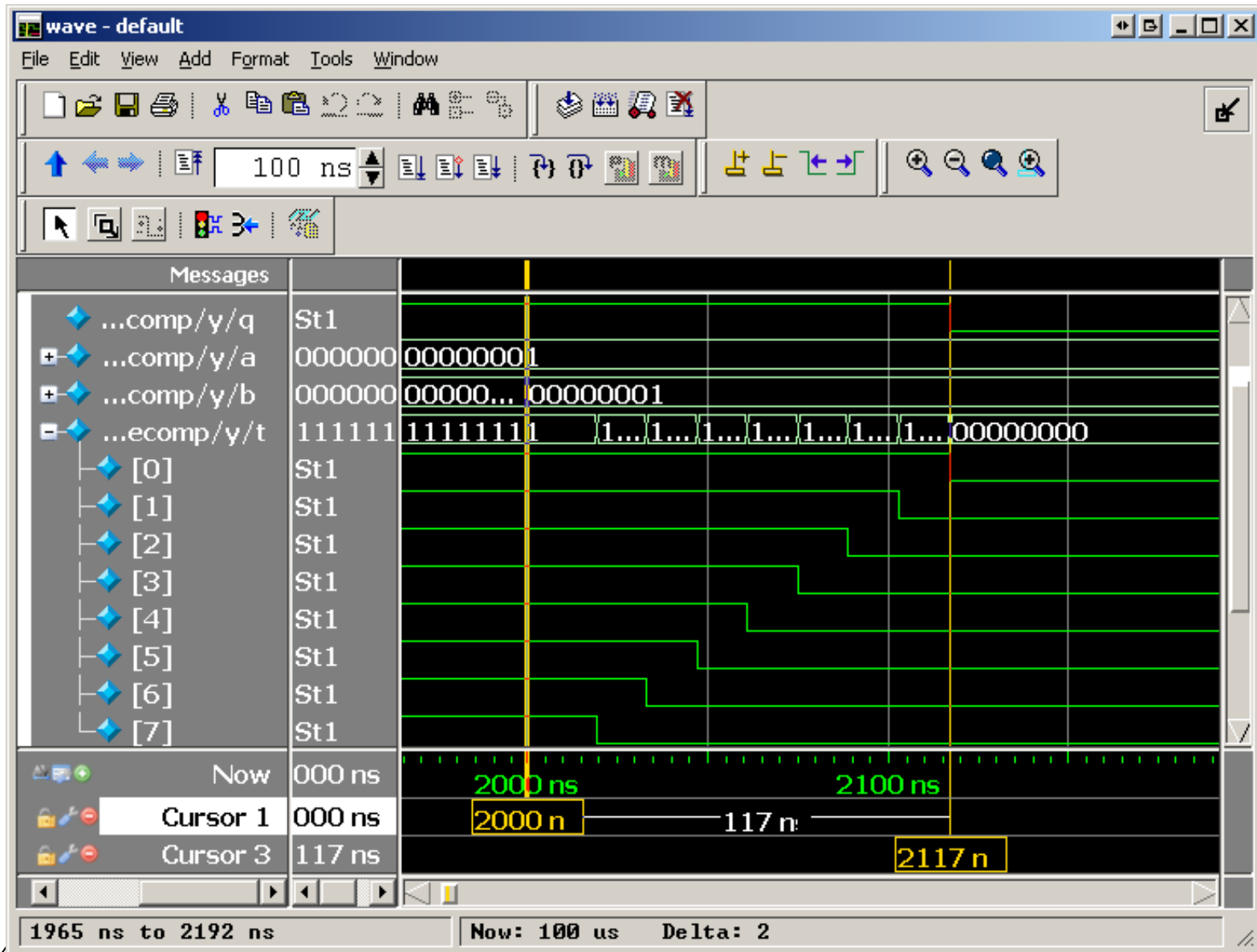

Testbench for worst-case timing

```
module tbytecomp;
    reg [0:7] a, b;
    wire  q;

    bytecomp y(q, a, b);

    initial begin
        a = 0;
        b = 0;
    end

    always begin
        #1000
        a = 1;
        b = 0;
        #1000
        a = 1;
        b = 1;
    end
endmodule
```


Latches and Flip-flops

- So far, the only flip-flop we used was a D-flipflop described at *dataflow* level

```
module syntst(q, d, clk);  
    input clk, d;  
    output q;  
    reg q;  
  
    always @(posedge clk)  
    begin  
        q <= d;  
    end  
  
endmodule
```

- We can also create storage modules out of gates

SR Latch

 

```
module sr_latch(Q, Qbar, S, R);
```

```
output Q, Qbar;
```



```
input S, R;
```

```
nor n1(Q, Sbar, Qbar);
```



```
nor n2(Qbar, Rbar, Q);
```

```
endmodule
```



SR Latch

 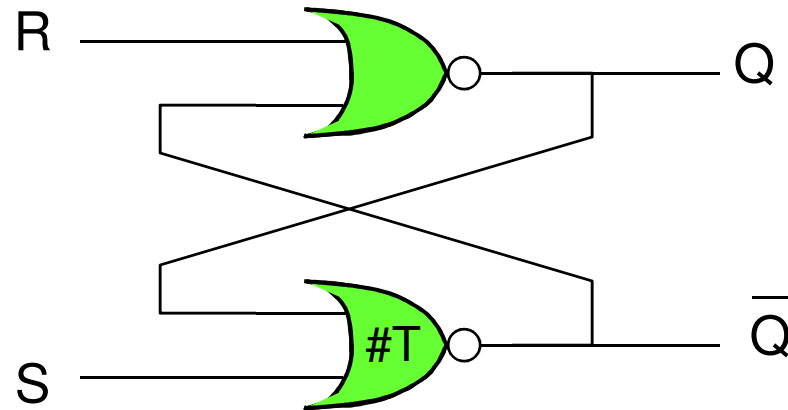

SR Latch

   


Level-Sensitive D-Latch



- ❑ clk to short: D will not propagate to SR
- ❑ clk to long: D may change while clk is high

Edge-Sensitive D-Latch

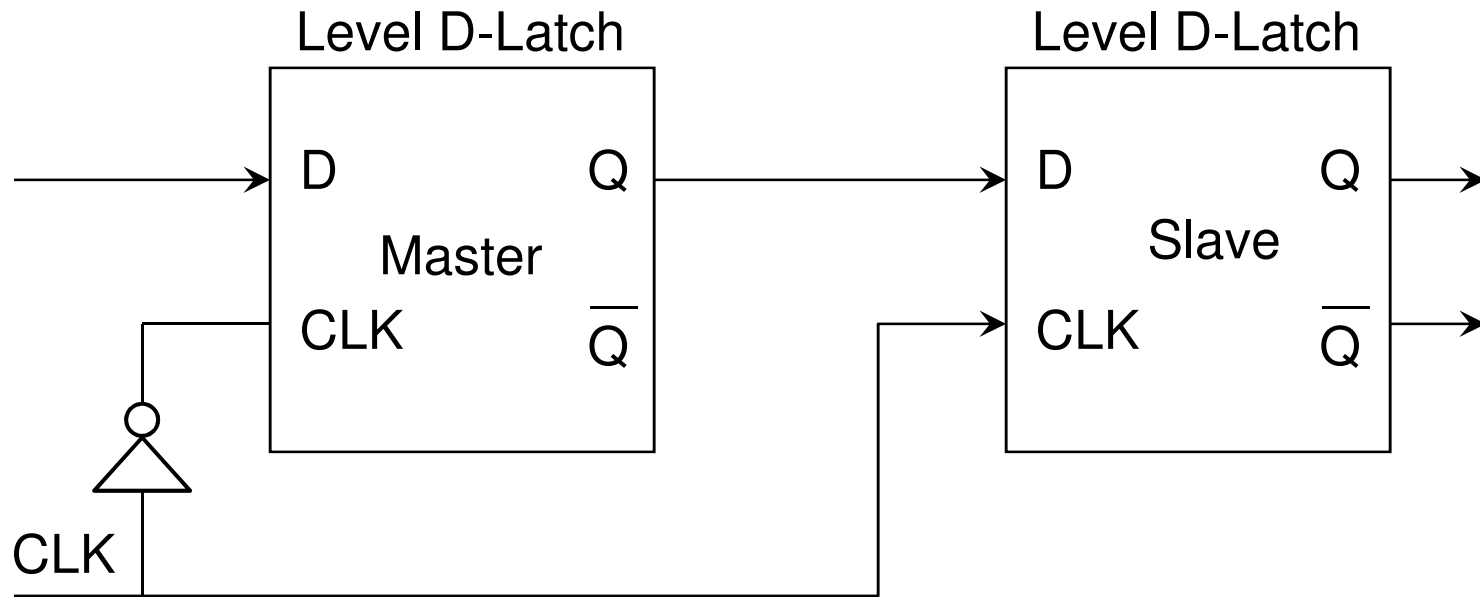

CLK	low	high
Master	open	close
Slave	close	open

Summary

- ❑ Gates are primitive modules for the Verilog simulator
- ❑ Create gate networks as structural Verilog netlists
- ❑ Annotate netlist with delays for timing analysis
- ❑ Evaluation of critical path requires more than decorating times - also clever analysis to trigger worst-case condition