
ECE 4514

Digital Design II

Spring 2008

Lecture 7:


Dataflow Modeling

A language Lecture

Patrick Schaumont

Today's topic

□ Dataflow Modeling

 

Model with submodules
and gates

=

Structural

Model with always
and initial blocks

=


*Behavioral
Procedural*

Model with
assign statements

=

*Behavioral
Dataflow*

Example

 

Structural

```
module nand(q, a, b)
output q;
input a, b;

wire n;

and G1(n, a, b);
not G2(q, n);
endmodule
```

Behavioral Procedural

```
module nand(q, a, b)
output q;
reg q;
input a, b;

always @(a or b)
    q = ~(a | b);

endmodule
```

Behavioral Dataflow

```
module nand(q, a, b)
output q;
input a, b;

assign q = ~(a | b);

endmodule
```

Key differences with procedural code

- ❑ Must assign nets (wires) instead of registers

*Behavioral - Procedural
assign reg*

```
module nand(q, a, b)
  output q;
  reg q;
  input a, b;

  always @(a or b)
    q = ~(a | b);
endmodule
```

*Procedural
Assignment*

*Behavioral - Dataflow
assign wire*

```
module nand(q, a, b)
  output q;
  input a, b;

  assign q = ~(a | b);
endmodule
```

*Continuous
Assignment*

Key differences with procedural code

- ❑ Must assign nets (wires) instead of registers

Behavioral - Procedural
assign reg

```
module nand(q, a, b)
  output q;
  reg q;
  input a, b;

  always @(a or b)
    q = ~(a | b);

endmodule
```


Behavioral - Dataflow
assign wire

```
module nand(q, a, b)
  output q;
  input a, b;

  assign q = ~(a | b);

endmodule
```

 Note that both will end up as the same hardware



Two forms of assignment

□ Net Declaration (*Palnitkar: Implicit Assignment*)


```
module nand(q, a, b)
  output q;
  input a, b;

  wire n = (a | b);
  ...
endmodule
```

□ Continuous Assignment

```
module nand(q, a, b)
  output q;
  input a, b;

  wire n;
  assign n = (a | b);
  ...
endmodule
```

 


Assign two wires

Concurrent Assign statements

```
module nand(q1, q2, a, b)
  output q1, q2;
  input a, b;

  assign q1 = ~(a | b);
  assign q2 = ~(a & b);
  ...
endmodule
```

 


Assign two wires

Single Assign statement with two independent assignments

```
module nand(q1, q2, a, b)
  output q1, q2;
  input a, b;

  assign q1 = ~(a | b),
         q2 = ~(a & b);
  ...
endmodule
```

 


Assign two wires

Single Assign statement with a vector assignment

```
module nand(q1, q2, a, b)
output q1, q2;
input a, b;

assign {q1, q2} = {~(a | b),
                  ~(a & b)};

...
endmodule
```

 

Useful to partition results from an expression:

```
reg a, b, c;
wire c0, d;
assign {c0, d} = a + b + c;
```

Delay in continuous assignments

```
module nand(q, a, b)
  output q;
  input a, b;

  wire n;
  assign #10 n = ~(a | b);
  ...
endmodule
```

Changes to n take an *inertial delay* of 10 units

```
module nand(q, a, b)
  output q;
  input a, b;

  wire n;
  assign (#10, #15) n = ~(a | b);
  ...
endmodule
```

Changes to n take an *inertial delay* of 10 units for rising edges and 15 units for falling edges

Delay in continuous implicit assignments

```
module nand(q, a, b)
output q;
input a, b;
```

```
wire #10 n = ~(a | b);
...
endmodule
```


Changes to n take an *inertial delay* of 10 units

```
module nand(q, a, b)
output q;
input a, b;
```

```
wire #10 n;
assign #10 n = ~(a | b);
...
endmodule
```

Changes to n take an *inertial delay* of 20 units

Operands and Operators

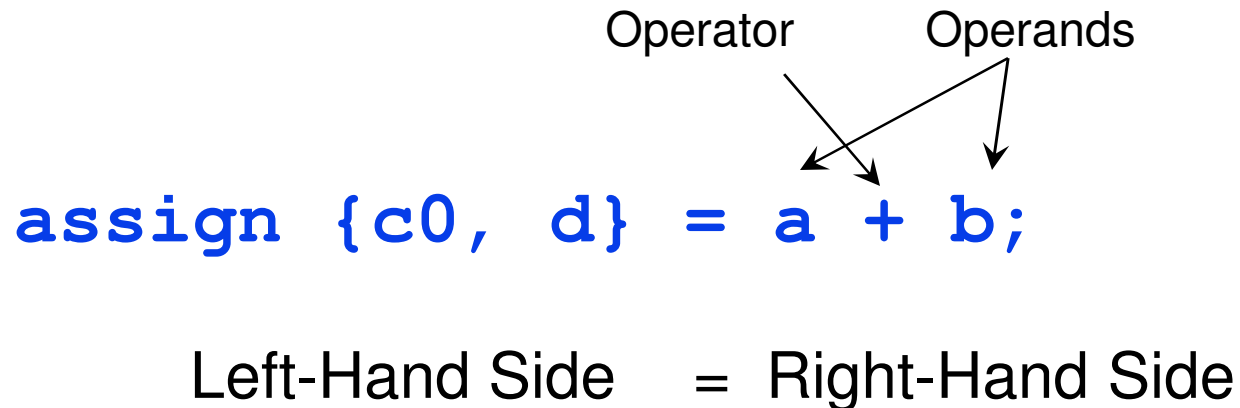

□ What we will cover:

- What operand types can I use?
- What operators are available ? What is their precedence ?
- What are the rules for expression precision ?

Operand Types

```
assign {c0, d} = a + b;
```

Left-Hand Side = Right-Hand Side

nets (wire)

nets (wire)
variable (reg)
parameters
numbers
function call

Operand Bit-select and Part-select

```
wire [7:0] n;
```

<code>n[3:0]</code>	Bit 3, 2, 1, 0
<code>n[3]</code>	Bit 3
<code>n[x]</code>	X
<code>n[3+:2]</code>	Bit 3, 4

Operand Memory, Memory Indexing

```
wire [7:0] n[0:99];
```

`n[15]`

Element 16

`n[15][5]`

Bit 3 of Element 16

`n[15][0:3]`

Bits 0:3 of Element 16


`n[15:0]`

Illegal

Operand Types

Left-Hand Side = Right-Hand Side

'net' can be

 

- net
- net bit-select or part-select
- indexed net
- indexed net bit-select or part-select
- concatenated net

```
wire [7:0] n[0:99];  
{n[15][0:3], n[2]} = 5_bit_expr;
```


Operators

- ❑ Arithmetic
- ❑ Bitwise
- ❑ Reduction
- ❑ Logical
- ❑ Relational
- ❑ Shift
- ❑ Selection
- ❑ Concatenation & Replication

Arithmetic Operators

- ❑ Commonly used in synthesis: + (add), - (subtract), * (multiply)
- ❑ Not commonly used in synthesis: / (divide), ** (power), % (modulo)
- ❑ Binary Expressions: $a + b$, $a - b$, $a * b$
- ❑ Unary Expressions: $+b$, $-a$
- ❑ Specifying constant operands
 - $a + 12$: add integer 12 to a
 - $a + 16'd12$: add a 16-bit integer 12 to a

General Rules for Arithmetic Precision

- ❑ Assignments will not lose precision if the target is large enough
 - If a and b are 15 bit, and c is 16 bit, then $c = a + b$ will not lose precision

- ❑ Assignments will lose precision if the target is not large enough
 - If a and b are 15 bit, and c is 8 bit, then $c = a + b$ captures the 8 lsb of the addition

- ❑ Standalone expressions *may* lose precision
 - If a and b are 15 bit, then the standalone expression $a + b$ uses 15 bit (max wordlength over a and b), and thus may lose precision
 - Standalone expressions occur in some system calls like e.g. `$display("a+b=%h", a+b);`

Bitwise Operators

- ❑ $\&$ (and), $|$ (or), \sim (negate), \wedge (xor), $\wedge\sim$ (xnor) - also $\sim\wedge$
- ❑ Perform a bit-by-bit comparison.
If input is N-bit, then output is N-bit.
- ❑ Similar truth table as for gates

AND

$\&$	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x

OR


$ $	0	1	x	z
0	0	1	x	x
1	1	1	1	1
x	x	1	x	x
z	x	1	x	x

NOT

\sim	
0	1
1	0
x	x
z	x

Bitwise Operators

 
- Gate networks can be written as expressions with bitwise operators



```
assign q = ~(a | (d | ~(b & c)));
```

Bitwise Operators

 - How to model gates-with-delays in expressions ?




```
assign q = #15 ~(a | (d | ~(b & c)));
```

???

Bitwise Operators

 - How to model gates-with-delays in expressions ?



Better: `assign q1 = #5 ~(b & c);`
`assign q2 = #5 q1 | d;`
`assign q = #5 q2 | a;`

Reduction Operator

- Condense all bits from a vector into a single bit using a specified logical operation

```
assign q1 = &a; // reduction-and
assign q2 = |b; // reduction-or
assign q3 = ^c; // reduction-xor
assign q4 = ~&d; // reduction-nand
assign q5 = ~|e; // reduction-nor
assign q6 = ~^f; // reduction-xor
```

- Similar to an N-input gate of the specified type, where N equals the wordlength of the operand

- Examples

- `| (4'b0001) =`
- `^ (4'b0111) =`
- `~| (2'b11) =`
- `& (2'b1x) =`

Reduction Operator

- Condense all bits from a vector into a single bit using a specified logical operation

```
assign q1 = &a; // reduction-and
assign q2 = |b; // reduction-or
assign q3 = ^c; // reduction-xor
assign q4 = ~&d; // reduction-nand
assign q5 = ~|e; // reduction-nor
assign q6 = ~^f; // reduction-xor
```

- Similar to an N-input gate of the specified type, where N equals the wordlength of the operand

- Examples

- $| (4'b0001) = 1$
- $^ (4'b0111) = 1$
- $\sim | (2'b11) = 0$
- $\& (2'b1x) = x$

Logical Operators

- ❑ || logical or, && logical and, ! logical not
- ❑ Outcome is a single bit: 1, 0, X
- ❑ When inputs are bitvectors:
 - Effect will be to reduce-OR operands, then perform a bitwise or/and/not corresponding to logical operation
 - Example
 - `(4'b1100) && (4'b0011) =`
 - `!(4'b100x) =`

Logical Operators

- ❑ || logical or, && logical and, ! logical not
- ❑ Outcome is a single bit: 1, 0, X
- ❑ When inputs are bitvectors:
 - Effect will be to reduce-OR operands, then perform a bitwise or/and/not corresponding to logical operation
 - Example
 - $(4'b1100) \ \&\& \ (4'b0011) = 1$
 - $!(4'b100x) = 1$

Relational Operators

- $a < b$, $a > b$, $a \leq b$, $a \geq b$

- Result is 1'b1 if true, 1'b0 if false, 1'bx if either a or b x

- signed comparison requires both a and b to be signed, otherwise unsigned comparison

- Note that the result of a signed comparison may be *different* than that of an unsigned comparison
 - $(4'bs1100 < 4'bs0111)$ but $(4'b1100 > 4'b0111)$



means: a two's complement constant

Relational operators - Equality tests

- $a == b$, $a != b$ tests a *logical equality*
 - will be 1 or 0 when a and b are fully known
 - when any bit of a or b is X, then the result is X

4'b101X != 4'b101X

- $a === b$, $a !== b$ tests a *case equality*
 - will always be 1 or 0
 - will include X's and Z's in the comparison

4'b101X === 4'b101X

Shift Operator

- ❑ Logical shift-left <<, Logical shift-right >>
- ❑ Arithmetic shift-left <<<, Arithmetic shift-right >>>

- ❑ Difference between logical and arithmetic shift:
 - Sign-bit is preserved on arithmetic shift-right of signed operand


Selection Operator

- ❑ Ternary operator ? :
- ❑ Shorthand notation for a multiplexer
 - `assign q = c ? a : b;`
- ❑ `c` is or-reduced.
 - If result is 1, then `q = a`.
 - If result is 0, then `q = b`.
 - If result is `x`, then `q` is combined, bit by bit, from `a` and `b`.

a	1110011
b	0000001
c	xxx00x1

❑ **Important operation! (see lecture 8)**

Selection operator

 

```
wire [7:0] d;  
wire [7:0] next_r;  
reg [7:0] r;  
  
wire c;  
  
always @(posedge clk)  
    r = next_r;  
  
assign next_r = c ? d : r;
```


Concatenation and Replication

- ❑ Form wire bundles from single wires or smaller wire bundles
 - $\{a, b[3:2], c\} = \{a, b[3], b[2], c\} =$ a 4-bit vector

- ❑ Concatenation can be replicated
 - $4\{a\} = \{a, a, a, a\}$
 - $\{a, 3\{b,c\}\} = \{a, b, c, b, c, b, c\}$

Operator Guessing Game

&&

|

~|

===

>@

5 { }

>=

Operator Guessing Game

&&

logical AND

|

bitwise/reduction OR

~|

reduction NOR

===

case equality

>@

???

5 { }


replication

>=

relational

Operator Precedence

+ - ! ~ & ~& ~ ^ ~^ ~^ (unary)	Highest precedence
**	
* / %	
+ - (binary)	
<< >> <<< >>>	
< <= > >=	
== != === !==	
& (binary)	
^ ~ ^ (binary)	
(binary)	
&&	
?: (conditional operator)	
{ } { }	Lowest precedence



Example 1

□ Write a 3-to-1 multiplexer

- Inputs D0, D1, D2 (4-bit)
- Select input S (2-bit)
- Output Y (4-bit)

S	Y
0	D0
1	D0
2	D1
3	D2

Example 1

□ Write a 3-to-1 multiplexer

- Inputs D0, D1, D2 (4-bit)
- Select input S (2-bit)
- Output Y (4-bit)

S	Y
0	D0
1	D0
2	D1
3	D2

```
module mux(Y, S, D0, D1, D2);  
    output [7:0] Y;  
    input  [1:0] S;  
    input  [7:0] D0, D1, D2;  
  
    assign Y = (S == 0) ? D0 :  
               (S == 1) ? D0 :  
               (S == 2) ? D1 : D2;  
  
endmodule
```

Example 1

□ Write a 3-to-1 multiplexer

- Inputs D0, D1, D2 (4-bit)
- Select input S (2-bit)
- Output Y (4-bit)

S	Y
0	D0
1	D0
2	D1
3	D2

```
module mux(Y, S, D0, D1, D2);  
    output [7:0] Y;  
    input  [1:0] S;  
    input  [7:0] D0, D1, D2;  
  
    assign Y = (S[1]) ? ((S[0]) ? D1 : D2) : D0;  
  
endmodule
```

Example 2

- Develop an 8-bit * 8-bit multiplier with 8-bit output, reflecting the 8 msb of the multiplication

Example 2

- Develop an 8-bit * 8-bit multiplier with 8-bit output, reflecting the 8 msb of the multiplication

```
module mul(Y, D0, D1);  
    output [7:0] Y;  
    input  [7:0] D0, D1;  
    wire   [15:0] mul_out;  
  
    assign mul_out = D0 * D1;  
    assign Y = mul_out[15:8];  
  
endmodule
```

Example 3

- Develop a rounding module with 8-bit input and 4-bit output. The 4-bit output reflects the *rounded* output of the 8 input bits. That is, if the 4 lsb of the input are bigger than 0111, then the output should be incremented.

Example 3

- Develop a rounding module with 8-bit input and 4-bit output. The 4-bit input captures the *rounded* output of the 8 input bits. That is, if the 4 lsb of the input are bigger than 0111, then the output should be incremented.

Rounding Trick: Add 1/2 lsb

1001	1100	8-bit input
0000	1000	add 1/2 lsb of 4-bit output
<hr/>		
1010		4-bit output

Example 3

- Develop a rounding module with 8-bit input and 4-bit output. The 4-bit input captures the *rounded* output of the 8 input bits. That is, if the 4 lsb of the input are bigger than 0111, then the output should be incremented.

```
module round(Y, D);  
    output [3:0] Y;  
    input  [7:0] D;  
  
    wire [7:0] A;  
  
    assign A = D + 4'b1000;  
    assign Y = A[7:4];  
  
endmodule
```

Example 4

- ❑ Develop a multiply-accumulate module with 40-bit accumulator and 2x16-bit inputs. The accumulator register is triggered on pos clock edge and has a negative asynchronous reset.

Example 4

- Develop a multiply-accumulate module with 40-bit accumulator and 2x16-bit inputs. The accumulator register is triggered on pos clock edge and has a negative asynchronous reset.

```
module mac(Y, clk, rst, D0, D1);
    output [39:0] Y;
    input  clk;
    input  rst;
    input  [15:0] D0, D1;
    reg    [39:0] Y;
    wire   [39:0] next_Y;


    always @(posedge clk or negedge rst)
        Y = (rst) ? next_Y : 0;

    assign next_Y = Y + (D0 * D1);

endmodule
```


Dataflow Expressions

 - ❑ Dataflow expressions are VERY powerful
- ❑ They can be used as a generic datapath modeling technique



Dataflow Expressions

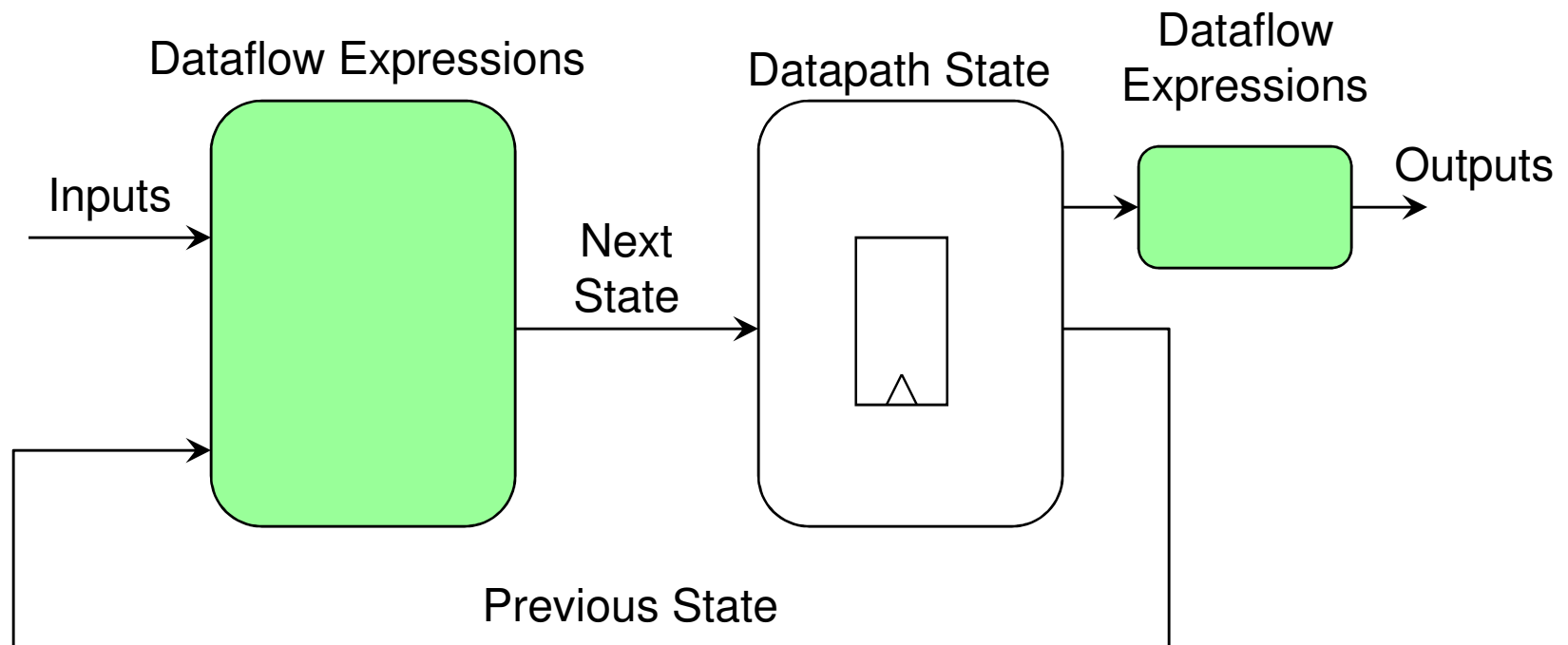- ❑ Looks like a Moore FSM
 - But, Dataflow Expressions can easily capture arithmetic. So, more flexibility than FSM.
 - See Lecture 8 - Multiplexed Datapaths



Summary

- ❑ Dataflow Modeling = Modeling using continuous assignments to nets.
- ❑ Rich set of operators available
 - Arithmetic, Logical, Relational, Bitwise, Reduction, Shift, Concatentation, Replication, Selection.
- ❑ Precision - expressions will not loose precision if their target is big enough.
- ❑ Delay - assignments follow inertial model.