
ECE 4514

Digital Design II

Spring 2008

Lecture 8:

Multiplexed Datapaths

A Methods Lecture

Patrick Schaumont

Today's topic

- ❑ An design method that uses dataflow modeling
- ❑ *A Design Method*
 - A canned sequence of steps, commands
 - Is easy to learn, easy to remember, easy to apply
 - Allows a designer to concentrate on *design* rather than on tools
- ❑ The method we will discuss is called


Multiplexed Datapaths

Multiplexed Datapaths - Disclaimer

- ❑ We will cover very specific Verilog modeling guidelines to build hardware modules called 'multiplexed datapaths'
- ❑ Not the only way to build hardware in Verilog
 - We will see other 'design methods' later
- ❑ But, if you use the 'multiplexed datapath' method, you **MUST** stick to the following guidelines

What is a multiplexed datapath ?

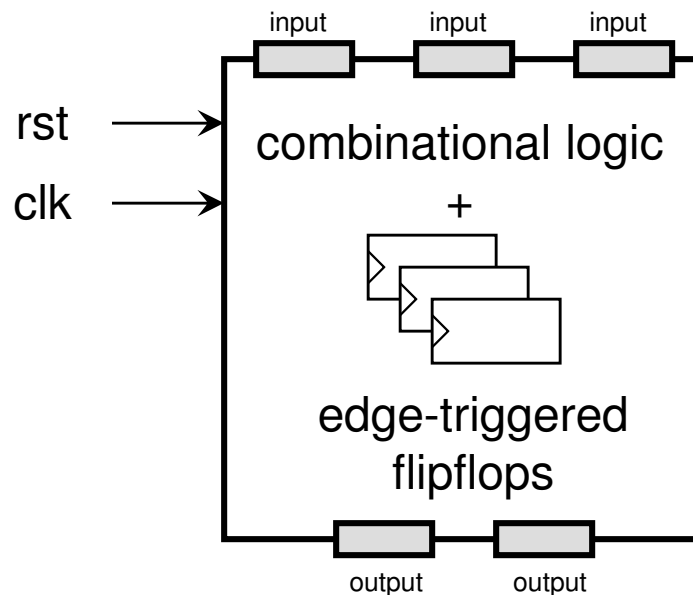- ❑ A module with a single clk and rst input
- ❑ Zero or more inputs, one or more outputs
- ❑ Edge-triggered flip-flops
- ❑ Outputs depend *only* on registers



Why single-clock ?

- ❑ A module with a single clk and rst input
- ❑ Zero or more inputs, one or more outputs
- ❑ Edge-triggered flip-flops
- ❑ Outputs depend *only* on registers

Simplifies generation and distribution of clock signal
in the implementation

Why edge-triggered flip-flops ?


- ❑ A module with a single clk and rst input
- ❑ Zero or more inputs, one or more outputs
- ❑ Edge-triggered flip-flops
- ❑ Outputs depend *only* on registers

A single type of storage module simplifies test
A single type of reset signal simplifies initialization

Why outputs depend only on registers ?


- ❑ A module with a single clk and rst input
- ❑ Zero or more inputs, one or more outputs
- ❑ Edge-triggered flip-flops
- ❑ Outputs depend *only* on registers

 Make sure that system-level delay, i.e. critical path, is just $\max(\text{module-level delay})$, not $\text{sum}(\text{module-level delay})$




$$\text{System Delay} = \max(\text{delay1}, \text{delay2}, \text{delay3}) + \text{routing_delay}$$

Template for a Multiplexed Datapath

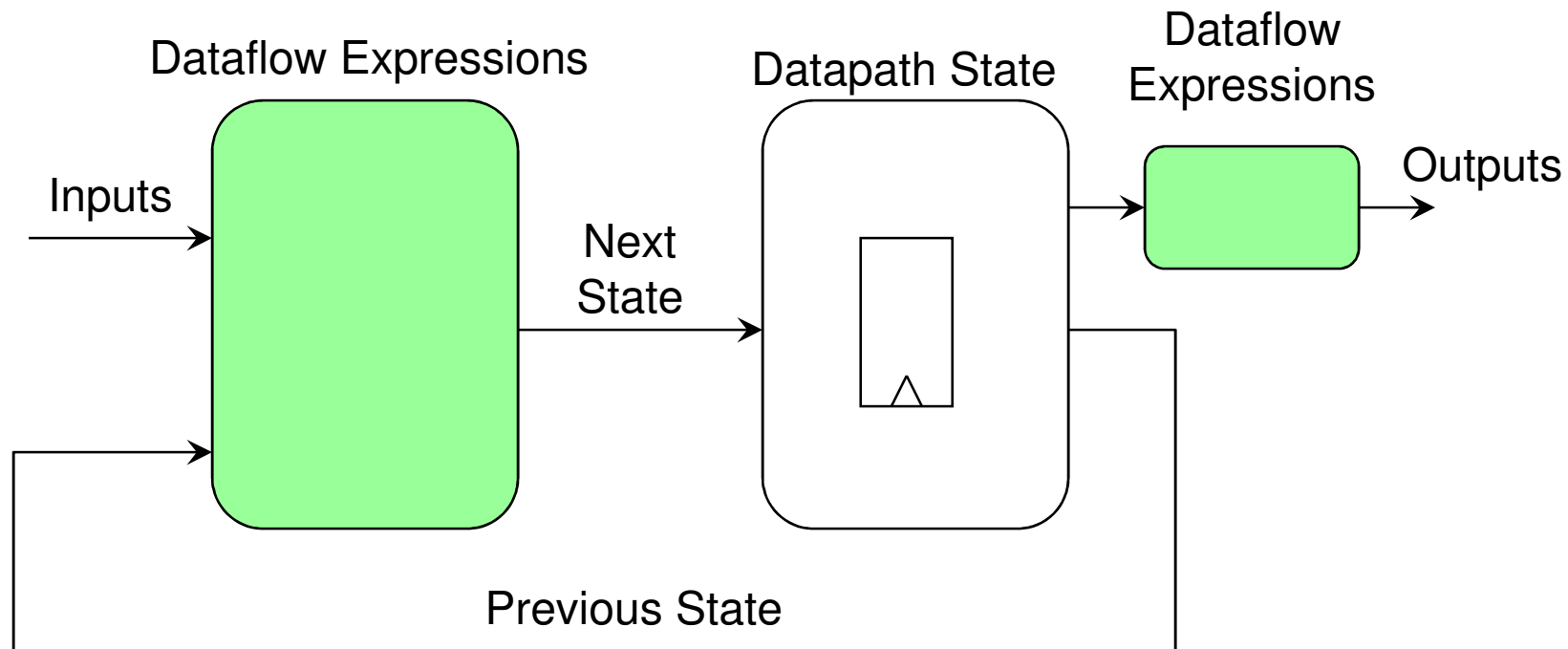


How to model an edge-triggered register
 
```
module a_module(q, rst, clk, d);  
    output q;  
    input rst;  
    input clk;  
    input d;  
    wire next_r1;  
    reg r1;  
  
    always @(posedge clk or negedge rst)  
        if (rst)  
            r1 = next_r1;  
        else  
            r1 = 0;  
  
    assign next_r1 = d;  
    assign q = r1;  
endmodule
```



How to model an edge-triggered register
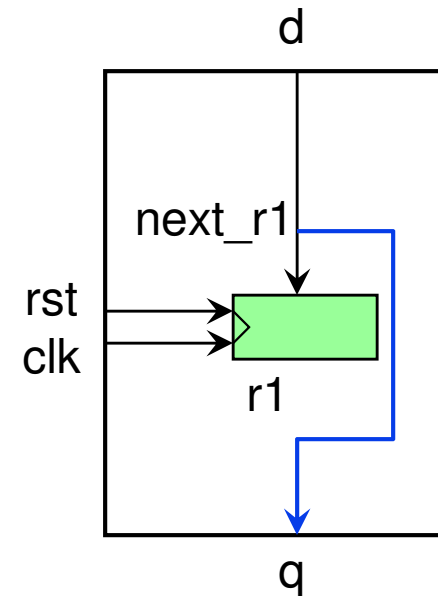
```
module a_module(q, rst, clk, d);  
    output q;  
    input rst;  
    input clk;  
    input d;  
    wire next_r1;  
    reg r1;  
  
    always @(posedge clk or negedge rst)  
        if (rst)  
            r1 = next_r1;  
        else  
            r1 = 0;  
  
    assign next_r1 = d;  
    assign q = next_r1;  
endmodule
```




No!

How to model two edge-triggered registers

```
module a_module(q, rst, clk, d);
    output q;
    input rst;
    input clk;
    input d;
    wire next_r1, next_r2;
    reg r1, r2;

    always @(posedge clk or negedge rst)
        if (rst) begin
            r1 = next_r1;
            r2 = next_r2;
        end else begin
            r1 = 0;
            r2 = 0;
        end
    end

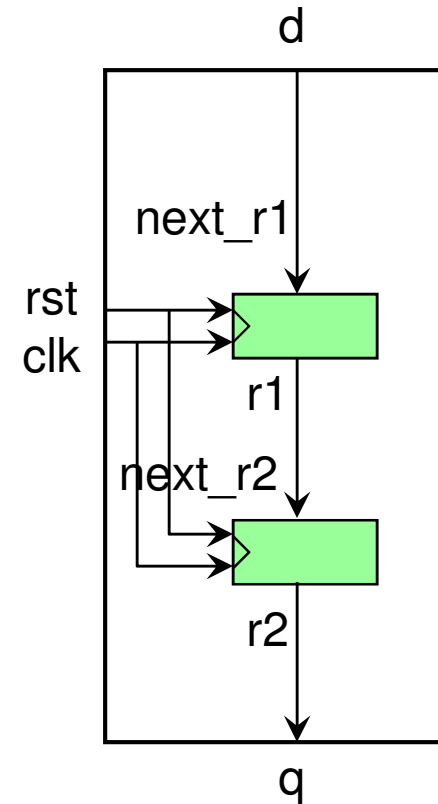    assign next_r1 = d;
    assign next_r2 = r1;
    assign q = r2;
endmodule
```




How to model two edge-triggered registers

```
module a_module(q, rst, clk, d);
  output q;
  input rst;
  input clk;
  input d;
  wire next_r1, next_r2;
  reg r1, r2;

  always @(posedge clk or negedge rst)
    if (rst) begin
      r1 = next_r1;
      r2 = next_r2;
    end else begin
      r1 = 0;
      r2 = 0;
    end

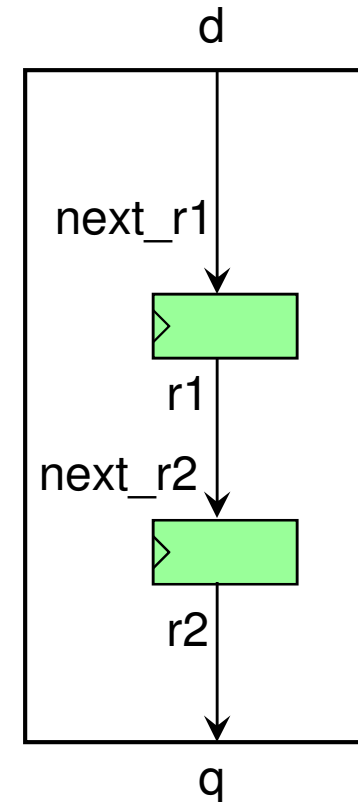
  assign next_r1 = d;
  assign next_r2 = r1;
  assign q = r2;
endmodule
```



**Will leave out drawing of clk net
and rst net from now**


Add two inputs, capture in a register
 
```
module a_module(q, rst, clk, d1, d2);  
    output q;  
    input rst;  
    input clk;  
    input d1, d2;  
  
    wire next_r1;  
    reg r1;  
  
    always @(posedge clk or negedge rst)  
        if (rst)  
            r1 = next_r1;  
        else  
            r1 = 0;  
  
    assign next_r1 = d1 + d2;  
    assign q = r1;  
endmodule
```




Take a close look at the addition
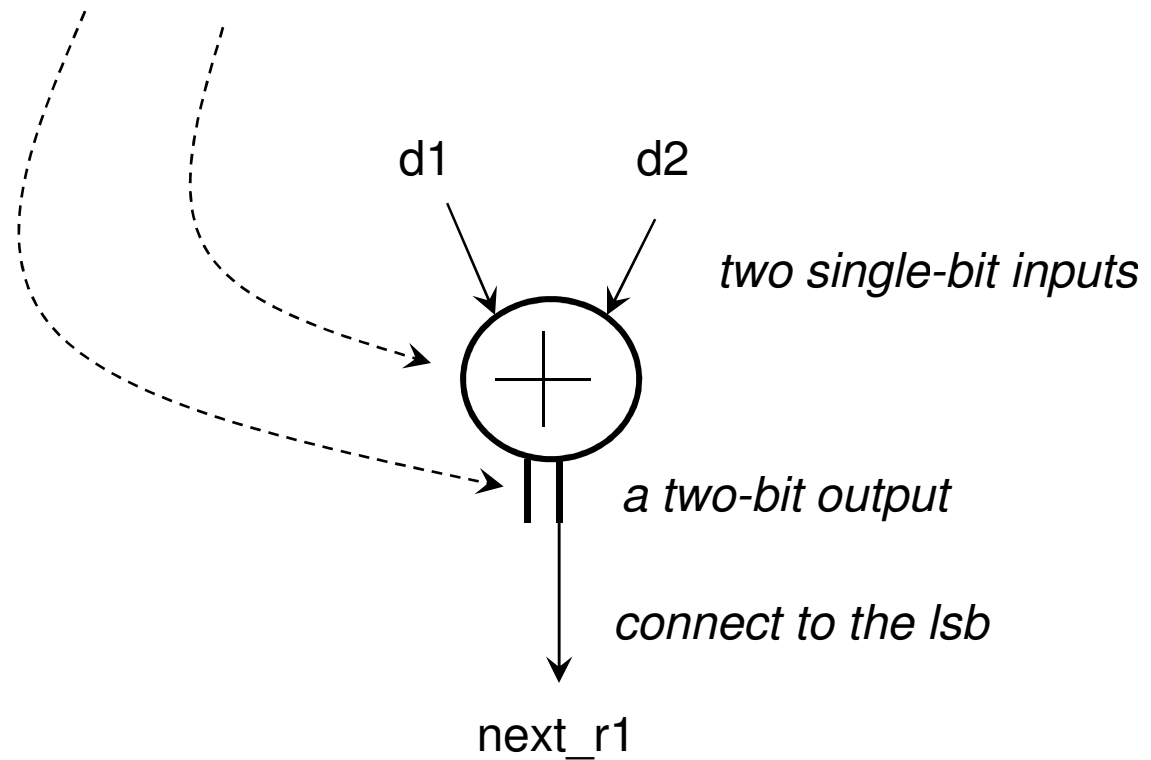
```
input d1, d2;  
wire next_r1;  
  
assign next_r1 = d1 + d2;
```



How to get the carry bit ?
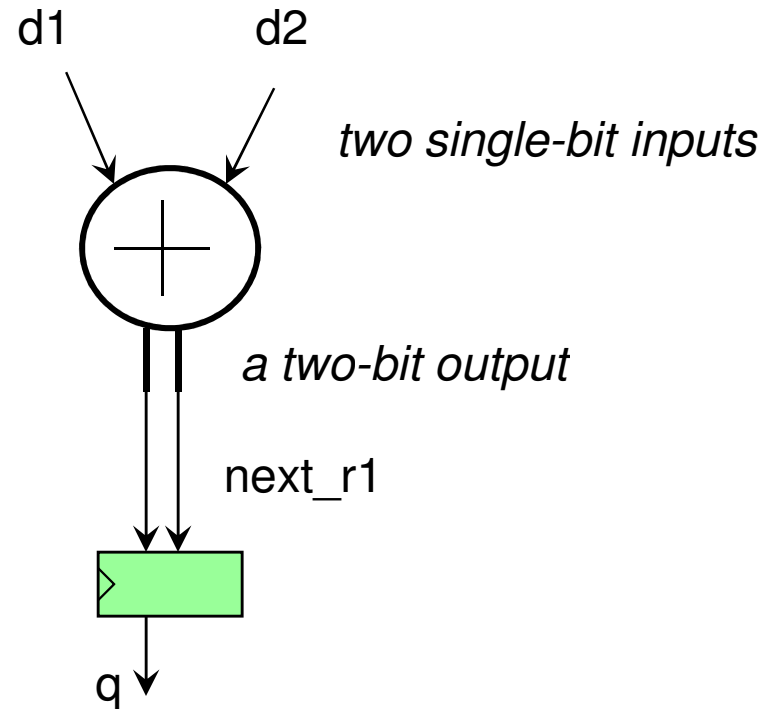
```
input d1, d2;  
wire [1:0] next_r1;  
reg [1:0] r1;  
  
assign next_r1 = d1 + d2;  
assign q = r1[1];
```



Not so good, will require a two-bit register

Better solution

```
module get_carry(q, rst, clk, d1, d2);
    output q;
    input rst;
    input clk;
    input d1, d2;


    wire next_r1;
    reg r1;
    wire dummy;

    always @(posedge clk or negedge rst)
        if (rst)
            r1 = next_r1;
        else
            r1 = 0;


    assign {next_r1, dummy} = d1 + d2;
    assign q = r1;
endmodule
```


How to model an multiplexed register

 
```
module a_module(q, rst, clk, d, c);  
    output q;  
    input rst;  
    input clk;  
    input d, c;  
    wire next_r1;  
    reg r1;  
  
    always @(posedge clk or negedge rst)  
        if (rst)  
            r1 = next_r1;  
        else  
            r1 = 0;  
  
    assign next_r1 = c ? d : r1;  
    assign q = r1;  
endmodule
```



Multiplexer allows controlled update

 


 - ❑ Eg. d is only valid once every three clock cycles
- ❑ Capture d in register only when $c = 1$
- ❑ Otherwise, retain value of q
- ❑ c is a 'logical' clock signal (in contrast to the physical clock signal clk)




Muxed registers are key to Muxed Datapath

Overall Idea

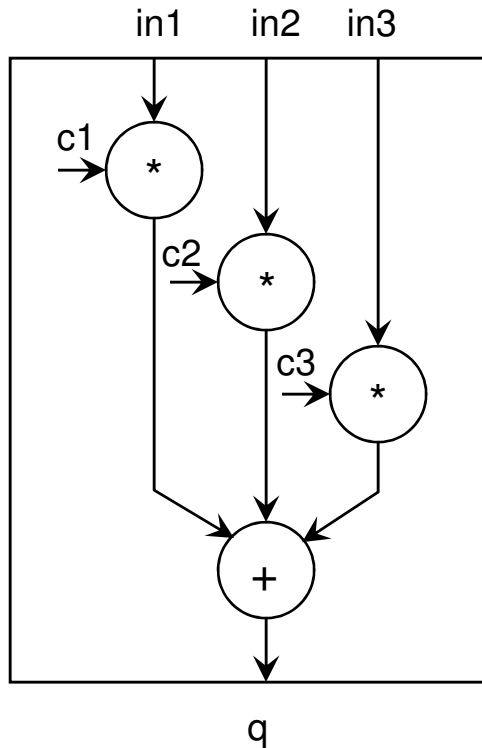


 
One clock cycle
3 Multiplier
2 Adders (2-input)





Three clock cycles
1 Multiplier
1 Adder
 n Multiplexers

Muxed registers are key to Muxed Datapath

Overall Idea

 
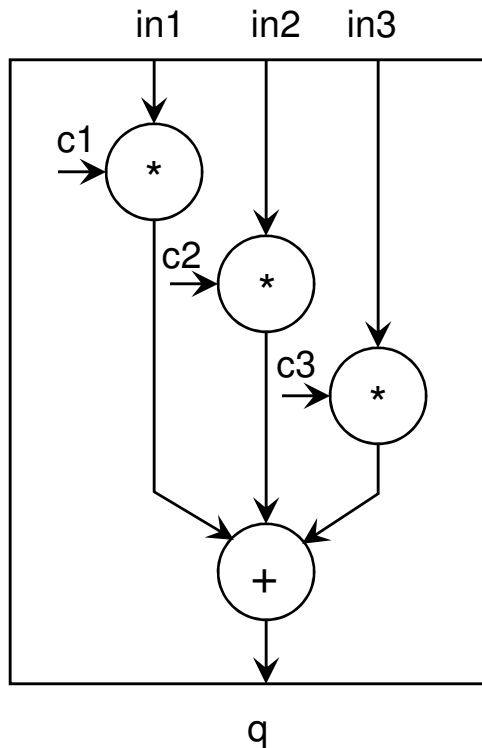


AREA
TIME
TRADEOFF

  

Muxed registers are key to Muxed Datapath

Overall Idea

 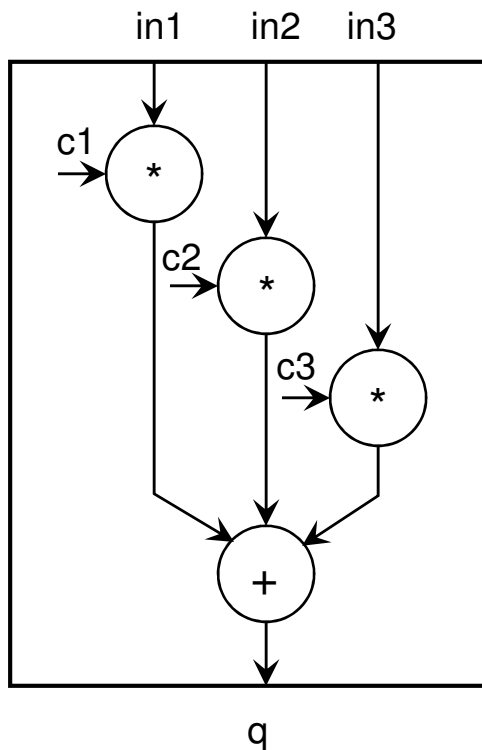

Pitfall #1: Time doesn't scale linearly

Time = cycles * period

Period ~ Critical Path

Critical Path_{non-muxed} >> Critical Path_{muxed}


Pitfall #2: Area doesn't scale linearly

Area = Operations + Overhead

Overhead ~ muxes + regs

#-Muxes_{muxed} >> #-Muxes_{non-muxed}

Let's try this

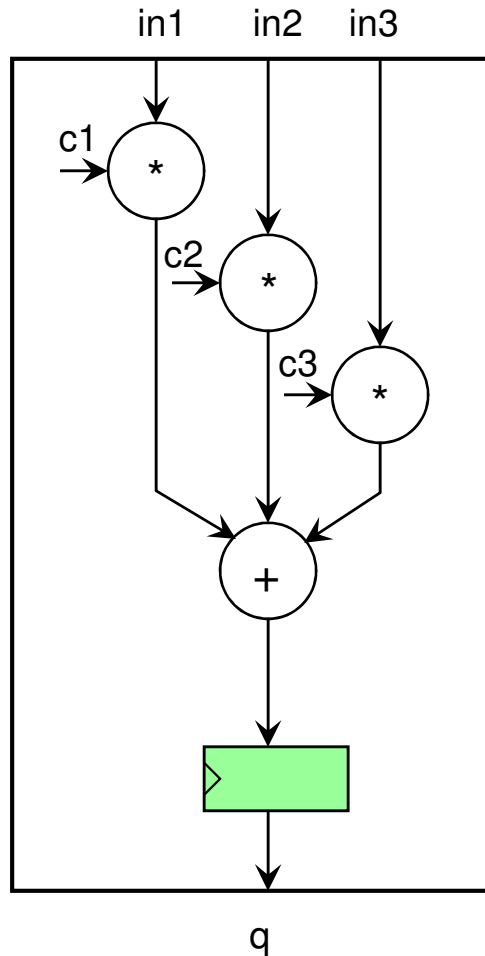

```
module vecmul(q, rst, clk, in1, in2, in3);
    output [7:0] q;
    input rst, rst;
    input [7:0] in1, in2, in3;
    parameter c1 = 8'd2;
    parameter c2 = 8'd4;
    parameter c3 = 8'd6;


    wire next_r1;
    reg r1;

    always @(posedge clk or negedge rst)
        if (rst)
            r1 = next_r1;
        else
            r1 = 0;

    assign next_r1 = c1 * in1 +
                    c2 * in2 +
                    c3 * in3;

    assign q = r1;
endmodule
```

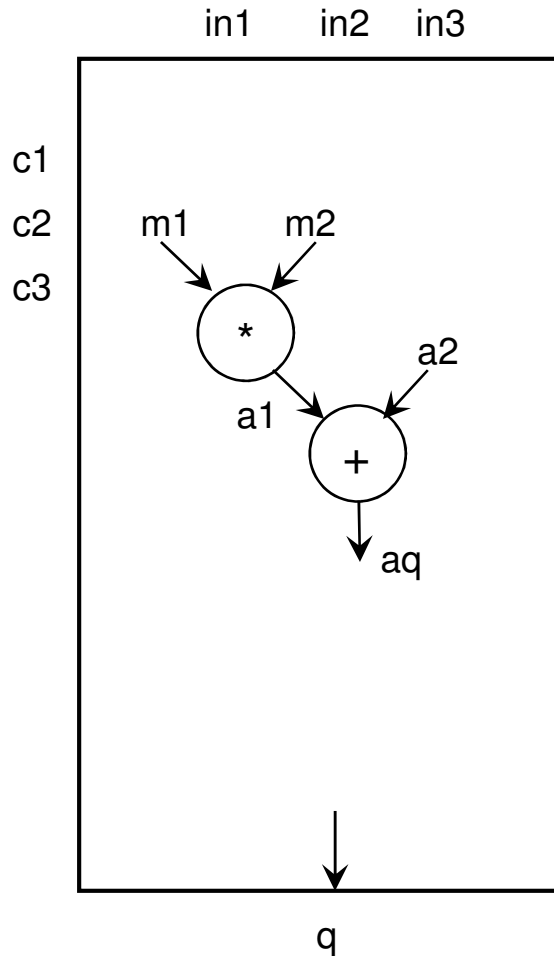Now, we reduce the number of *, + operations



```
module vecmul(q, rst, clk, in1, in2, in3);
    output [7:0] q;
    input rst, rst;
    input [7:0] in1, in2, in3;
    parameter c1 = 8'd20;
    parameter c2 = 8'd40;
    parameter c3 = 8'd60;


    wire next_r1;
    reg r1;

    wire [7:0] m1, m2;
    wire [10:0] a1, a2, aq; // 16-bit worst case

    assign aq = a2 + a1;
    assign a1 = m1 * m2;

endmodule
```

Add muxes on m1, m2. Add control input.

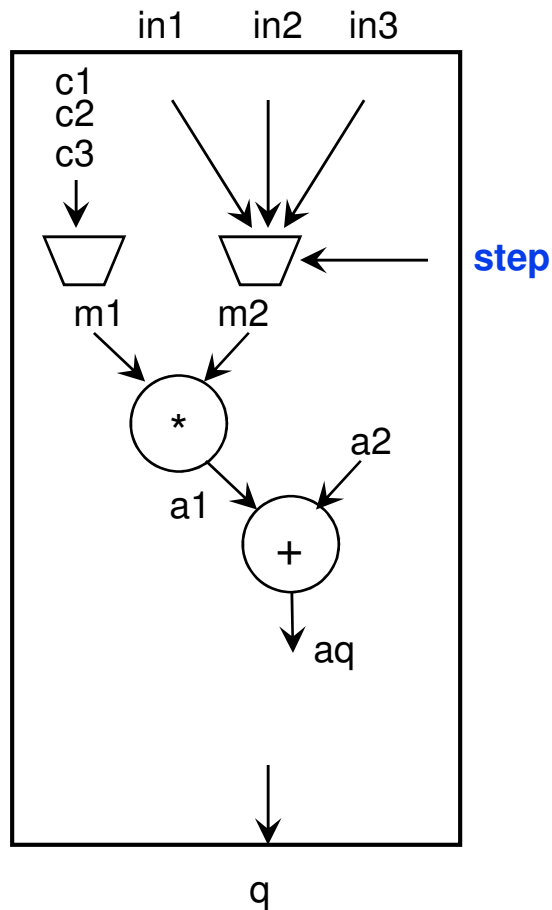

```
module vecmul(q, rst, clk, in1, in2, in3, step);
    output [7:0] q;
    input rst, rst;
    input [7:0] in1, in2, in3;
    input [1:0] step;
    parameter c1 = 8'd20;
    parameter c2 = 8'd40;
    parameter c3 = 8'd60;

    wire next_r1;
    reg r1;


    wire [7:0] m1, m2;
    wire [10:0] a1, a2, aq; // 16-bit worst case

    assign aq = a2 + a1;
    assign a1 = m1 * m2;
    assign m1 = (step == 0) ? c1 :
                (step == 1) ? c2 : c3;
    assign m2 = (step == 0) ? in1 :
                (step == 1) ? in2 : in3;

endmodule
```

step is a control input

Add muxes on a2. Add accumulator reg.

 

```

module vecmul(q, rst, clk, in1, in2, in3, step);
  output [7:0] q;
  input rst, rst;
  input [7:0] in1, in2, in3;
  input [1:0] step;
  parameter c1 = 8'd20;
  parameter c2 = 8'd40;
  parameter c3 = 8'd60;

  wire next_r1;
  reg r1;

  wire [7:0] m1, m2;
  wire [10:0] a1, a2, aq; // 16-bit worst case
  reg [10:0] aq_reg;


  always @(posedge clk) aq_reg = aq;

  assign aq = a2 + a1;
  assign a1 = m1 * m2;
  assign m1 = (step == 0) ? c1 :
              (step == 1) ? c2 : c3;
  assign m2 = (step == 0) ? in1 :
              (step == 1) ? in2 : in3;
  assign a2 = (step == 0) ? 0 : aq_reg;

endmodule

```

System Interconnect.

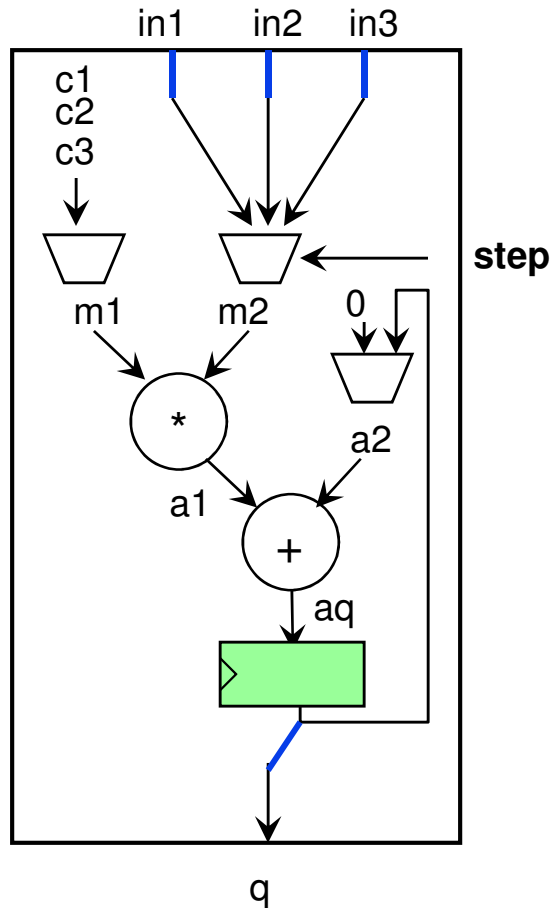

```

module vecmul(q, rst, clk, in1, in2, in3, step);
  output [7:0] q;
  input rst, rst;
  input [7:0] in1, in2, in3;
  input [1:0] step;
  parameter c1 = 8'd20;
  parameter c2 = 8'd40;
  parameter c3 = 8'd60;

  wire next_r1;
  reg r1;


  wire [7:0] m1, m2;
  wire [10:0] a1, a2, aq; // 16-bit worst case
  reg [10:0] aq_reg;

  always @(posedge clk) aq_reg = aq;

  assign aq = a2 + a1;
  assign a1 = m1 * m2;
  assign m1 = (step == 0) ? c1 :
              (step == 1) ? c2 : c3;
  assign m2 = (step == 0) ? in1 :
              (step == 1) ? in2 : in3;
  assign a2 = (step == 0) ? 0 : aq_reg;
  assign q = aq_reg;
endmodule

```

Simple Optimizations

 

```

module vecmul(q, rst, clk, in, step);
    output [7:0] q;
    input rst, rst;
    input [7:0] in;
    input [1:0] step;
    parameter c1 = 8'd20;
    parameter c2 = 8'd40;
    parameter c3 = 8'd60;

    wire next_r1;
    reg r1;


    wire [7:0] m1;
    wire [10:0] a1, a2, aq; // 16-bit worst case
    reg [10:0] aq_reg;

    always @(posedge clk) aq_reg = aq;

    assign aq = a2 + a1;
    assign a1 = m1 * in;
    assign m1 = (step == 0) ? c1 :
                (step == 1) ? c2 : c3;
    assign a2 = (step == 0) ? 0 : aq_reg;
    assign q = aq_reg;
endmodule

```

Result of 'Muxed Datapath'

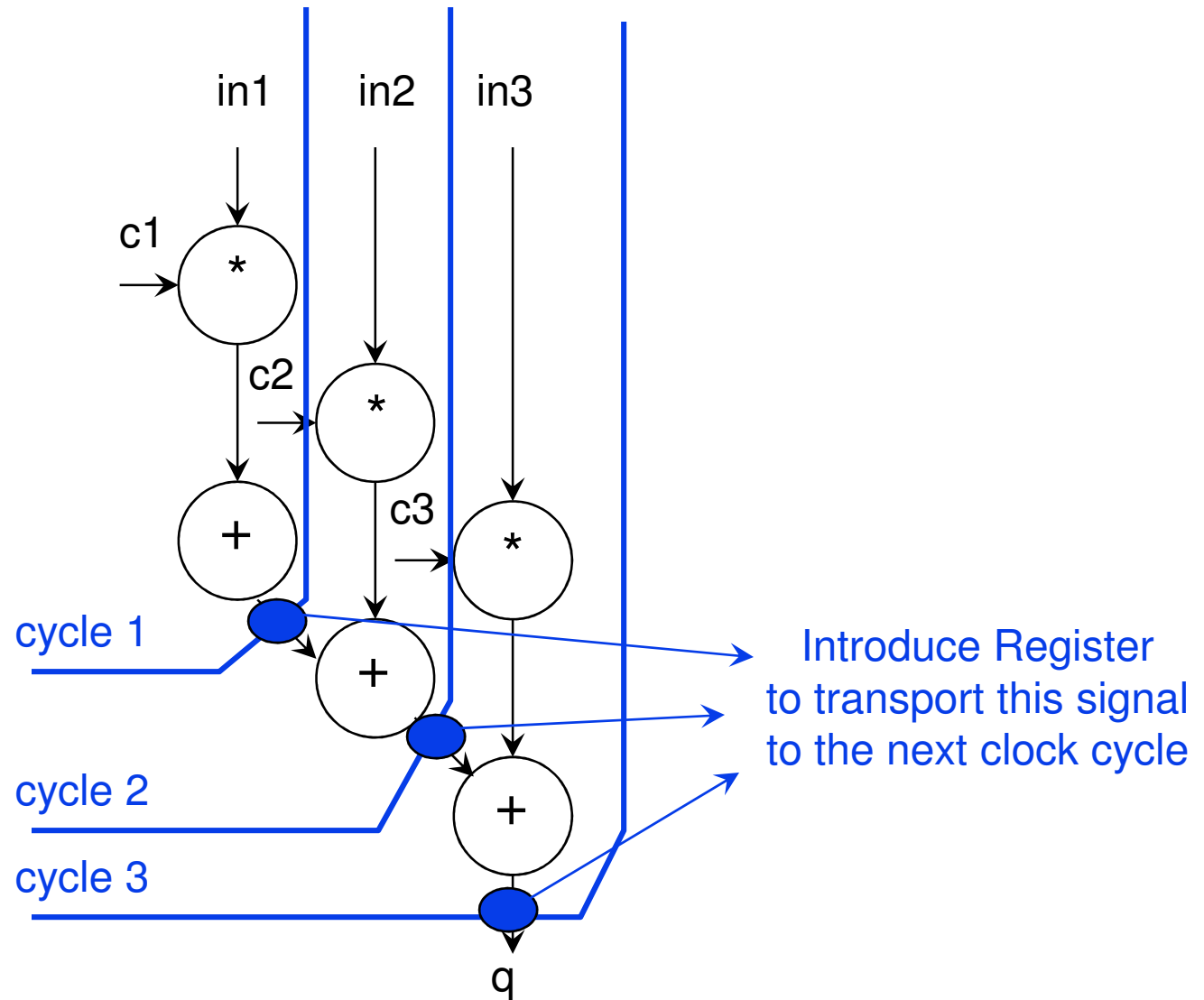

Automatic Generation of Muxed Datapaths


- ❑ There exists elaborate theory that will find the 'best' way of partitioning an operation graph
- ❑ It involves
 - **Allocation**: Deciding how much operators you need to implement all of the operations
 - **Assignment**: Deciding which operation will be execute on which operator
 - **Scheduling**: Decide the clock cycle during which an operation must be executed
- ❑ But in this course, we will work from you ingenuity

Can we design FSM using same Verilog Style?

- Yes!
- We can generate the *step* signal locally, if we want.
- We can also model an existing FSM using multiplexers and assign expressions.
 - Need to perform state assignment manually
 - Next-state encoding can be done with assign expressions

Example: Design this FSM as muxed datapath


Inputs i_1, i_2
Outputs o_1, o_2, o_3

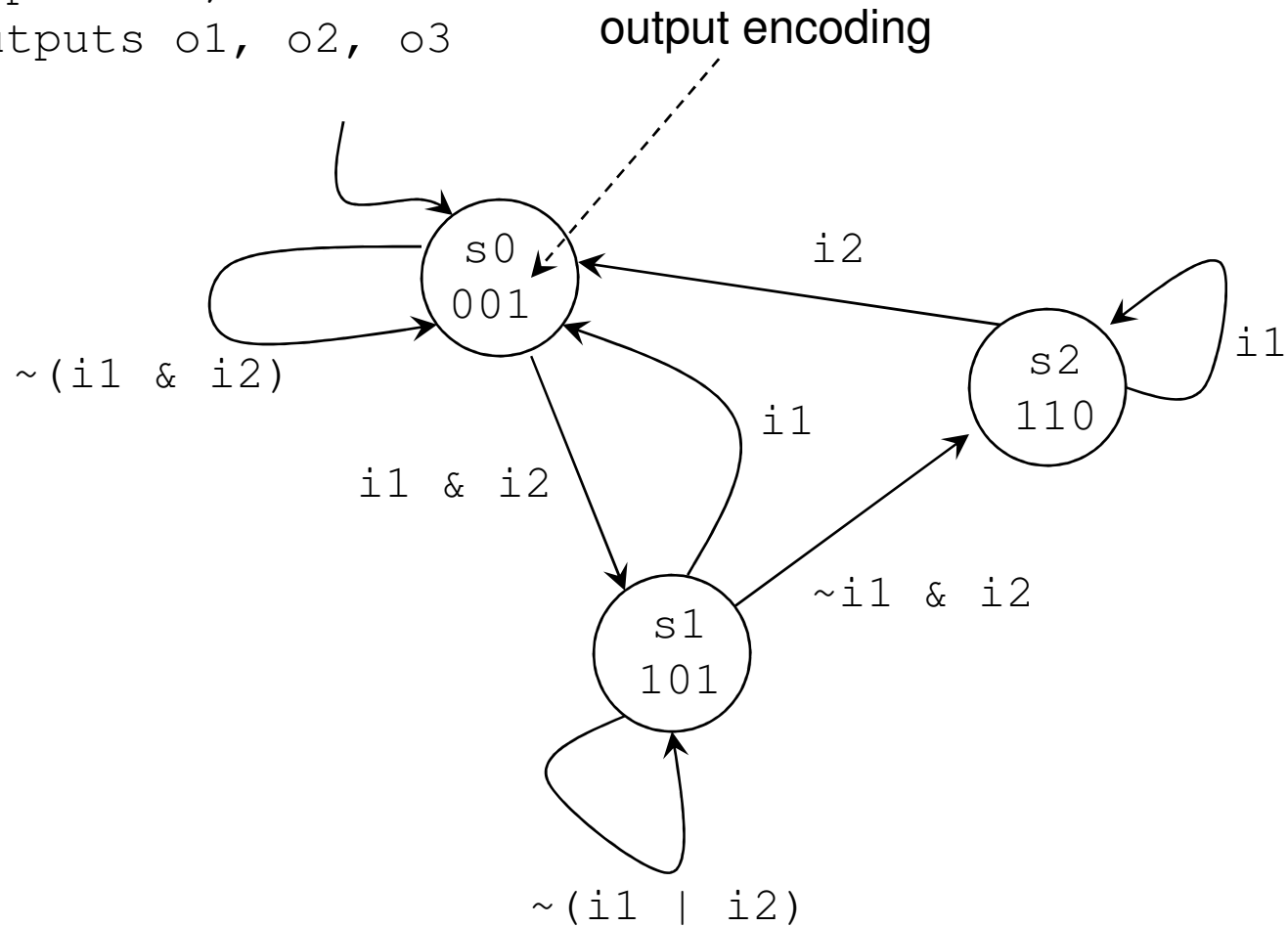

Example: Design this FSM as muxed datapath

Inputs i_1, i_2


Outputs o_1, o_2, o_3

 

Always verify if state transitions are complete

Example: Design this FSM as muxed datapath


Inputs i_1, i_2
Outputs o_1, o_2, o_3

 

Example: Design this FSM as muxed datapath

Inputs i_1, i_2


Outputs o_1, o_2, o_3

 

**OK, $\sim(i_1 \ \& \ i_2) \ | \ (i_1 \ \& \ i_2) = 1$
and $\sim(i_1 \ \& \ i_2) \ \& \ (i_1 \ \& \ i_2) = 0$**


Example: Design this FSM as muxed datapath

Inputs i_1, i_2
Outputs o_1, o_2, o_3

 

Example: Design this FSM as muxed datapath

Inputs i_1, i_2
Outputs o_1, o_2, o_3

 


OK, since $\sim(i_1 | i_2) = \sim i_1 \& \sim i_2$,

the all transitions are covered exactly


Example: Design this FSM as muxed datapath

Inputs i_1, i_2
Outputs o_1, o_2, o_3

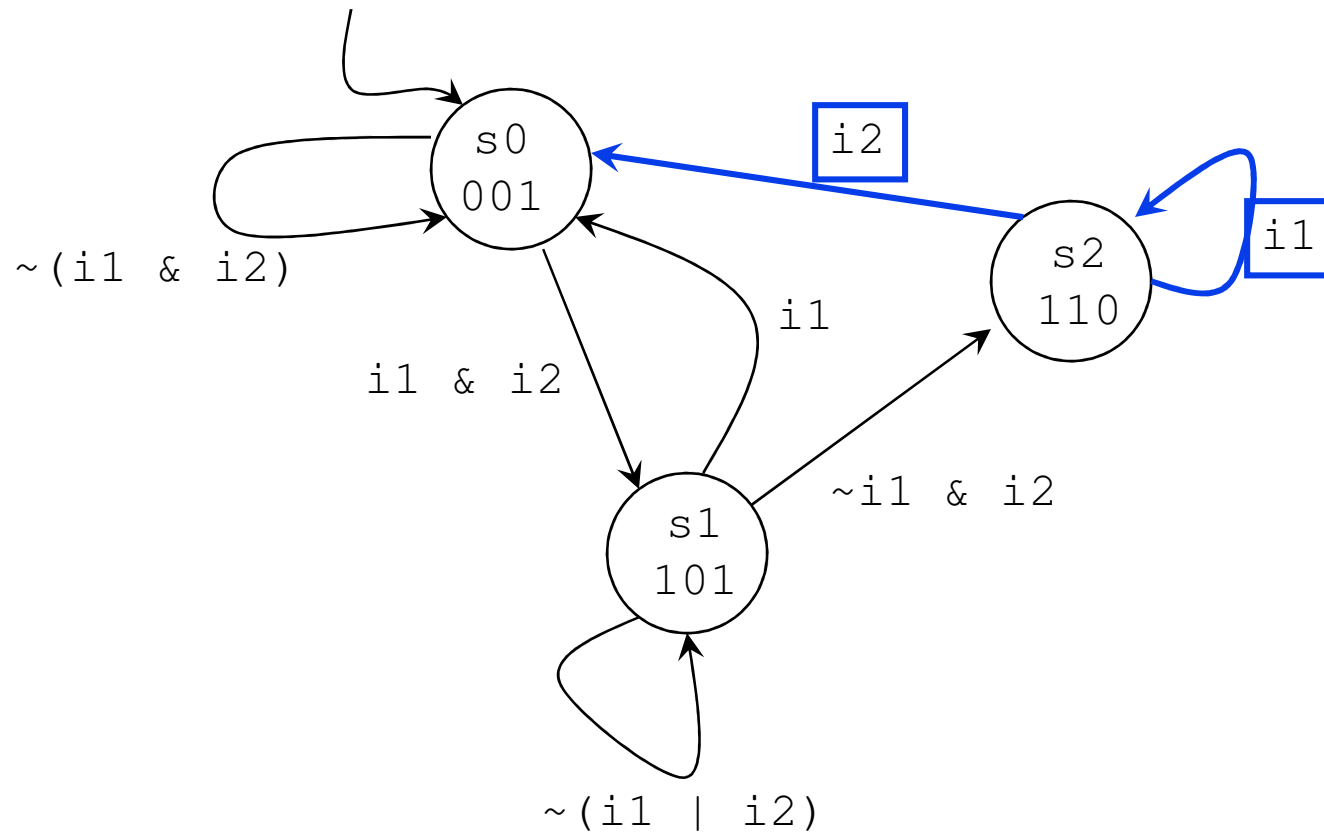

Example: Design this FSM as muxed datapath

Inputs i_1, i_2
Outputs o_1, o_2, o_3

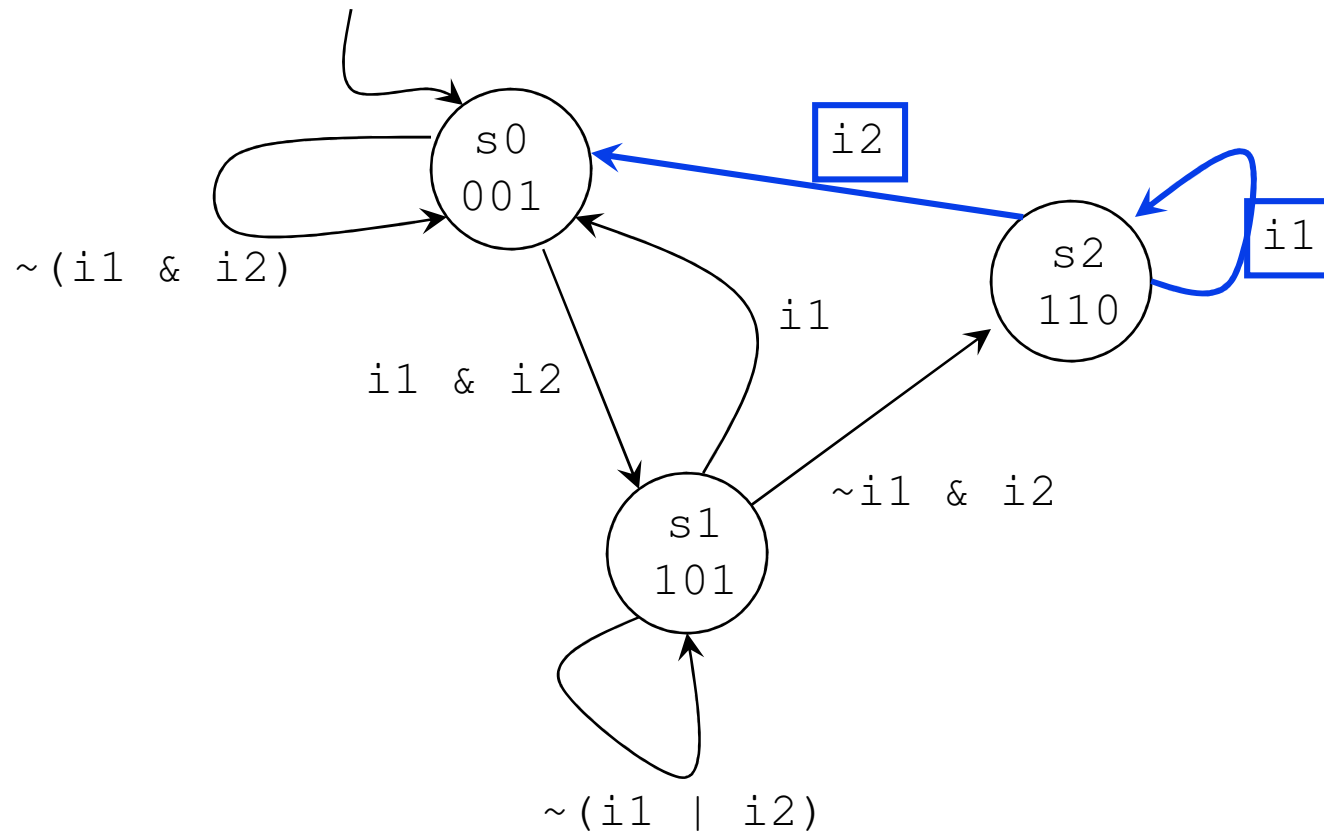


Ambiguous! What if $i_1 = 1$ and $i_2 = 1$?

What if $i_1 = 0$ and $i_2 = 0$?

Example: Design this FSM as muxed datapath

Inputs i_1, i_2
Outputs o_1, o_2, o_3

 


**Resolved (by modifying conditions -
required change will depend on the application)**

Example: Design this FSM as muxed datapath

Inputs i_1, i_2

Outputs o_1, o_2, o_3

 

Example: Design this FSM as muxed datapath


```
module fsm(o, rst, clk, i);
    output [2:0] o;
    input rst;
    input clk;
    input [1:0] i;
    parameter s0 = 3'b001, s1 = 3'b101, s2 = 3'b110;
    reg [2:0] o; // state register
    wire [2:0] next_o;

    // rst not shown in always block
    always @(posedge clk)
        if (rst)
            o = next_o;
        else
            o = s0;

    assign next_o = (o == s0) ? (&i ? s1 : s0) :
                    (o == s1) ? (i1 ? s1 : (i2 ? s2 : s1)) :
                    (o == s2) ? (i2 ? s0 : s2);

endmodule
```

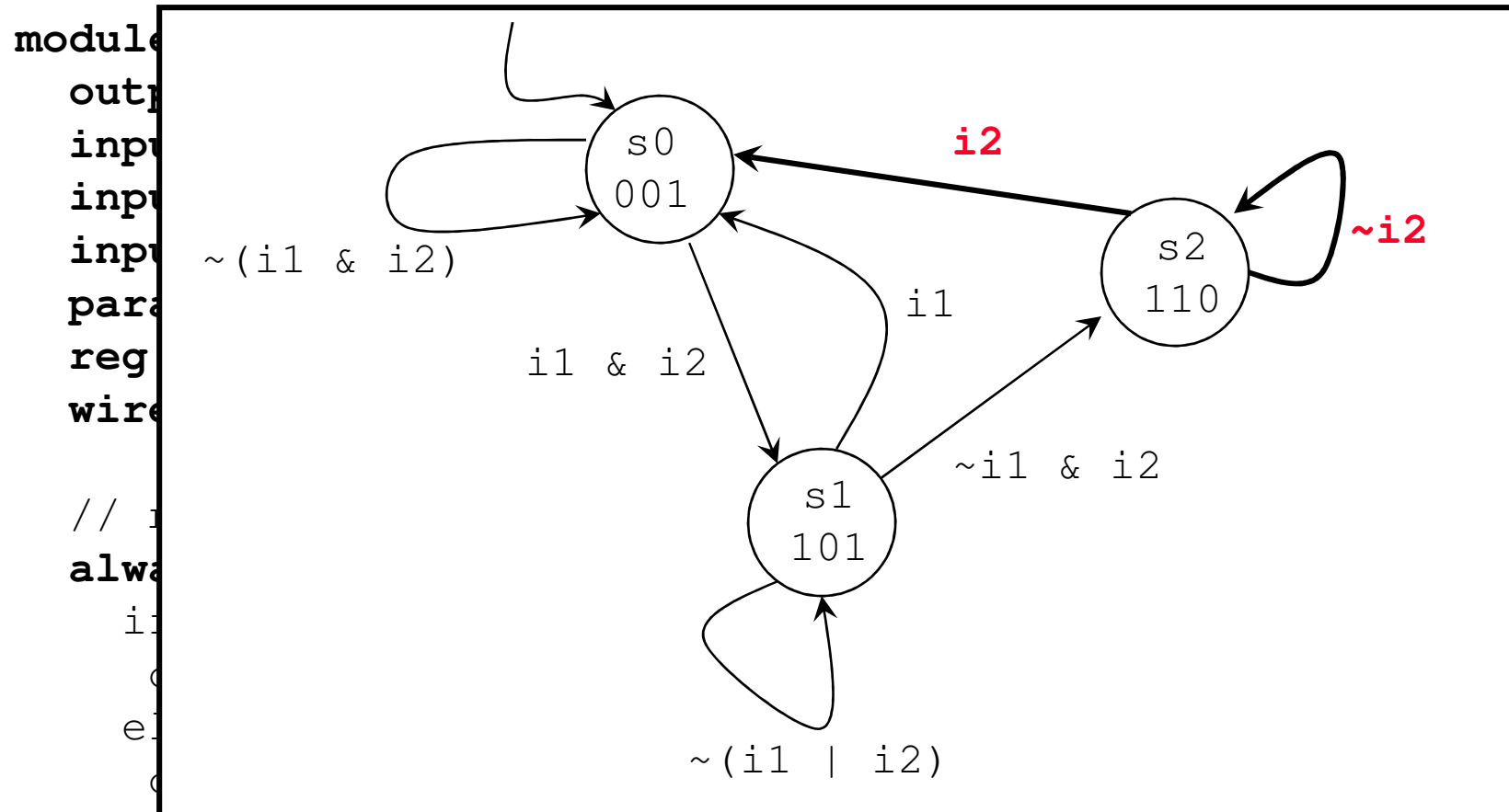
Example: Design this FSM as muxed datapath



```
assign next_o = (o == s0) ? (&i ? s1 : s0) :
                 (o == s1) ? (i1 ? s1 : (i2 ? s2 : s1)) :
                 (o == s2) ? (i2 ? s0 : s2);
```

endmodule

Note that FSM can be given by table

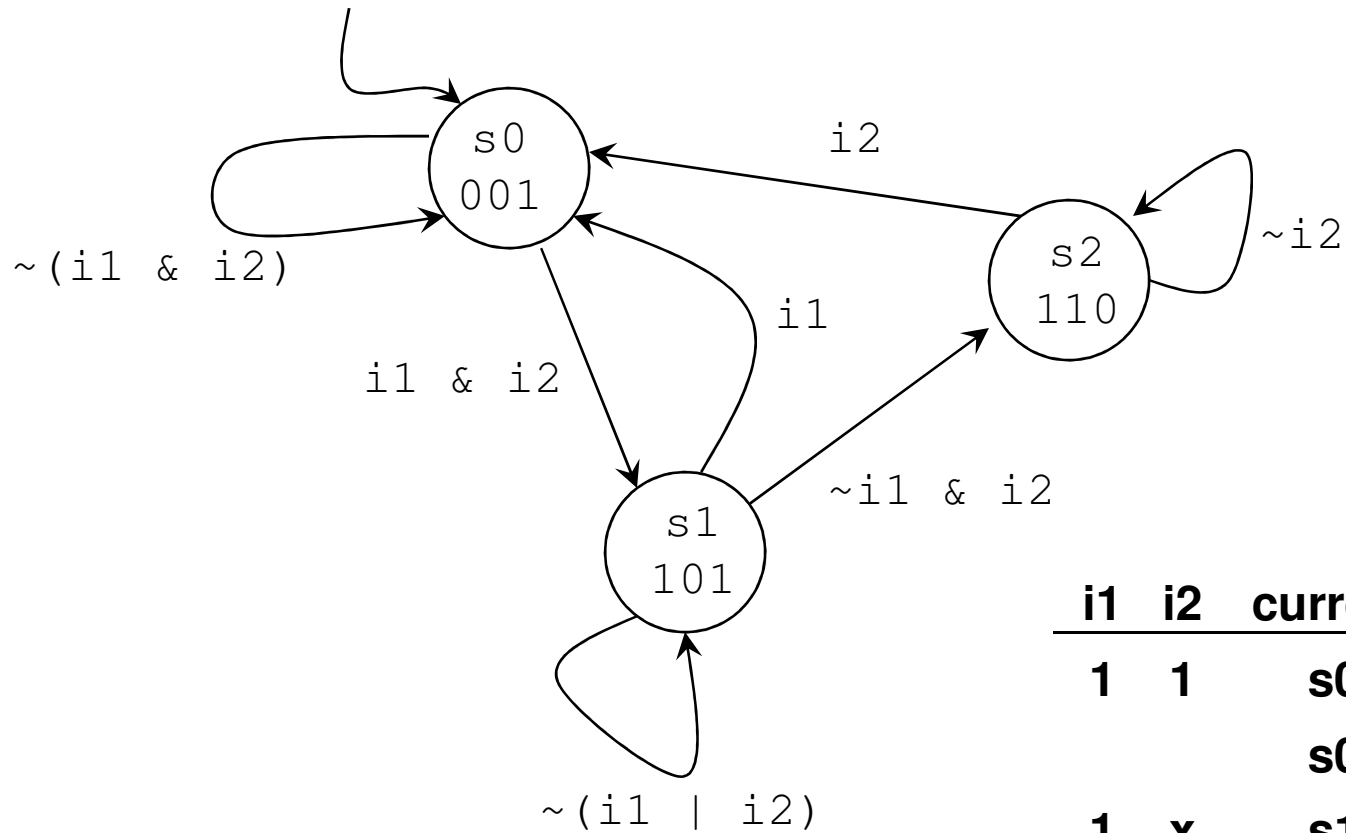

i1	i2	current	next	out
1	1	s0	s1	001
		s0	s0	001
1	x	s1	s0	101
0	1	s1	s2	101
0	0	s1	s1	101
x	0	s2	s2	110
x	1	s2	s0	110

Summary

□ Multiplexed Datapath

- Model Registers with reg and wire
- Model Datapath logic using assign expressions
- Use multiplexers to control register update

